

### Exercise 4.4

- a) Plot the  $i_A$  vs.  $v_A$  characteristics for the nonlinear network shown in Figure 4.3. Assume the diode is ideal.

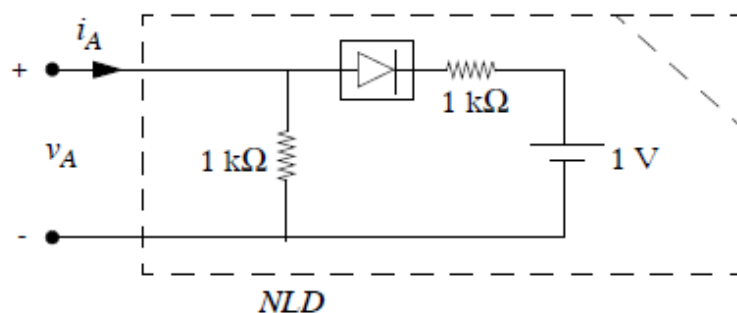


Figure 4.3:

- b) The nonlinear network from part (a) is connected as shown in Figure 4.4. Draw the load line on your  $i - v$  characteristic from part (a), and find  $i_T$ .

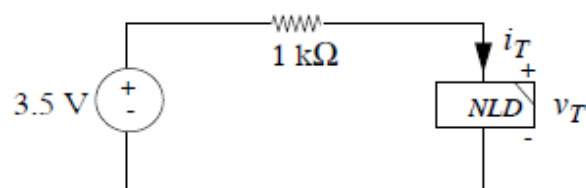


Figure 4.4:

Solution:

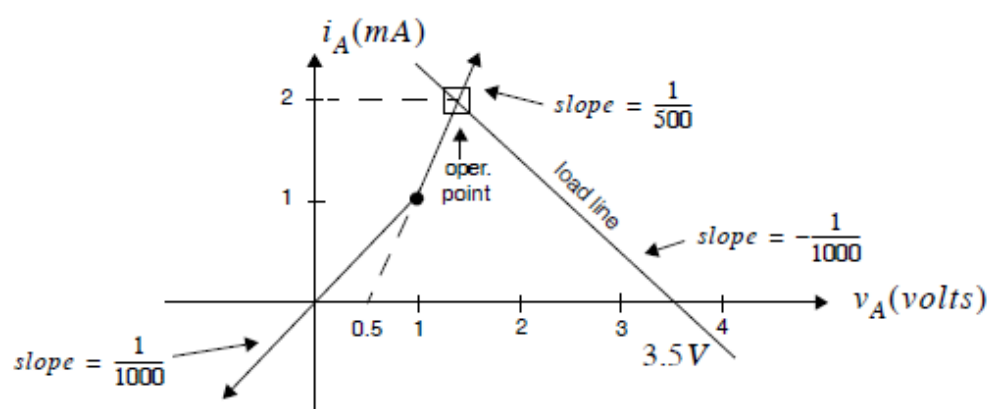


Figure 4.5:

a)  $v_A > 1$ : Diode on

$$i_A = \frac{v_A}{1000 \parallel 1000}$$

$v_A < 1$ : Diode off

$$i_A = \frac{v_A}{1000}$$

b) Load line:

KVL:

$$3.5V - i_T (1000) - v_T = 0$$

$$i_T = \frac{3.5 - v_T}{1000}$$

Operating point occurs at intersection, and we find that

$$i_T = 2mA$$

ANS:: (b)  $i_T = 2mA$

**Exercise 4.6** For the circuit in Figure 4.7, find the input characteristic,  $i$  versus  $v$ , and the transfer characteristic  $i_2$  versus  $v$ .  $I$  is fixed and positive. Express your results in graphs, labeling all slopes, intercepts, and coordinates of any break points.

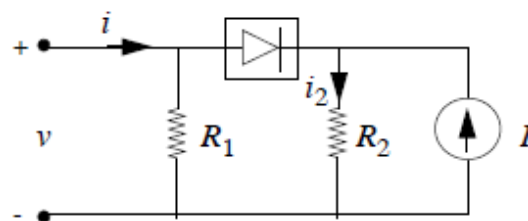




Figure 4.7:

Solution)

When diode is on,

$$i_2 = \frac{v}{R_2}$$

$$i = \frac{V(R_1 + R_2)}{R_1 R_2}$$

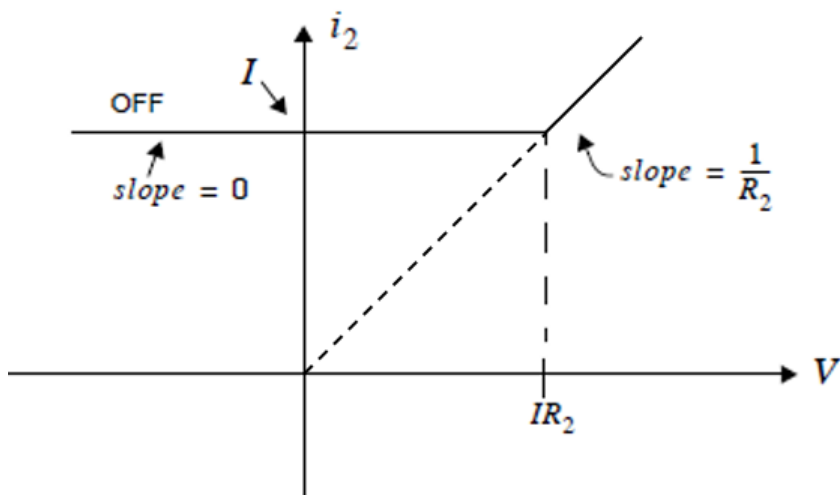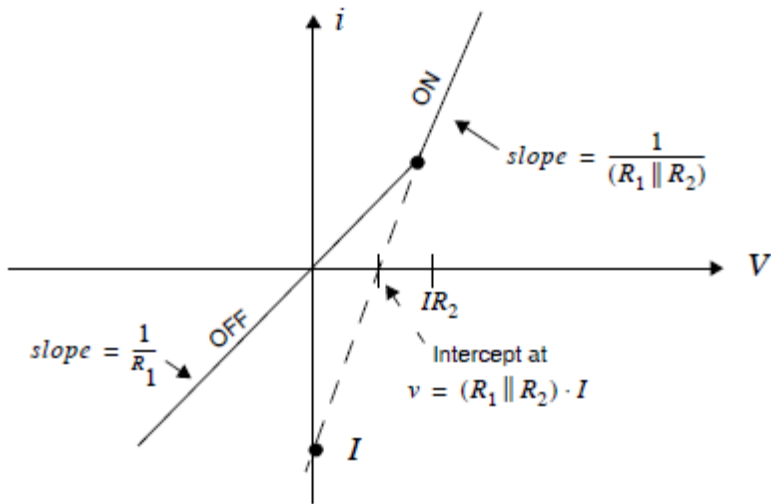

**Problem 4.11** This problem concerns the circuit illustrated in Figure 4.29:

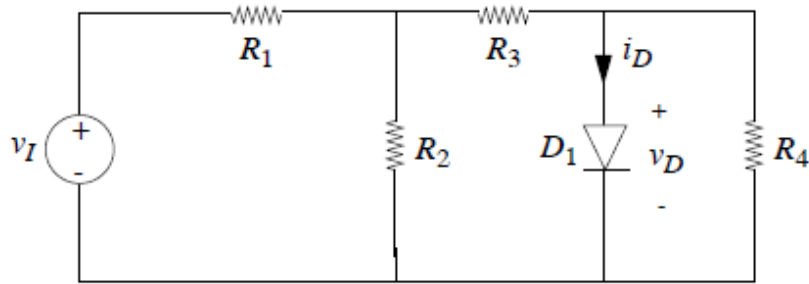


Figure 4.29:

$$R_1 = 1.0k\Omega \quad R_2 = 1.0k\Omega \quad R_3 = 0.5k\Omega \quad R_4 = 1k\Omega$$

For  $D_1$  :  $i_D = I_S(e^{v_D/V_{TH}} - 1)$  with  $I_S = 1 \times 10^{-9}A$  and  $V_{TH} = 25mV$ .

- Find the Thévenin equivalent circuit for the circuit connected to the diode.
- Assume that for bias point determination the diode can be modeled by an ideal diode and a 0.6 volt battery. What are  $v_D$  and  $i_D$  when  $v_I = 4$  volts?
- Find a linear equivalent model for this diode valid for small signal incremental operation about the bias point determined from part b.
- Use your model of part c) to find  $v_d(t)$  if  $v_I = 4 + 0.004 \cos \omega t$  volts.

**Solution:**

- $R_{TH} = 0.5 \text{ k}\Omega \quad V_{OC} = \frac{1}{4}v_I$
- $v_D = 0.6V, i_D = 0.8mA$
- $r_d = \frac{V_{TH}}{I_S} \exp\left(\frac{-V_D}{V_{TH}}\right) = 9.44 \times 10^{-4}\Omega$
- $v_d = 1.88 \times 10^{-9} \cos \omega t$

**Problem 4.12** Consider the circuit in Figure 4.30. The voltage source and the current source are the sum of a dc-level and an ac-perturbation:

$$v = V + \Delta v$$

$$i = I + \Delta i$$

such that  $V = 30V$  (dc),  $I = 10A$  (dc),  $\Delta v = 100mV$  (ac),  $\Delta i = 50mA$  (ac).

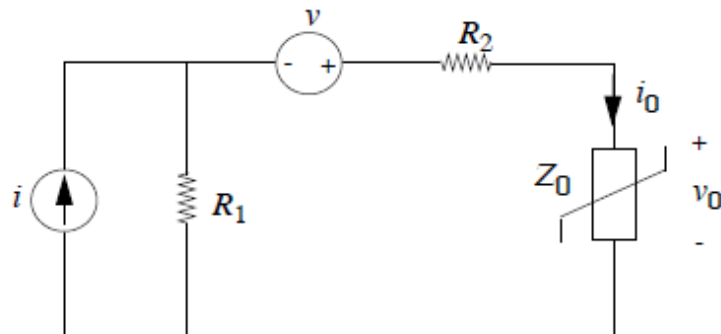


Figure 4.30:

The resistors have the following values:  $R_1 = R_2 = 1/2$  ohm. The nonlinear element  $Z_0$  has the characteristic:

$$i_0 = v_0 + v_0^2$$

Find, by incremental analysis, the DC and AC components of the output voltage  $v_0$ .

**Remark:** You can assume in your analysis that the nonlinear element is behaving as a passive element, i.e., is consuming power.

**Solution:** DC component:  $5V$

AC component from current source:  $0.002V$

AC component from voltage source:  $0.008V$

**ANS::** DC:  $5V$ , AC from current:  $0.002V$ , AC from voltage:  $0.008V$