

Digital Logic Design

4190.201

2014 Spring Semester

11. Sequential Logic Examples

Naehyuck Chang
Dept. of CSE
Seoul National University
naehyuck@snu.ac.kr



Sequential logic examples

- Basic design approach: a 4-step design process
- Hardware description languages and finite state machines
- Implementation examples and case studies
 - Finite-string pattern recognizer
 - Complex counter
 - Traffic light controller
 - Door combination lock

General FSM design procedure

- Determine inputs and outputs
- Determine possible states of machine
 - State minimization
- Encode states and outputs into a binary code
 - State assignment or state encoding
 - Output encoding
 - Possibly input encoding (if under our control)
- Realize logic to implement functions for states and outputs
 - Combinational logic implementation and optimization
 - Choices in steps 2 and 3 can have large effect on resulting logic

Finite string pattern recognizer (step 1)


- Finite string pattern recognizer
 - One input (X) and one output (Z)
 - Output is asserted whenever the input sequence ...010... has been observed, as long as the sequence ...100... has never been seen
- Step 1: understanding the problem statement
 - Sample input/output behavior:

X: 0 0 1 0 1 0 1 0 0 1 0 ...
Z: 0 0 0 1 0 1 0 1 0 0 0 ...

X: 1 1 0 1 1 0 1 0 0 1 0 ...
Z: 0 0 0 0 0 0 0 1 0 0 0 ...


Finite string pattern recognizer (step 2)

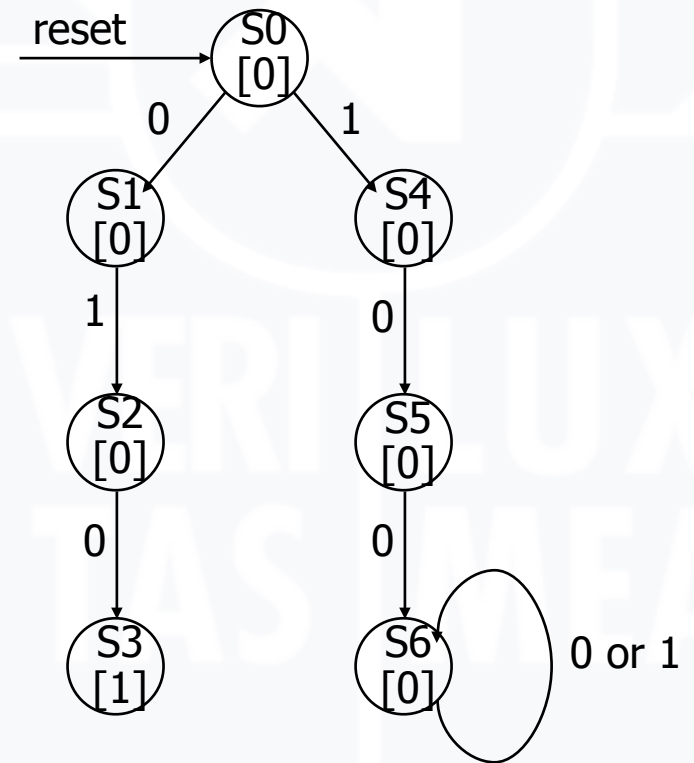- Step 2: draw state diagram
 - For the strings that must be recognized, i.e., 010 and 100
 - A Moore implementation




Finite string pattern recognizer (step 2, cont'd)

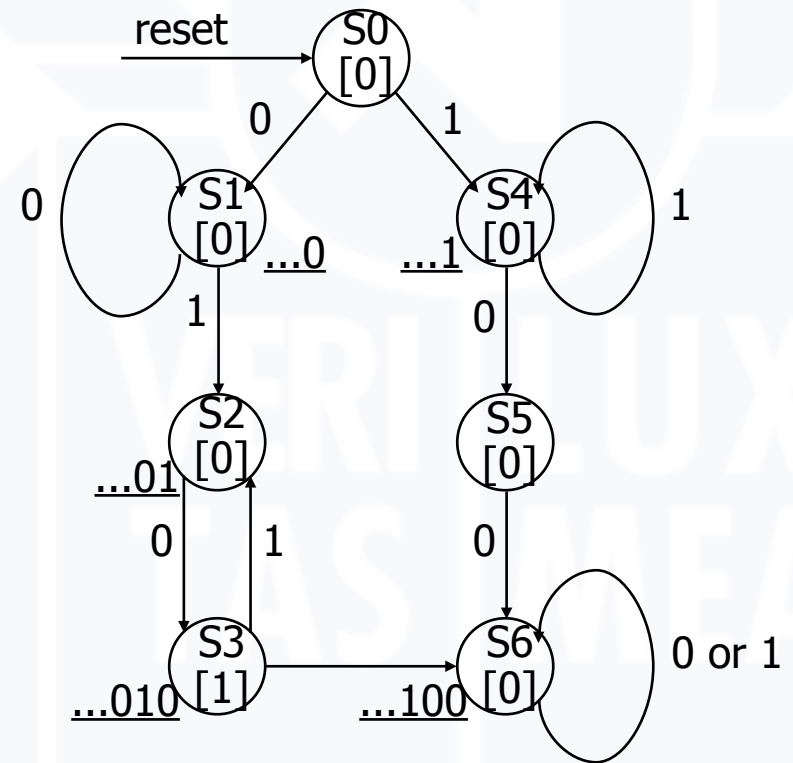- Exit conditions from state S3: have recognized ...010
 - If next input is 0 then have ...0100 = ...100 (state S6)
 - If next input is 1 then have ...0101 = ...01 (state S2)
- Exit conditions from S1: recognizes strings of form ...0 (no 1 seen)
 - Loop back to S1 if input is 0
- Exit conditions from S4: recognizes strings of form ...1 (no 0 seen)
 - Loop back to S4 if input is 1



Finite string pattern recognizer (step 2, cont'd)

- S2 and S5 still have incomplete transitions
 - S2 = ...01; If next input is 1, then string could be prefix of (01)1(00) S4 handles just this case
 - S5 = ...10; If next input is 1, then string could be prefix of (10)1(0) S2 handles just this case
- Reuse states as much as possible
 - look for same meaning
 - state minimization leads to smaller number of bits to represent states
- Once all states have a complete set of transitions we have a final state diagram

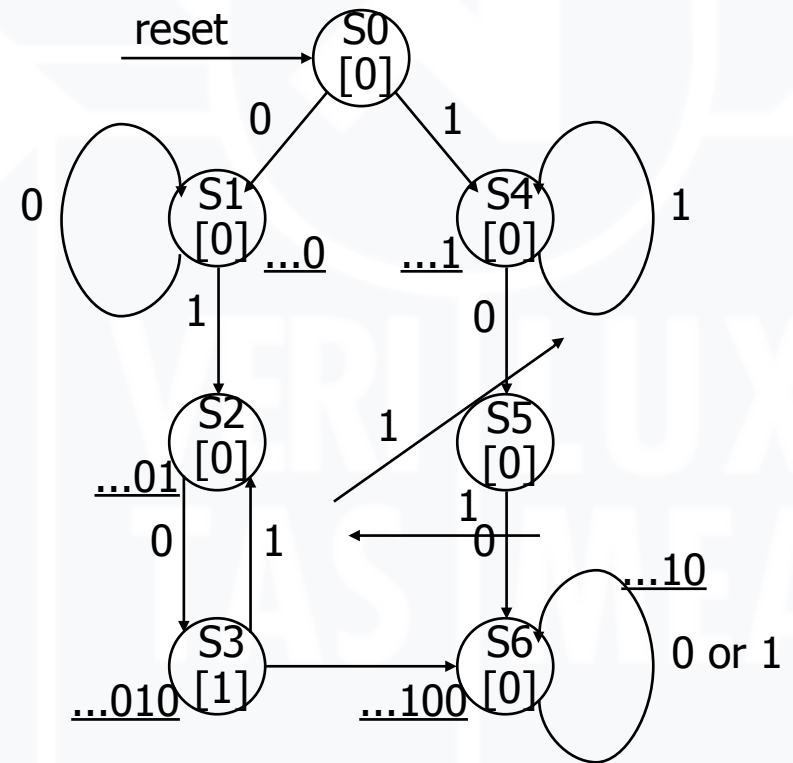

Finite string pattern recognizer (step 3)

- Verilog description including state assignment (or state encoding)

```
module string (clk, X, rst, Q0, Q1, Q2, Z);
input clk, X, rst;
output Q0, Q1, Q2, Z;

parameter S0 = [0,0,0]; //reset state
parameter S1 = [0,0,1]; //strings ending in ...0
parameter S2 = [0,1,0]; //strings ending in ...01
parameter S3 = [0,1,1]; //strings ending in ...010
parameter S4 = [1,0,0]; //strings ending in ...1
parameter S5 = [1,0,1]; //strings ending in ...10
parameter S6 = [1,1,0]; //strings ending in ...100

reg state[0:2];

assign Q0 = state[0];
assign Q1 = state[1];
assign Q2 = state[2];
assign Z = (state == S3);
```

```
always @(posedge clk) begin
    if (rst) state = S0;
    else
        case (state)
            S0: if (X) state = S4 else state = S1;
            S1: if (X) state = S2 else state = S1;
            S2: if (X) state = S4 else state = S3;
            S3: if (X) state = S2 else state = S6;
            S4: if (X) state = S4 else state = S5;
            S5: if (X) state = S2 else state = S6;
            S6: state = S6;
            default: begin
                $display ("invalid state reached");
                state = 3'bxxx;
            end
        endcase
    end
end

endmodule
```


Finite string pattern recognizer

- Review of process
 - Understanding problem
 - Write down sample inputs and outputs to understand specification
 - Derive a state diagram
 - Write down sequences of states and transitions for sequences to be recognized
 - Minimize number of states
 - Add missing transitions; reuse states as much as possible
 - State assignment or encoding
 - Encode states with unique patterns
 - Simulate realization
 - Verify I/O behavior of your state diagram to ensure it matches specification

Complex counter

- A synchronous 3-bit counter has a mode control M
 - When $M = 0$, the counter counts up in the binary sequence
 - When $M = 1$, the counter advances through the Gray code sequence

binary: 000, 001, 010, 011, 100, 101, 110, 111


Gray: 000, 001, 011, 010, 110, 111, 101, 100

- Valid I/O behavior (partial)

Mode Input M	Current State	Next State
0	000	001
0	001	010
1	010	110
1	110	111
1	111	101
0	101	110
0	110	111

Complex counter (state diagram)

 - Deriving state diagram
 - One state for each output combination
 - Add appropriate arcs for the mode control



Complex counter (state encoding)

Verilog description including state encoding

```
module string (clk, M, rst, Z0, Z1, Z2);  
  input clk, X, rst;  
  output Z0, Z1, Z2;
```

```
  parameter S0 = [0,0,0];  
  parameter S1 = [0,0,1];  
  parameter S2 = [0,1,0];  
  parameter S3 = [0,1,1];  
  parameter S4 = [1,0,0];  
  parameter S5 = [1,0,1];  
  parameter S6 = [1,1,0];  
  parameter S7 = [1,1,1];
```


```
  reg state[0:2];
```

```
  assign Z0 = state[0];  
  assign Z1 = state[1];  
  assign Z2 = state[2];
```

```
  always @(posedge clk) begin  
    if rst state = S0;  
    else  
      case (state)  
        S0: state = S1;  
        S1: if (M) state = S3 else state = S2;  
        S2: if (M) state = S6 else state = S3;  
        S3: if (M) state = S2 else state = S4;  
        S4: if (M) state = S0 else state = S5;  
        S5: if (M) state = S4 else state = S6;  
        S6: if (M) state = S7 else state = S7;  
        S7: if (M) state = S5 else state = S0;  
      endcase  
    end  
  end  
endmodule
```

Traffic light controller as two communicating FSMs


- Without separate timer
 - S0 would require 7 states
 - S1 would require 3 states
 - S2 would require 7 states
 - S3 would require 3 states
 - S1 and S3 have simple transformation
 - S0 and S2 would require many more arcs
 - C could change in any of seven states
- By factoring out timer
 - Greatly reduce number of states
 - 4 instead of 20
 - Counter only requires seven or eight states
 - 12 total instead of 20

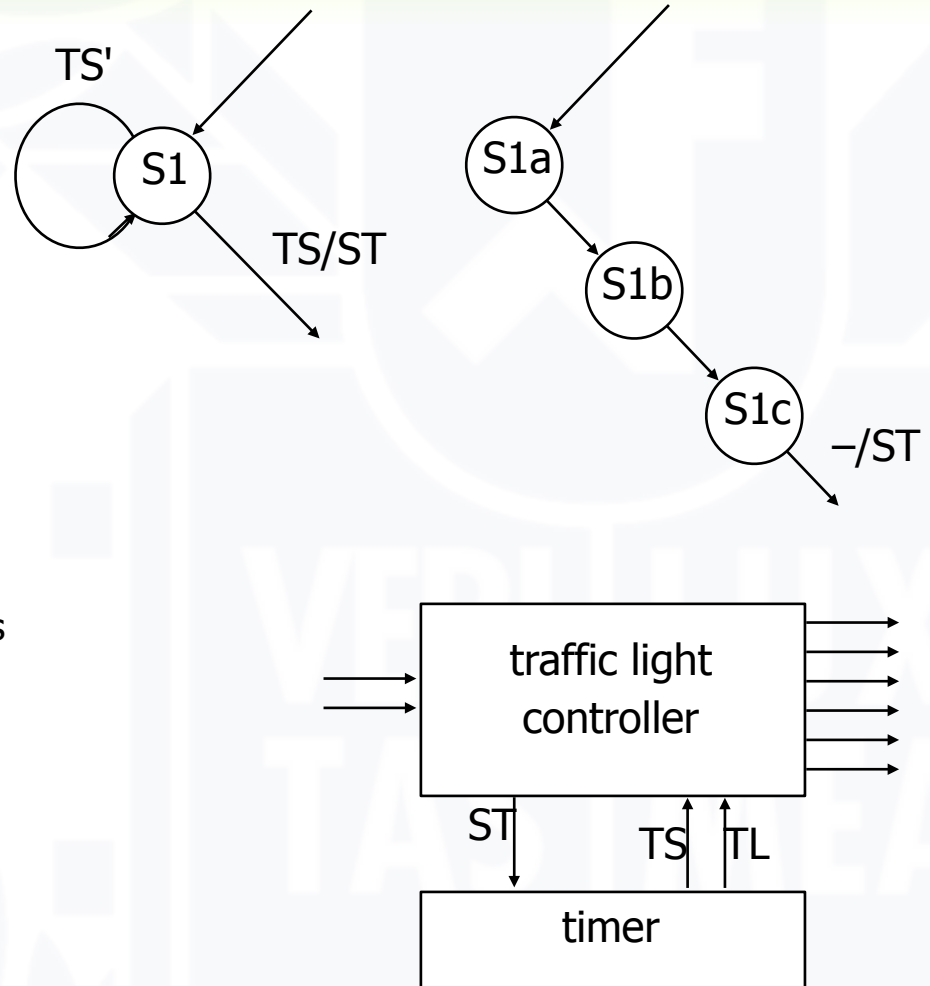

Traffic light controller FSM

Specification of inputs, outputs, and state elements

```
module FSM(HR, HY, HG, FR, FY, FG, ST, TS, TL, C, reset, Clk);  
    output    HR;  
    output    HY;  
    output    HG;  
    output    FR;  
    output    FY;  
    output    FG;  
    output    ST;  
    input     TS;  
    input     TL;  
    input     C;  
    input     reset;  
    input     Clk;  
  
    reg [6:1] state;  
    reg      ST;  
  
    parameter highwaygreen  = 6'b001100;  
    parameter highwayyellow = 6'b010100;  
    parameter farmroadgreen  = 6'b100001;  
    parameter farmroadyellow = 6'b100010;  
  
    assign HR = state[6];  
    assign HY = state[5];  
    assign HG = state[4];  
    assign FR = state[3];  
    assign FY = state[2];  
    assign FG = state[1];
```



The diagram shows three arrows originating from a common point at the bottom. One arrow points to the `state` register declaration (`reg [6:1] state;`). The other two arrows point to the parameter definitions for `highwaygreen` and `highwayyellow`, which are the first two parameters listed.


Specify state bits and codes
for each state as well as
connections to outputs

Traffic light controller FSM (cont'd)

```
initial begin state = highwaygreen; ST = 0; end

always @(posedge Clk)
begin
    if (reset)
        begin state = highwaygreen; ST = 1; end
    else
        begin
            ST = 0;
            case (state)
                highwaygreen:
                    if (TL & C) begin state = highwayyellow; ST = 1; end
                highwayyellow:
                    if (TS) begin state = farmroadgreen; ST = 1; end
                farmroadgreen:
                    if (TL | !C) begin state = farmroadyellow; ST = 1; end
                farmroadyellow:
                    if (TS) begin state = highwaygreen; ST = 1; end
            endcase
        end
    end
end
endmodule
```

case statement triggered by clock edge

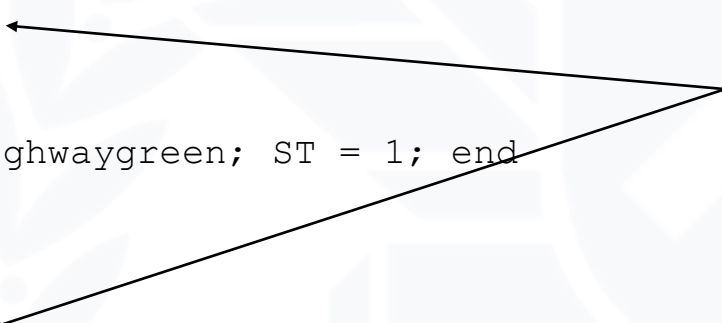

Timer for traffic light controller

● Another FSM

```
module Timer(TS, TL, ST, Clk);
    output TS;
    output TL;
    input    ST;
    input    Clk;
    integer  value;

    assign TS = (value >= 4); // 5 cycles after reset
    assign TL = (value >= 14); // 15 cycles after reset

    always @(posedge ST) value = 0; // async reset


    always @(posedge Clk) value = value + 1;

endmodule
```


Complete traffic light controller





- Tying it all together (FSM + timer)
 - Structural Verilog (same as a schematic drawing)
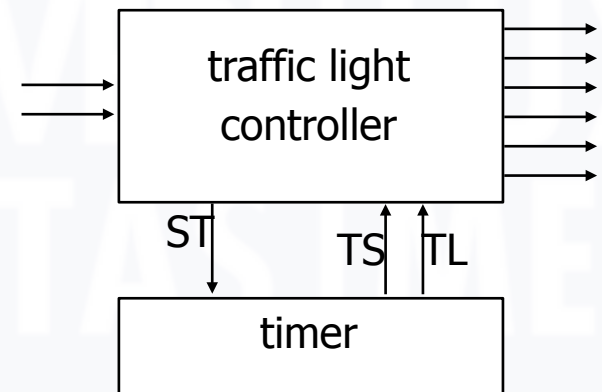
```
module main(HR, HY, HG, FR, FY, FG, reset, C, Clk);  
    output HR, HY, HG, FR, FY, FG;  
    input  reset, C, Clk;  
  
    Timer part1(TS, TL, ST, Clk);  
    FSM   part2(HR, HY, HG, FR, FY, FG, ST, TS, TL, C, reset, Clk);  
endmodule
```



Communicating finite state machines

    
- One machine's output is another machine's input



Machines advance in lock step
initial inputs/outputs: $X = 0$, $Y = 0$

Data-path and control

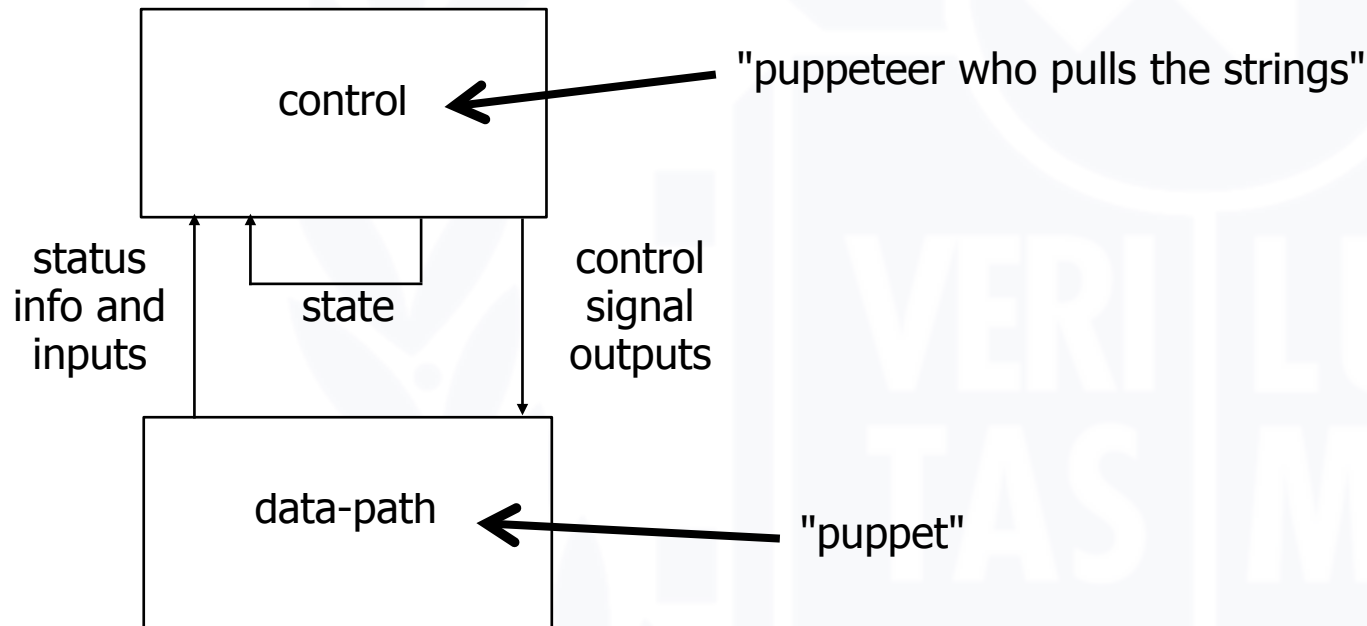- Digital hardware systems = data-path + control
 - Datapath: registers, counters, combinational functional units (e.g., ALU), communication (e.g., busses)
 - Control: FSM generating sequences of control signals that instructs datapath what to do next



Digital combinational lock


- Door combination lock:
 - Punch in 3 values in sequence and the door opens; if there is an error the lock must be reset; once the door opens the lock must be reset
 - Inputs: sequence of input values, reset
 - Outputs: door open/close
 - Memory: must remember combination or always have it available
- Open questions: how do you set the internal combination?
 - Stored in registers (how loaded?)
 - Hardwired via switches set by user

Implementation in software

```
integer combination_lock ( ) {  
    integer v1, v2, v3;  
    integer error = 0;  
    static integer c[3] = 3, 4, 2;  
  
    while (!new_value( ));  
    v1 = read_value( );  
    if (v1 != c[1]) then error = 1;  
  
    while (!new_value( ));  
    v2 = read_value( );  
    if (v2 != c[2]) then error = 1;  
  
    while (!new_value( ));  
    v3 = read_value( );  
    if (v3 != c[3]) then error = 1;  
  
    if (error == 1) then return(0); else return (1);  
}
```


Determining details of the specification

 - How many bits per input value?
- How many values in sequence?
- How do we know a new input value is entered?
- What are the states and state transitions of the system?




Digital combination lock state diagram

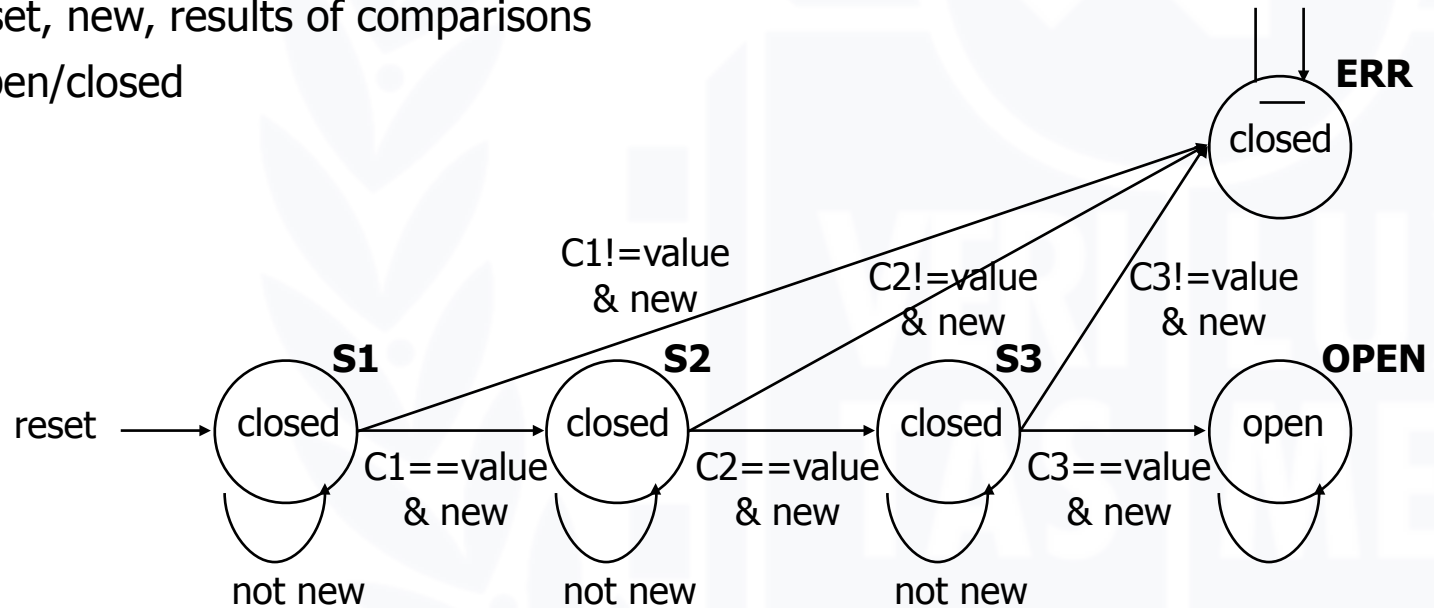- States: 5 states
 - Represent point in execution of machine
 - Each state has outputs
- Transitions: 6 from state to state, 5 self transitions, 1 global
 - Changes of state occur when clock says its ok
 - Based on value of inputs
- Inputs: reset, new, results of comparisons
- Output: open/closed



Data-path and control structure

 - Data-path
 - Storage registers for combination values
 - Multiplexer
 - Comparator
- Control
 - Finite-state machine controller
 - Control for data-path (which value to compare)



State table for combination lock

- Finite-state machine
 - Refine state diagram to take internal structure into account
 - State table ready for encoding


reset	new	equal	state	next state	mux	open/closed
1	—	—	—	S1	C1	closed
0	0	—	S1	S1	C1	closed
0	1	0	S1	ERR	—	closed
0	1	1	S1	S2	C2	closed
...						
0	1	1	S3	OPEN	—	open
...						

Encodings for combination lock

- Encode state table
 - State can be: S1, S2, S3, OPEN, or ERR
 - Needs at least 3 bits to encode: 000, 001, 010, 011, 100
 - And as many as 5: 00001, 00010, 00100, 01000, 10000
 - Choose 4 bits: 0001, 0010, 0100, 1000, 0000
 - Output mux can be: C1, C2, or C3
 - Needs 2 to 3 bits to encode
 - Choose 3 bits: 001, 010, 100
 - Output open/closed can be: open or closed
 - Needs 1 or 2 bits to encode
 - Choose 1 bit: 1, 0



reset	new	equal	state	next state	mux	open/closed
1	—	—	—	0001	001	0
0	0	—	0001	0001	001	0
0	1	0	0001	0000	—	0
0	1	1	0001	0010	010	0
...						
0	1	1	0100	1000	—	1
...						

 Mux is identical to last 3 bits of state
 open/closed is identical to first bit of state
 therefore, we do not even need to implement
 FFs to hold state, just use outputs





Data-path implementation for combination lock

 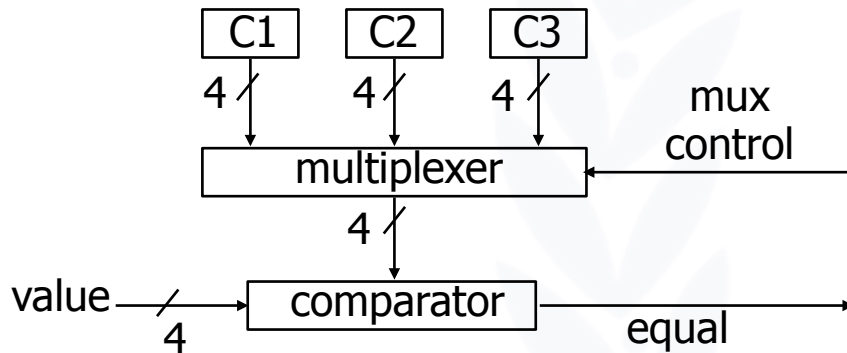- Multiplexer
 - Easy to implement as combinational logic when few inputs
 - Logic can easily get too big for most PLDs




Data-path implementation (cont'd)

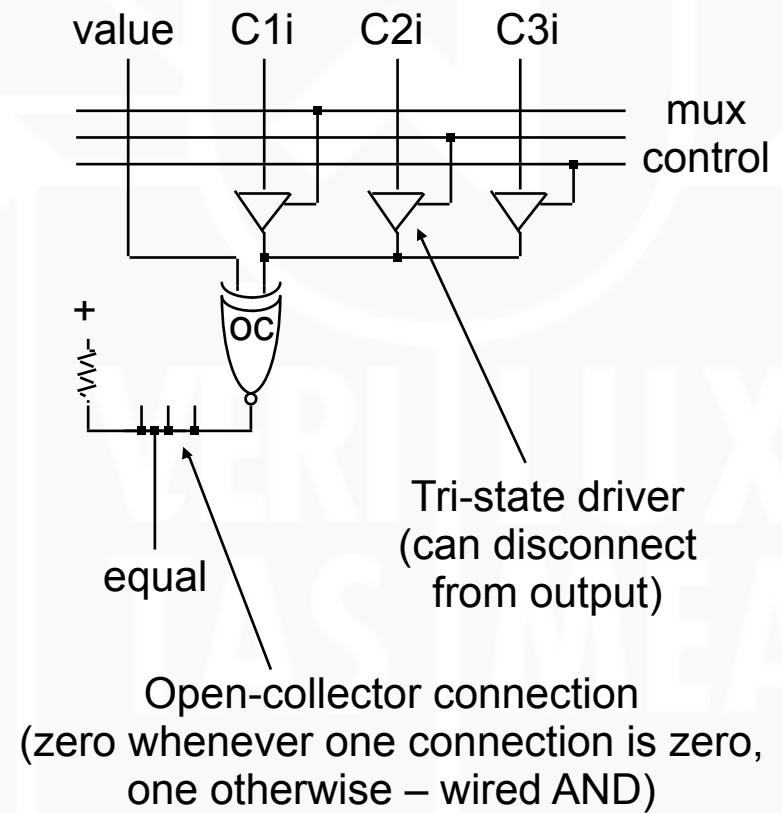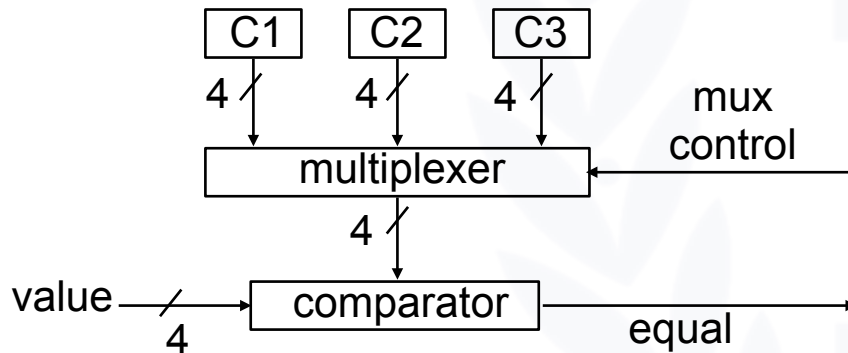- Tri-state logic
 - Utilize a third output state: "no connection" or "float"
 - Connect outputs together as long as only one is "enabled"
 - Open-collector gates can only output 0, not 1
 - Can be used to implement logical AND with only wires




Tri-state gates

- The third value
 - Logic values: "0", "1"
 - Don't care: "X" (must be 0 or 1 in real circuit!)
 - Third value or state: "Z" — high impedance, infinite R, no connection
- Tri-state gates
 - Additional input – output enable (OE)
 - Output values are 0, 1, and Z
 - When OE is high, the gate functions normally
 - When OE is low, the gate is disconnected from wire at output
 - Allows more than one gate to be connected to the same output wire
 - As long as only one has its output enabled at any one time (otherwise, sparks could fly)

 


Non-inverting
tri-state
buffer

In	OE	Out
X	0	Z
0	1	0
1	1	1

 

Tri-state and multiplexing

 - When using tri-state logic
 - Make sure never more than one "driver" for a wire at any one time (Pulling high and low at the same time can severely damage circuits)
 - Make sure to only use value on wire when its being driven (Using a floating value may cause failures)
- Using tri-state gates to implement an economical multiplexer




When Select is high
Input1 is connected to F

When Select is low
Input0 is connected to F

This is essentially a 2:1 mux

Open-collector gates and wired-AND


- Open collector: another way to connect gate outputs to the same wire
 - Gate only has the ability to pull its output low
 - It cannot actively drive the wire high (default – pulled high through resistor)
- Wired-AND can be implemented with open collector logic
 - If A and B are "1", output is actively pulled low
 - If C and D are "1", output is actively pulled low
 - If one gate output is low and the other high, then low wins
 - If both gate outputs are "1", the wire value "floats", pulled high by resistor
 - Low to high transition usually slower than it would have been with a gate pulling high
 - Hence, the two NAND functions are ANDed together

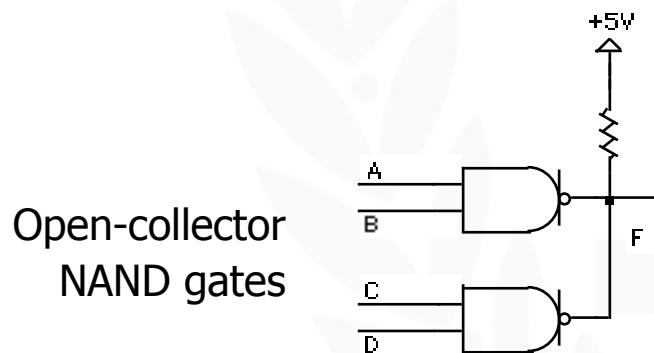

With outputs wired together
using "wired-AND"
to form $(AB)'(CD)'$

Digital combination lock (new data-path)

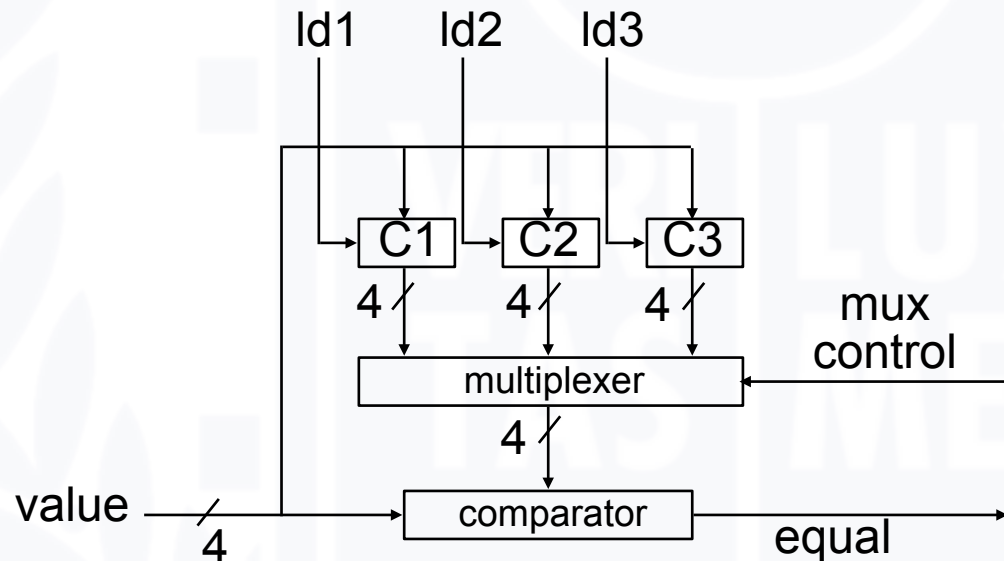- Decrease number of inputs
- Remove 3 code digits as inputs
 - Use code registers
 - Make them loadable from value
- Need 3 load signal inputs (net gain in input $(4*3)-3=9$)
 - Could be done with 2 signals and decoder (ld1, ld2, ld3, load none)



Section summary

- FSM design
 - Understanding the problem
 - Generating state diagram
 - Communicating state machines
- Four case studies
 - Understand I/O behavior
 - Draw diagrams
 - Enumerate states for the "goal"
 - Expand with error conditions
 - Reuse states whenever possible