

**Exercise 6.4** Consider, again, the inverter circuit shown in Figure 6.4. The MOSFET has a threshold voltage  $V_T = 2V$ . Assume that  $V_S = 5V$  and  $R_L = 10k$ . For this exercise, model the MOSFET using its switch-resistor model. Assume that the on-state resistance of the MOSFET is  $R_{ON} = 8k$ .

- Does the inverter satisfy the static discipline which has voltage thresholds given by  $V_{OL} = V_{IL} = 1V$  and  $V_{OH} = V_{IH} = 4V$ ? Explain.
- Does the inverter satisfy the static discipline for the voltage thresholds  $V_{OL} = V_{IL} = 2.5V$  and  $V_{OH} = V_{IH} = 3V$ ? Explain.
- Draw the input versus output voltage transfer curve for the inverter.
- Is there any value of  $V_{IL}$  for which the inverter will satisfy the static discipline? Explain.
- Now assume that  $R_{ON} = 1k$  and repeat parts (a), (b), and (c).

Solution:

- First find the relevant threshold output and input values for the inverter:

The output high voltage is 5.

The output low voltage is

$$V_S \cdot \frac{R_{ON}}{R_{ON} + R_L} = 5 \cdot \frac{8}{18} = 2.2$$

The lowest input voltage recognized as a logical 1 is

$$V_T = 2V$$

The highest input voltage recognized as a logical 0 is less than 2V.

With  $V_{OL} = V_{IL} = 1V$  and  $V_{OH} = V_{IH} = 4V$ :

No, the static discipline is not satisfied. A failure case is for an input voltage which is greater than  $V_{OH} = 4V$  (i.e., a valid 1). Since this high input voltage is greater than the threshold, the inverter output voltage is 2.2V, which is greater than  $V_{OL} = 1V$ . But this is not a valid 0. Valid 0 outputs would be outputs that are less than 1V.

 


Figure 6.7:

- b) With  $V_{OL} = V_{IL} = 2.5V$  and  $V_{OH} = V_{IH} = 3V$ :

No. Now we have a failure case when the input is, say, 2.3V (i.e., a valid 0). But since  $2.3 > V_T$ , the output will be 2.2V. For a valid inverter the output should have been a valid 1. Thus, this violates the inverter's static discipline.

- c) See Figure 6.7 for transfer curve.

- d) No. The lowest value the inverter output ever reaches is 2.2V, which is still higher than 2V. Thus the inverter output can never turn the MOSFET in a receiving inverter off. This implies that we will never be able to satisfy the discipline.

- e) a)  $R_{ON} = 1k$

$$V_{OL} = V_S \cdot \left( \frac{R_{ON}}{R_{ON} + R_L} \right) = 5 \cdot \frac{1}{11} = 0.45$$

With  $V_{OL} = V_{IL} = 1V$  and  $V_{OH} = V_{IH} = 4V$ :

Yes, we satisfy the static discipline. For valid 0 input ( $< V_{IL}$ ), then output is always a valid 1 ( $> V_{OH}$ ). For valid 1 input ( $> V_{IH}$ ), the output is always a valid 0 ( $< V_{OL}$ ).

- b) With  $V_{OL} = V_{IL} = 2.5V$  and  $V_{OH} = V_{IH} = 3V$ :

No. Counter case is if the input is 2.3V which is  $< V_{IL}$  (valid 0), then it will produce an output 0 as well (i.e.,  $< V_{OL}$ ).

- c) See Figure 6.8 for transfer curve.

ANS:: (a) no (b) no (d) no (e-a) yes (e-b) no

**Exercise 6.5** Compute the worst-case power consumed by the inverter shown in Figure 6.4. The MOSFET has a threshold voltage  $V_T = 2V$ . Assume that  $V_S = 5V$  and  $R_L = 10k$ . Model the MOSFET using its switch-resistor model, and assume that the on-state resistance of the MOSFET is  $R_{ON} = 1k$ .

Solution:

Power dissipated:

$$\begin{aligned} Power &= V_S I = \frac{V_S^2}{R_L + R_{ON}} \\ &= 5^2 \cdot \left( \frac{1}{(10 + 1)10^3} \right) \\ &= 2.27mW \end{aligned}$$

ANS:: 2.27 mW

### Problem 6.1

- Write a truth table and a boolean equation relating the output  $Z$  to  $A$ ,  $\overline{A}$ ,  $B$ , and  $C$ , when these are input to the circuit shown in Figure 6.10.
- Suppose the circuit in Figure 6.10 suffers a manufacturing error which results in a short between the pair of wires depicted in Figure 6.11. Write a truth table and a boolean equation relating the output  $Z$  to  $A$ ,  $\overline{A}$ ,  $B$ , and  $C$ , for the resulting circuit.

Solution:

$A$	$\overline{A}$	$B$	$C$	$Z$
0	1	0	0	1
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0

$A$	$\overline{A}$	$B$	$C$	$Z$
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0

ANS.: (a)  $Z = \overline{A} + B$  (b)  $Z = \overline{A} + B + C$

**Problem 6.3** Consider a family of logic gates which operates under the static discipline with the following voltage thresholds:  $V_{OL} = 1$  V,  $V_{IL} = 1.3$  V,  $V_{OH} = 4$  V, and  $V_{IH} = 3$  V. Consider the N-input NAND gate design shown in Figure 6.13. In the design  $R = 100k$  and  $R_{ON}$  for the MOSFETs is given to be  $1k$ .  $V_T$  for the MOSFETs is 1.5V. What is the maximum value of  $N$  for which the NAND gate will satisfy the static discipline? What is the maximum power dissipated by the NAND gate for this value of  $N$ ?

 


Figure 6.13:

Solution:

Voltage value at  $Z$  will equal  $V_S$  during a logical 1. During a logical 0,  $V_S$  is divided between  $N R_{ON}$  and  $R$ . Therefore, we require

$$V_{Z=0} \leq V_{OL}$$

$$V_{Z=0} = V_S * \frac{N * R_{ON}}{N * R_{ON} + 100k} \leq 1V$$

$$(V_S - 1)NR_{ON} \leq 100k$$

$$N \leq \frac{100k}{(V_S - 1)R_{ON}}$$

**Maximum power dissipation when all switches on.**

$$P_{MAX} = \frac{V_S^2}{100k + NR_{ON}}$$

$$\text{ANS:: } N = \frac{100k}{(V_S - 1)R_{ON}}, P_{MAX} = \frac{V_S^2}{100k + NR_{ON}}$$