

Exercise 3.3 Find the Thévenin Equivalent for each network in Figure 3.4.

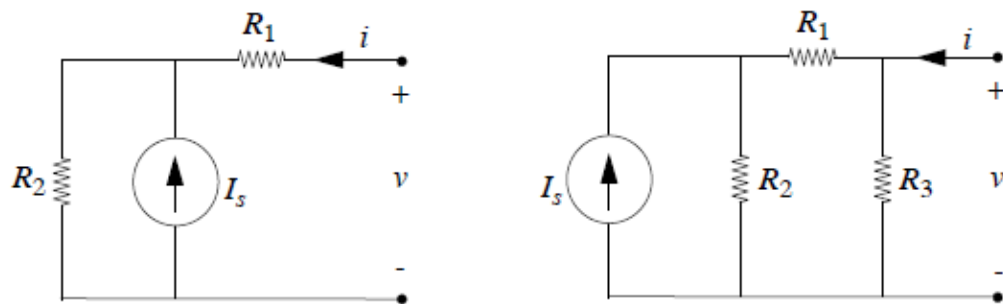


Figure 3.4:

Solution:

Left network:

$R_T = R_1 + R_2$ when I_S is made an open circuit.

$V_{OC} = I_S R_2$ since no current flows through R_1 in the open circuit case.

$R_T = R_3 || (R_1 + R_2)$ when I_S current source is made an open circuit.

Since $V_{OC} = R_3 \cdot$ (current through R_3) by Ohm's Law,

$$V_{OC} = \underbrace{\frac{I_S \cdot R_2}{R_1 + R_2 + R_3}}_{\substack{\text{current di-} \\ \text{vider relation} \\ \text{for fraction of} \\ I_S \text{ that will} \\ \text{flow through} \\ R_1 \text{ and } R_3}} \cdot R_3$$

ANS:: Left: $V_{OC} = I_S R_2, R_T = R_1 + R_2$, **Right:** $V_{OC} = \frac{I_S R_2 R_3}{R_1 + R_2 + R_3}, R_T = R_3 || (R_1 + R_2)$

Exercise 3.10 Find the Norton equivalent at the terminals marked xx in the circuit in Figure 3.12.

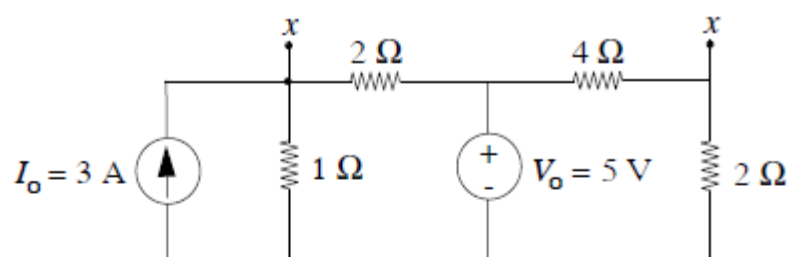


Figure 3.12:

Solution:

$$R_T = 2 \parallel 1 + 4 \parallel 2 = 2\Omega \quad \text{when both sources are "shut off"}$$

$$I_{SC} = \underbrace{1}_{\substack{\text{when} \\ \text{voltage} \\ \text{source} \\ \text{shut off}}} + \underbrace{0}_{\substack{\text{when} \\ \text{current} \\ \text{source} \\ \text{shut off}}} = 1 \text{ A, by superposition}$$

$$\text{ANS: } R_T = 2\Omega \text{ and } I_{SC} = 1 \text{ A}$$

Exercise 3.16 For the circuit shown in Figure 3.20, use superposition to find v in terms of the R 's and source amplitudes.

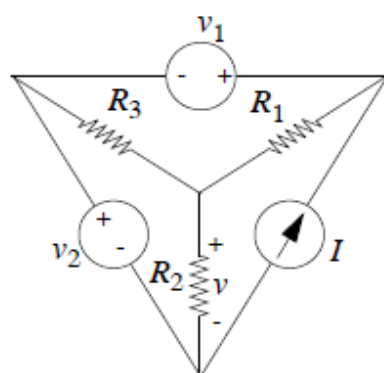


Figure 3.20:

Solution:

Redraw:

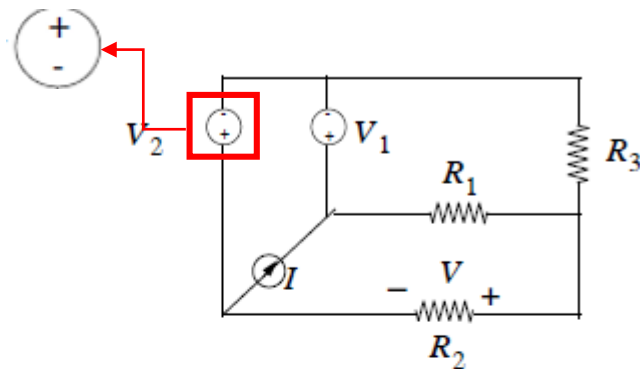


Figure 3.21:

Superposition:

1.

V_2, V_1 off; I on:

$V = 0$ since no current through R_2

2.

V_2 on; V_1 and I off:

$$V = \underbrace{\frac{R_2}{R_2 + R_1 \parallel R_3}}_{\text{voltage divider}} \cdot V_2$$

V_1 on; V_2 and I off:

$$V = \frac{R_2 \parallel R_3}{R_1 + R_2 \parallel R_3} \cdot V_1$$

Superposition:

$$V = V_1 \cdot \frac{R_2 \parallel R_3}{R_1 + R_2 \parallel R_3} \cdot \underbrace{\frac{R_2}{R_2 + R_1 \parallel R_3}}_{\text{voltage divider}} \cdot V_2$$

$$\text{ANS: } V = V_1 \cdot \frac{R_2 \parallel R_3}{R_1 + R_2 \parallel R_3} \cdot \underbrace{\frac{R_2}{R_2 + R_1 \parallel R_3}}_{\text{voltage divider}} \cdot V_2$$

Exercise 3.25 Find the node potential E in Figure 3.39.

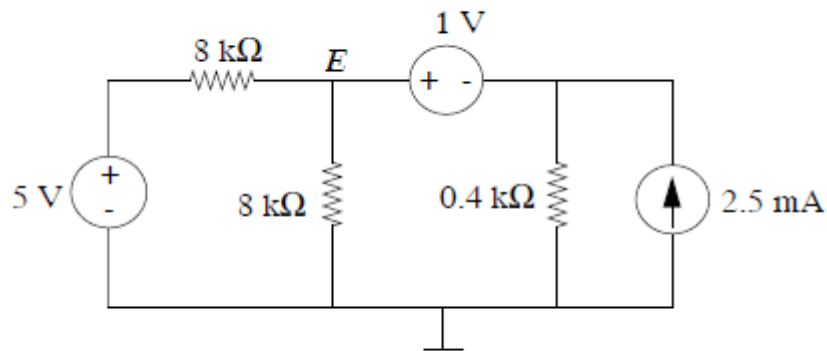


Figure 3.39:

Solution:

By superposition...

1) 5v on / 1v, 2.5mA off

$$E = 5 \times \frac{(8||0.4)}{8 + (8||0.4)} = \frac{5}{22}$$

2) 1v on / 5v, 2.5mA off

$$E = 1 \times \frac{(8||8)}{(8||8) + 0.4} = \frac{10}{11}$$

3) 2.5mA on / 1v, 5v off

$$E = 2.5 \times (8||8||0.4) = \frac{10}{11}$$

$$\therefore E = \frac{5}{22} + \frac{10}{11} + \frac{10}{11} = \frac{45}{22}$$

Problem 3.3 Find V_0 in Figure 3.49. Solve by (1) Node Method, (2) Superposition. All resistances are in Ohms.

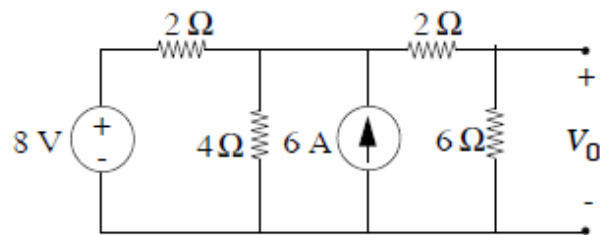


Figure 3.49:

Solution:

(1) Node Method

Label the nodes e_1 and e_2 as shown in Figure 3.50.

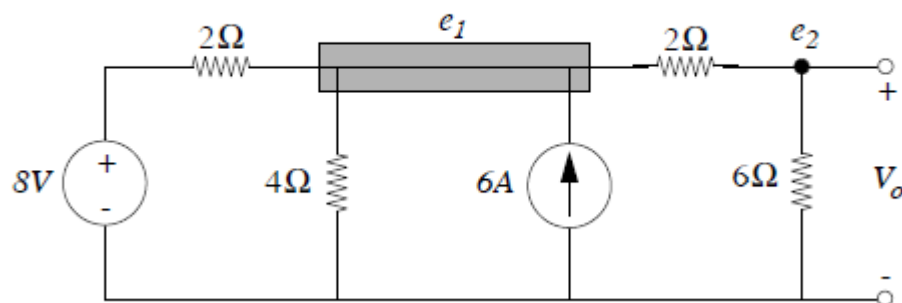


Figure 3.50:

By the node method, we obtain the following two equations:

$$\frac{8V - e_1}{2 \text{ Ohms}} - \frac{e_1}{4 \text{ Ohms}} + 6 \text{ A} + \frac{e_2 - e_1}{2 \text{ Ohms}} = 0$$

$$\frac{e_1 - e_2}{2 \text{ Ohms}} - \frac{e_2}{6 \text{ Ohms}} = 0$$

Thus, $V_0 = e_2 = 8.57 \text{ V}$

(2) Superposition

Find the voltage due to each source independently, as shown in Figure 3.51 and Figure 3.52.

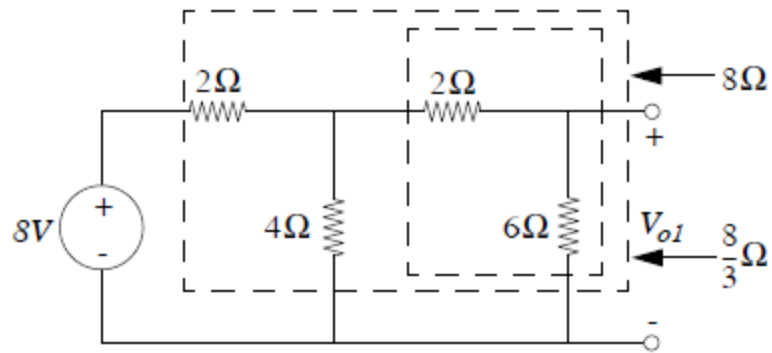


Figure 3.51:

$$V_{01} = (8 \text{ V}) \left(\frac{\frac{8}{3} \text{ Ohms}}{2 + \frac{8}{3} \text{ Ohms}} \frac{6 \text{ Ohms}}{8 \text{ Ohms}} \right) = 3.43 \text{ V}$$

$$V_{02} = (6 \text{ A}) \left(\frac{\frac{4}{3} \text{ Ohms}}{8 + \frac{4}{3} \text{ Ohms}} (6 \text{ Ohms}) \right) = 5.14 \text{ V}$$

$$V_0 = V_{01} + V_{02} = 8.57 \text{ V}$$

ANS:: 8.57 V

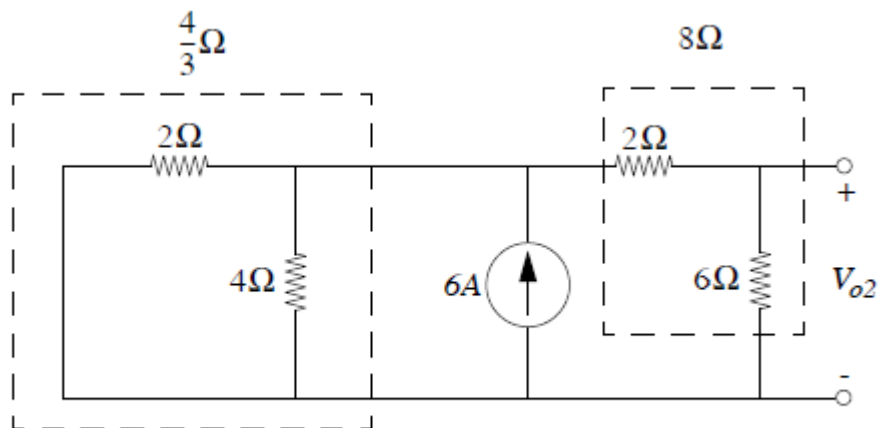


Figure 3.52:

Problem 3.8

- a) Determine the equation relating i to v in Figure 3.63.

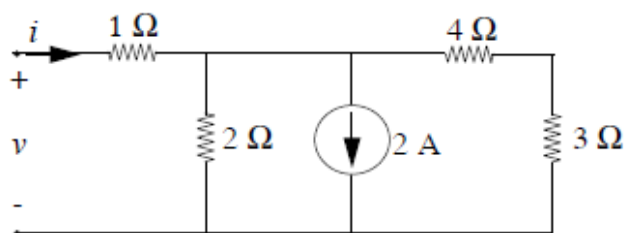


Figure 3.63:

- b) Plot the i - v characteristic of the network.
 c) Draw the Thévenin equivalent circuit.
 d) Draw the Norton equivalent circuit.

Solution:

- a) See Figure 3.64.

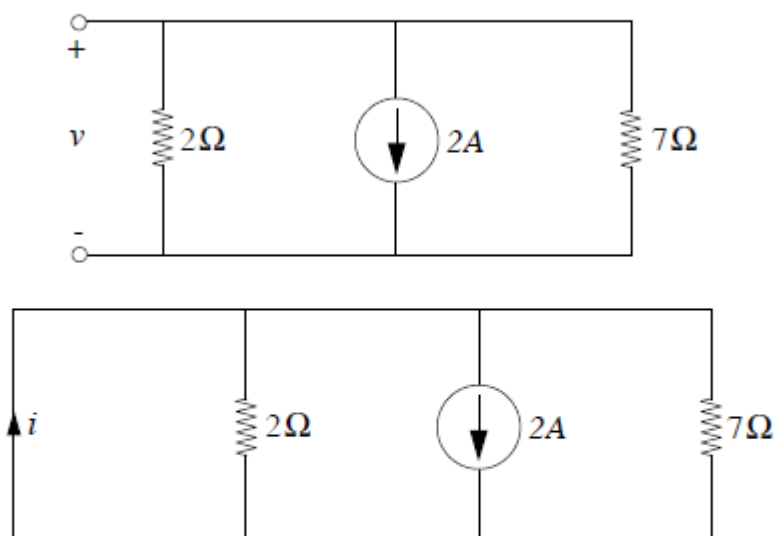


Figure 3.64:

In (i), $i = 0$, so $v = -(2 \text{ A}) \frac{(2 \text{ Ohms})(7 \text{ Ohms})}{2+7 \text{ Ohms}} = -3.11 \text{ V}$.

In (ii), $v = 0$, so $i = (2 \text{ A}) \frac{\frac{14}{9} \text{ Ohms}}{1+\frac{14}{9} \text{ Ohms}} = 1.22 \text{ A}$.

Hence, by linearity, $v = (2.55 \text{ Ohms})i - 3.11 \text{ V}$

b) See Figure 3.65.

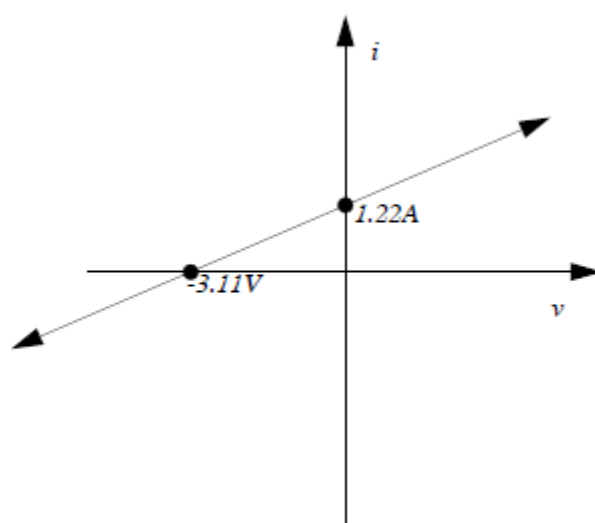


Figure 3.65:

c) See Figure 3.66.

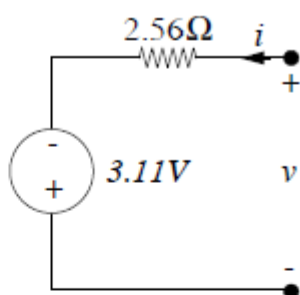


Figure 3.66:

d) See Figure 3.67.

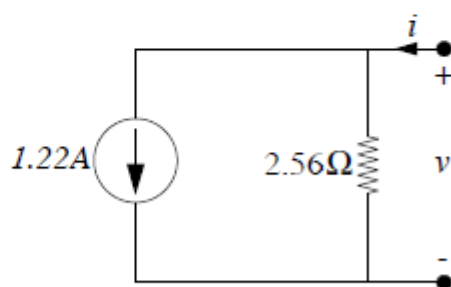


Figure 3.67:

ANS:: (a) $v = (2.55\text{Ohms})i - 3.11V$

Problem 3.13

- a) Find the Thévenin equivalent for the network in Figure 3.80 at the terminals CB . The current source is a *controlled source*. The current flowing through the current source is βI_1 , where β is some constant. (We will discuss controlled sources in more detail in the later chapters.)

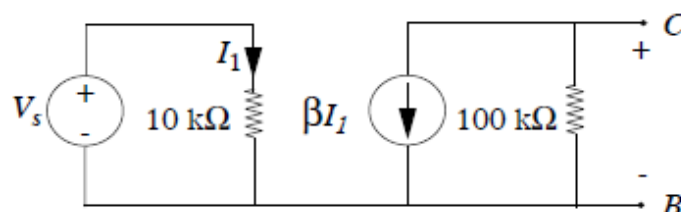


Figure 3.80:

- b) Now suppose you connect a load resistor across the output of your equivalent circuit as shown in Figure 3.81. Find the value of R_L which will provide the maximum power transfer to the load.

Solution:

a) $R_{TH} = 100k\Omega$

$$v_T = v_{OC} = (100\text{ k}\Omega)(-\beta \frac{V_S}{10\text{ k}\Omega}) = -10\beta V_S$$

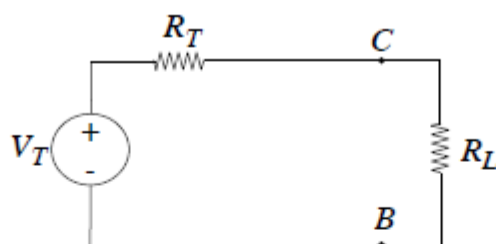


Figure 3.81:

b) $P = I^2 R = R_L (\frac{V_T}{R_T + R_L})^2 = V_T^2 R_L (R_T + R_L)^{-2}$

To maximize P , we write P as a function of R_L and set its derivative with respect to R_L equal to zero. So,

$$P'(R_L) = V_T^2 [(R_T + R_L)^{-2} - 2R_L(R_T + R_L)^{-3}] = 0$$

$$\Rightarrow R_L = R_T$$

ANS:: (a) $R_{TH} = 100k\Omega$, $v_T = -10\beta V_S$ (b) $R_L = R_T$