

Exercise 2.3 Find the equivalent resistance between the indicated terminals (all resistances in ohms) in Figure 2.3.

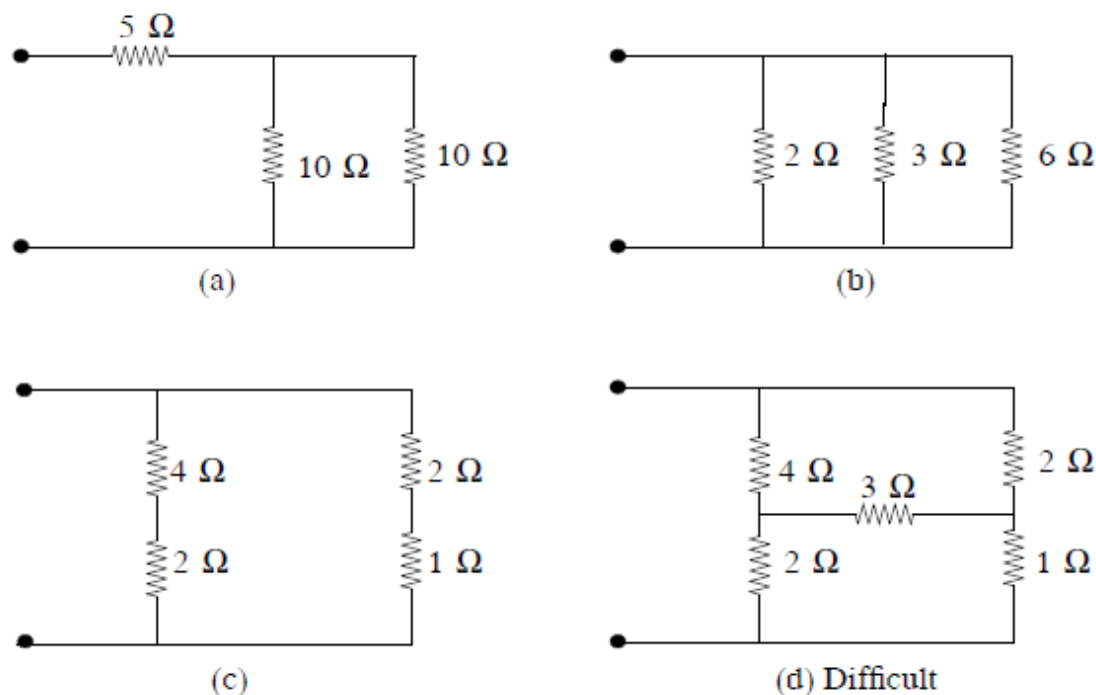


Figure 2.3:

Solution:

- a) $R_{EQ} = 5 + 10 || 10 = 10\Omega$
- b) $R_{EQ} = [2 || 3] || 6 = 1\Omega$
- c) $R_{EQ} = (4 + 2) || (2 + 1) = 2\Omega$
- d) Apply test voltage: $R_{EQ} = \frac{v_{test}}{i_{test}}$

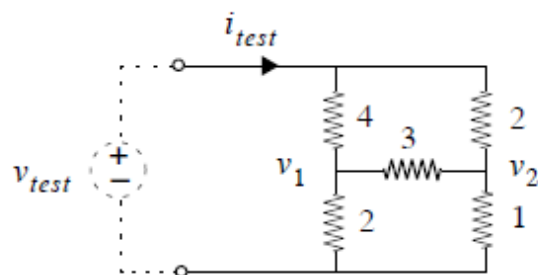


Figure 2.4:

$$\frac{(v_{test} - v_1)}{4} + \frac{(0 - v_1)}{2} + \frac{(v_2 - v_1)}{3} = 0$$

$$\frac{(v_{test} - v_2)}{2} + \frac{(v_1 - v_2)}{3} + \frac{(0 - v_2)}{1} = 0$$

$$v_1 = \frac{v_{test}}{3}, \quad v_2 = \frac{v_{test}}{3}$$

Substitute these expressions into the equation below:

$$i_{test} + \frac{(v_1 - v_{test})}{4} + \frac{(v_2 - v_{test})}{2} = 0$$

$$\frac{v_{test}}{i_{test}} = R_{EQ} = 2\Omega$$

ANS:: (a) 10Ω (b) 1Ω (c) 2Ω (d) 2Ω

Exercise 2.8 Sketch the i-v characteristics for the networks in Figure 2.12. Label intercepts and slopes.

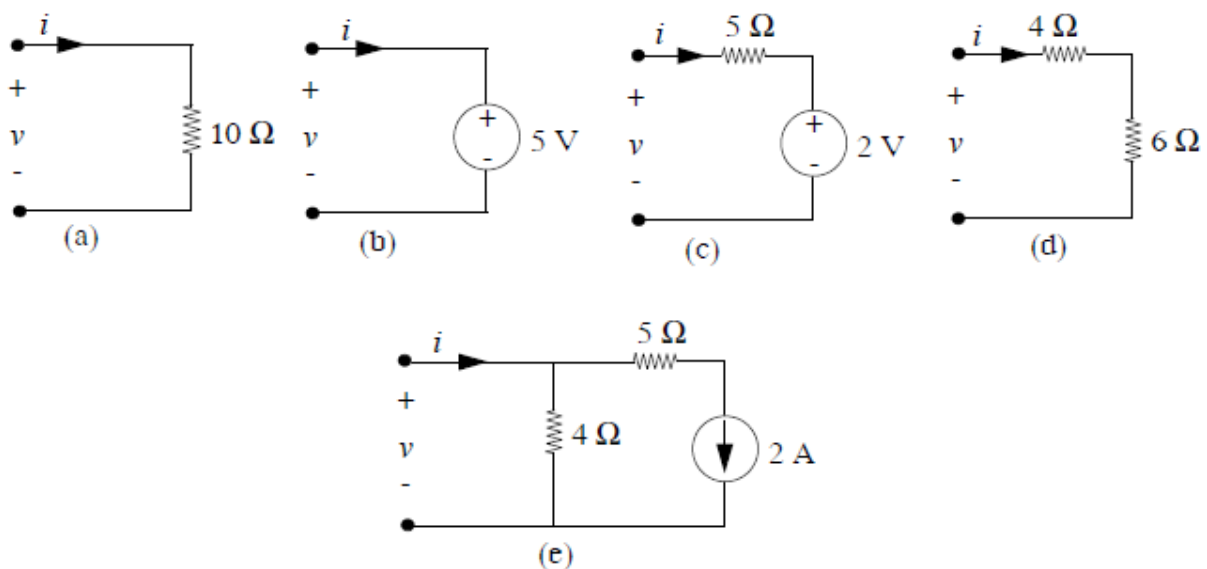


Figure 2.12:

Solution:

c) See Figure 2.15

$$v = 5i + 2$$

$$i = \frac{1}{5}v - \frac{2}{5}$$


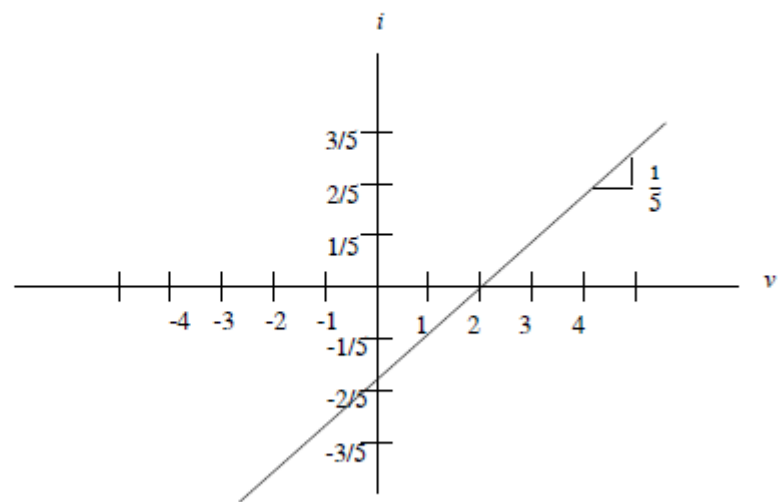
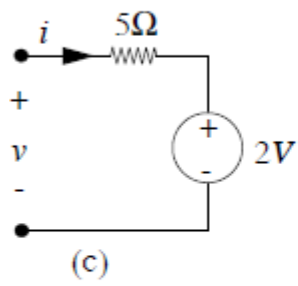


Figure 2.15:

e)

$$v = 4i - 8$$

$$i = v/4 + 2$$

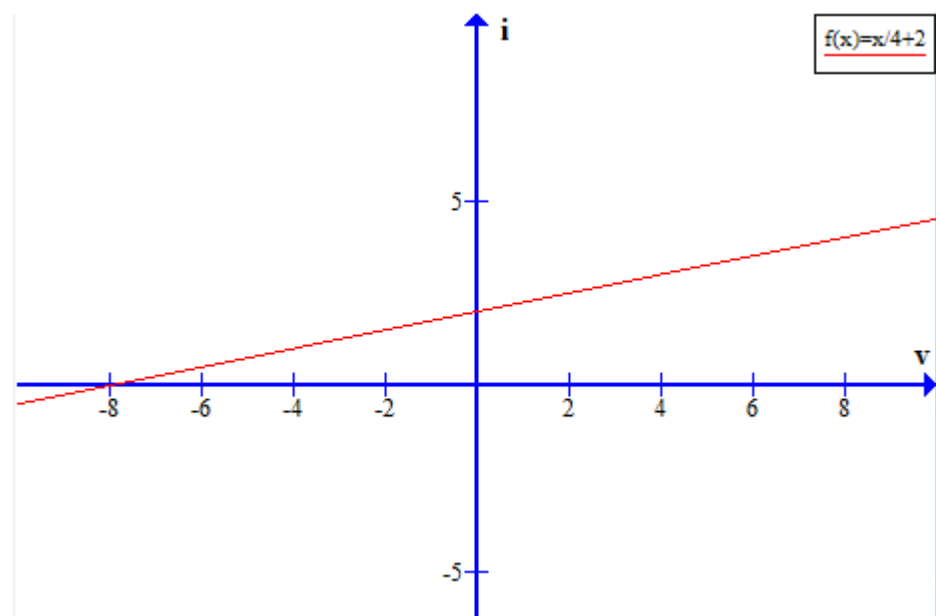

Problem 2.6 In each network in Figure 2.28, find the *numerical* values of the indicated variables (Units are Amperes, Volts and Ohms).

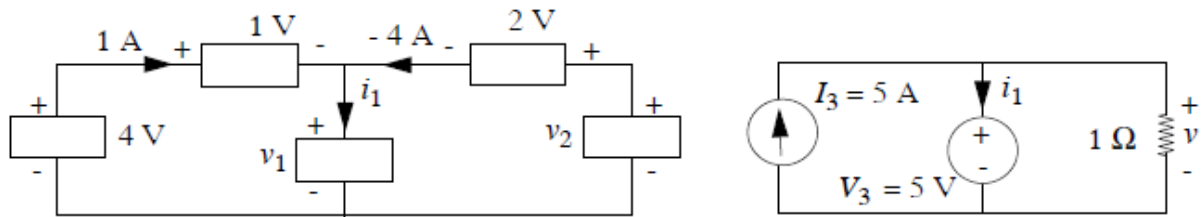


Figure 2.28:

Solution:

Top figure, $v_1 = 4\text{ V} - 1\text{ V} = 3\text{ V}$, $v_2 = 3\text{ V} + 2\text{ V} = 5\text{ V}$, $i_1 = -3\text{ A}$

Bottom figure, since 5V is in parallel across the $1\ \Omega$ resistor, all 5A of I_3 go through the resistor. $v = 5\text{ V}$, $i_1 = 0\text{ A}$

Top: $v_1 = 3\text{ V}$, $v_2 = 5\text{ V}$, $i_1 = -3\text{ A}$, Bottom: $v = 5\text{ V}$, $i_1 = 0\text{ A}$.

ANS:: Top: $v_1 = 3\text{ V}$, $v_2 = 5\text{ V}$, $i_1 = -3\text{ A}$, Bottom: $v = 5\text{ V}$, $i_1 = 0\text{ A}$.

Problem 2.9 Calculate the power dissipated in the resistor R in Figure 2.31.

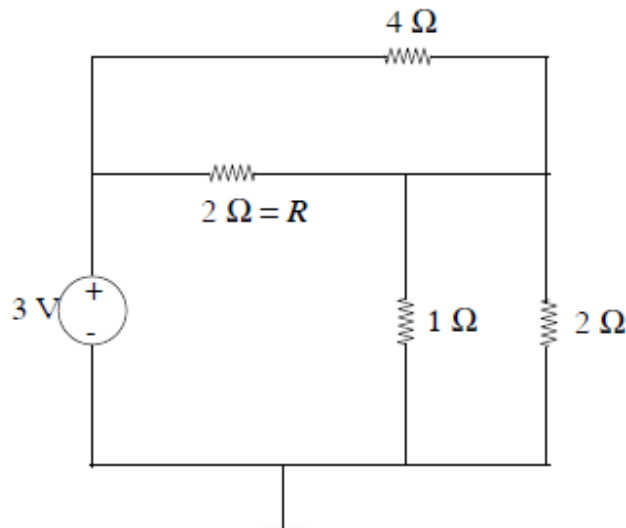


Figure 2.31:

Solution:

The equivalent resistance is $2\ \Omega$, so $\frac{3}{2}\text{ A}$ of current is split between the $2\ \Omega$ and $4\ \Omega$ resistors. Therefore, 1A current goes through R .

$$\text{Power} = 2W$$

$$\text{ANS:: Power} = 2W$$

Problem 2.11 Consider the network in Figure 2.33 in which a non-ideal battery drives a load resistor R_L . The battery is modeled as a voltage source V_S in series with a resistor R_S . The following are some proofs about power transfer.

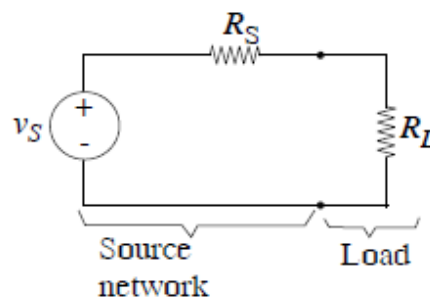


Figure 2.33:

- Prove that for R_S variable and R_L fixed, the power dissipated in R_L is maximum when $R_S = 0$.
- Prove that for R_S fixed and R_L variable, the power dissipated in R_L is maximum when $R_S = R_L$ ("matched resistances").

a) Power dissipated in resistor R_L :

$$P = I_{circuit}^2 R_L$$

$$P = \frac{V_S^2}{(R_S + R_L)^2} R_L$$

$$P|_{R_S=0} = \frac{V_S^2}{(0 + R_L)^2} R_L = \frac{V_S^2}{R_L}$$

$$\lim_{R_S \rightarrow \infty} \frac{V_S^2}{(R_S + R_L)^2} R_L = 0$$

So, power dissipated in R_L maximum when $R_S = 0$. Otherwise power in R_L decreases as R_S increases.

b)

$$P = I_{circuit}^2 R_L$$

$$P = \frac{V_S^2}{(R_S + R_L)^2} R_L$$

Maximize with respect to R_L :

$$\frac{dP}{dR_L} = \frac{(R_S + R_L)^2 (V_S^2) - (V_S^2 R_L)(2(R_S + R_L))}{(R_S + R_L)^4} = 0$$

$$\frac{V_S^2}{(R_S + R_L)^2} = \frac{2V_S^2 R_L}{(R_S + R_L)^3}$$

$$(R_S + R_L)V^2 = 2V^2 R_L$$

$$\rightarrow R_S = R_L \text{ (when this holds power maximized in } R_L)$$