

**Exercise 7.6** Consider the MOSFET amplifier shown in Figure 7.6. Assume that the amplifier is operated under the saturation discipline. In its saturation region, the MOSFET is characterized by the equation

$$i_{DS} = \frac{K}{2}(v_{GS} - V_T)^2$$

where  $i_{DS}$  is the drain-to-source current when a voltage  $v_{GS}$  is applied across its gate-to-source terminals.

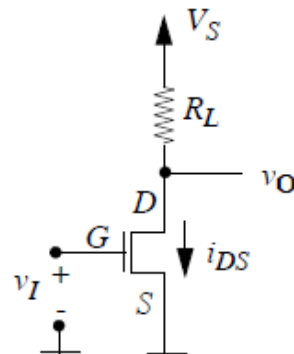


Figure 7.6:

- Draw the equivalent circuit for the amplifier based on the SCS model of the MOSFET.
- Write an expression relating  $v_O$  to  $i_{DS}$ .
- Write an expression relating  $i_{DS}$  to  $v_I$ .
- Write an expression relating  $v_O$  to  $v_I$ .
- Suppose that an input voltage  $V_I$  results in an output voltage  $V_O$ . By what factor must  $V_I$  be increased (or decreased) so that the output voltage is doubled.
- Suppose, again, that an input voltage  $V_I$  results in an output voltage  $V_O$ . Suppose, further, that we desire an output voltage that is  $2V_O$ . Assuming that both the input voltage and the MOSFET do not change, what are all the possible ways of accomplishing the desired doubling of the output voltage.
- The power consumed by the MOSFET amplifier in Figure 7.6 is given by  $V_S i_{DS}$ , assuming that no current is drawn out of the  $v_O$  terminal. Which of the alternatives for doubling  $V_O$  from parts (e) and (f) will result in the lowest power consumption.

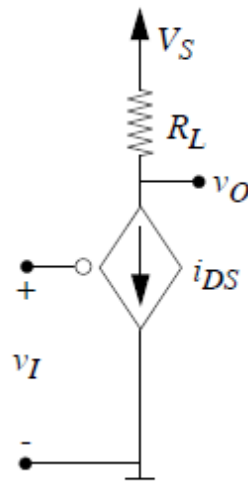


Figure 7.7:

**Solution:**

a) See Figure 7.7.

b)  $v_O = V_S - R_L i_{DS}$

c)  $i_{DS} = \frac{K}{2}(v_I - V_T)^2$  for  $v_I \geq V_T$ ;  $i_{DS} = 0$  otherwise

d)  $v_O = V_S - \frac{R_L K}{2}(v_I - V_T)^2$  for  $v_I \geq V_T$ ;  $v_O = V_S$  otherwise

e)  $V_O = V_S - \frac{R_L K}{2}(V_I - V_T)^2$

$$2V_O = V_S - \frac{R_L K}{2}(NV_I - V_T)^2$$

$$V_S - 2V_O = \frac{R_L K}{2}(NV_I - V_T)^2$$

$$\frac{2}{R_L K}(V_S - 2V_O) = (NV_I - V_T)^2$$

$$NV_I - V_T = \sqrt{\frac{2}{R_L K}(V_S - 2V_O)}$$

$$N = \frac{\sqrt{\frac{2}{R_L K}(V_S - 2V_O)} + V_T}{V_I}; 2V_O \leq V_S$$

Scale  $V_I$  by factor  $N$

f)  $V_O = V_S - \frac{K R_L}{2}(V_I - V_T)^2$

This can be accomplished by changing  $V_S$ ,  $R_L$ , or by changing both.

By changing  $R_L$ :

$$2V_O = V_S - \frac{K R_L N_R}{2}(V_I - V_T)^2$$

$$N_R = \frac{2V_S - 4V_O}{K R_L (V_I - V_T)^2}$$

Scale  $R_L$  by factor  $N_R$ . This will only work if  $2V_O \leq V_S$

By changing  $V_S$ :

$$2V_O = N_S V_S - \frac{K R_L}{2} (V_I - V_T)^2$$

$$N_S = \frac{2V_O + \frac{K R_L}{2} (V_I - V_T)^2}{V_S}$$

Scale  $V_S$  by factor  $N_S$

By changing  $V_S$  and  $R_L$ :

Scale  $V_S$  by factor  $X$  and scale  $R_L$  by factor  $Y$  where

$$X = \frac{2V_O + \frac{K R_L Y}{2} (V_I - V_T)^2}{V_S}. \text{ This will only work if } 2V_O \leq X V_S$$

g) The alternative from part e results in the lowest power consumption.

ANS:: (b)  $v_O = V_S - R_L i_{DS}$  (c)  $i_{DS} = \frac{K}{2} (v_I - V_T)^2$  for  $v_I \geq V_T$ ;  $i_{DS} = 0$  otherwise

(d)  $v_O = V_S - \frac{R_L K}{2} (v_I - V_T)^2$  for  $v_I \geq V_T$ ;  $v_O = V_S$  otherwise (e)  $N = \frac{\sqrt{\frac{2}{R_L K} (V_S - 2V_O) + V_T}}{V_I}$   
 (g) e

**Exercise 7.9** Consider the bipolar junction transistor (BJT) amplifier shown in Figure 7.10. Assume that the BJT is characterized by the large signal model from Exercise 7.8, and that the BJT operates in its active region. Assume further that  $V_S = 5V$ ,  $R_L = 10k$ ,  $R_I = 500k$ , and  $\beta = 100$ .


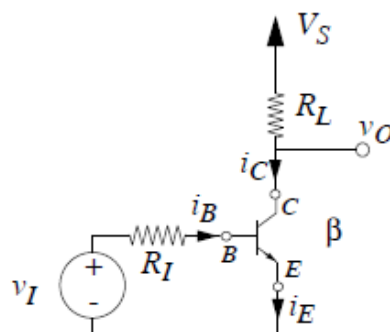


Figure 7.10:

- Draw the equivalent circuit for the BJT amplifier based on the large signal BJT model from Exercise 7.8.
- Write an expression relating  $v_O$  to  $i_C$ .
- Write an expression relating  $i_C$  to  $v_I$ .
- Write an expression relating  $i_E$  to  $i_B$ .
- Write an expression relating  $v_O$  to  $v_I$ .
- What is the value of  $v_O$  for an input voltage  $v_I = 0.7V$ ? What are the corresponding values of  $i_B$ ,  $i_C$  and  $i_E$ .

**Solution:**

a)

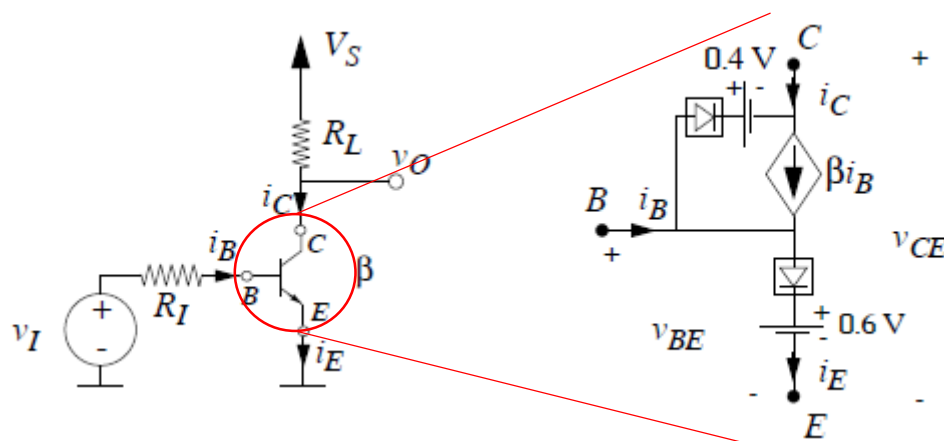

b)

$$v_O = V_S - i_C R_L$$

c)

$$i_C = \beta i_B = \beta \frac{v_I - 0.6}{R_I}$$

d)

$$i_E = i_B(\beta + 1)$$

e)

$$v_O = V_S - \frac{v_I - 0.6}{R_I} \beta R_L$$

Or, substituting known values

$$v_O = 6.2 - 2v_I$$

f)  $v_O = 4.8V$ ,  $i_B = 0.2\mu A$ ,  $i_C = 20\mu A$ , and  $i_E = 20.2\mu A$ .

ANS:: (b)  $v_O = V_S - i_C R_L$  (c)  $i_C = \beta \frac{v_I - 0.6}{R_I}$  (d)  $i_E = i_B(\beta + 1)$  (e)  $v_O = 6.2 - 2v_I$   
(f)  $v_O = 4.8V$ ,  $i_B = 0.2\mu A$ ,  $i_C = 20\mu A$ , and  $i_E = 20.2\mu A$ .

**Exercise 7.10** In this exercise you will perform a large signal analysis of the BJT amplifier shown in Figure 7.10. Assume that the BJT is characterized by the large signal model from Exercise 7.8. Assume further that  $V_S = 5V$ ,  $R_L = 10k$ ,  $R_I = 500k$ , and  $\beta = 100$ .

- Write an expression relating  $v_O$  to  $v_I$ .
- What is the lowest value of the input voltage  $v_I$  for which the BJT operates in its active region? What are the corresponding values of  $i_B$ ,  $i_C$ , and  $v_O$ ?
- What is the highest value of the input voltage  $v_I$  for which the BJT operates in its active region? What are the corresponding values of  $i_B$ ,  $i_C$ , and  $v_O$ ?
- Sketch a graph of  $v_O$  versus  $v_I$  for the parameter values given above.

Solution:

a)

$$v_O = V_S - \frac{v_I - 0.6}{R_I} \beta R_L$$

Or, substituting known values

$$v_O = 6.2 - 2v_I$$

b)

$$v_I = 0.6V$$

The BJT goes into cutoff if  $v_I$  goes any lower.

The corresponding values of  $i_B$ ,  $i_C$ , and  $v_O$  are as follows.  $i_B = 0$ ,  $i_C = 0$ , and  $v_O = 5V$ .

- c) As  $v_I$  increases, the BJT enters saturation when the collector diode gets forward biased. This happens when the base voltage is greater than the collector voltage by 0.4V. In other words, when  $v_{CE} = v_{BE} - 0.4$ , or when  $v_{CE} = v_O$  falls to 0.2V. The corresponding value of  $v_I$  is obtained by solving

$$v_O = 0.2 = 6.2 - 2v_I$$

Solving, we get  $v_I = 3V$ . In other words, when  $v_I$  rises to 3V, the output falls to 0.2V, and the BJT goes into saturation.

The corresponding values of  $i_B$ ,  $i_C$ , and  $v_O$  are as follows.  $i_B = 24/5\mu A$ ,  $i_C = 480\mu A$ , and  $v_O = 0.2V$ .

d) A graph of  $v_O$  versus  $v_I$  is made up of three straightline segments.

In the first segment,  $v_O$  is at 5V for  $v_I$  ranging from 0V to 0.6V.

In the second segment,  $v_O$  decreases linearly from 5V to 0.2V as  $v_I$  increases from 0.6V to 3V. In other words, the second segment follows the equation

$$v_O = 0.2 = 6.2 - 2v_I$$

for  $v_I = 0.6V$  to  $v_I = 3V$ .

In the third segment,  $v_O$  stays at 0.2V for  $v_I$  greater than 3V.

ANS:: (a)  $v_O = 6.2 - 2v_I$  (b)  $v_I = 0.6V$ ,  $i_B = 0$ ,  $i_C = 0$ , and  $v_O = 5V$ . (c)  $v_I = 3V$ ,  $i_B = 24/5\mu A$ ,  $i_C = 480\mu A$ , and  $v_O = 0.2V$ .

**Problem 7.1** Consider the MOSFET voltage divider circuit shown in Figure 7.11. Assume that both MOSFETs operate in the saturation region. Determine the output voltage  $V_O$  as a function of the supply voltage  $V_S$ , the gate voltages  $V_A$  and  $V_B$ , and the MOSFET geometries  $L_1, W_1$  and  $L_2, W_2$ . Assume that the MOSFET threshold voltage is  $V_T$ , and remember,  $K = K_n \frac{W}{L}$ .

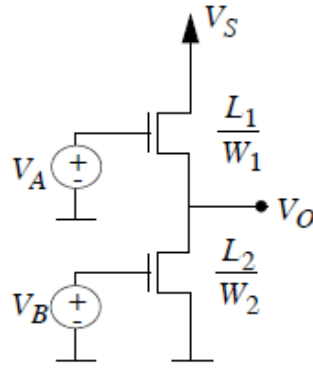


Figure 7.11:

**Solution:**

Since the current through both MOSFETs must be the same,  $V_O$  is forced to a value such that this is the case.

$$\frac{K_n W_2}{2L_2} (V_B - V_T)^2 = \frac{K_n W_1}{2L_1} (V_A - V_O - V_T)^2$$

$$V_O = V_A - V_T - \sqrt{\frac{W_2 L_1}{L_2 W_1}} (V_B - V_T)^2$$

$$\text{ANS:: } V_O = V_A - V_T - \sqrt{\frac{W_2 L_1}{L_2 W_1}} (V_B - V_T)^2$$



## Problem 7.2

Solution:

- a) When there is current going through  $R$ , the current is limited by two quantities: either  $\frac{V_S}{R}$  or  $\frac{K}{2}(v_{GS} - V_T)^2$ , whichever is lower. If the limit is  $V_S/R$ , then the MOSFET is in the closed-switch region. If the limit is  $\frac{K}{2}(v_{GS} - V_T)^2$ , then the MOSFET is in the saturation region.

**open-switch region** For  $v_{GS} \leq V_T$ , the MOSFET is open, therefore  $v_{OUT} = V_S$ .

**saturation region** When  $v_{GS}$  begins to exceed  $V_T$ , the quantity  $v_{GS} - V_T$  is still small, so the current is limited by  $\frac{K}{2}(v_{GS} - V_T)^2$ . This current determines the output voltage, which is given by  $v_{OUT} = V_S - \frac{KR}{2}(v_{IN} - V_T)^2$ .

**closed-switch region**  $i_{DS}$  increases until it reaches  $\frac{V_S}{R}$  at some gate voltage  $V_{IN_T}$ . Now  $v_{DS}$  drops to zeros, and both  $i_{DS}$  and  $v_{DS}$  are no longer affected by the increase in  $v_{GS}$ .

In summary,

$$v_{OUT} = \begin{cases} V_S & 0 \leq v_{IN} \leq V_T \\ V_S - \frac{KR}{2}(v_{IN} - V_T)^2 & v_T \leq v_{IN} \leq V_{IN_T} \\ 0 & V_{IN_T} \leq v_{IN} \leq V_{IN_{MAX}} \end{cases}$$

- b) The lowest value of  $v_{IN}$  for which  $v_{OUT} = 0$  occurs when  $v_{IN}$  is at the *transition* between the saturation region and the closed-switch region. At this point, the saturation region current limit and the closed-switch region current limit are the same,

$$i_{DS} = \frac{V_S}{R} = \frac{K}{2}(V_{IN_T} - V_T)^2$$

Solving for  $V_{IN_T}$  we get


$$V_{IN_T} = \sqrt{\frac{2V_S}{KR}} + V_T$$

- c) Combining the results of part (a) and (b), we obtain the following equations.

$$v_{OUT} = \begin{cases} 15 & 0 \leq v_{IN} \leq 1 \\ 15 - 15(v_{IN} - 1)^2 & 1 \leq v_{IN} \leq 2 \\ 0 & 2 \leq v_{IN} \leq 3 \end{cases}$$

The graph is shown in the figure.

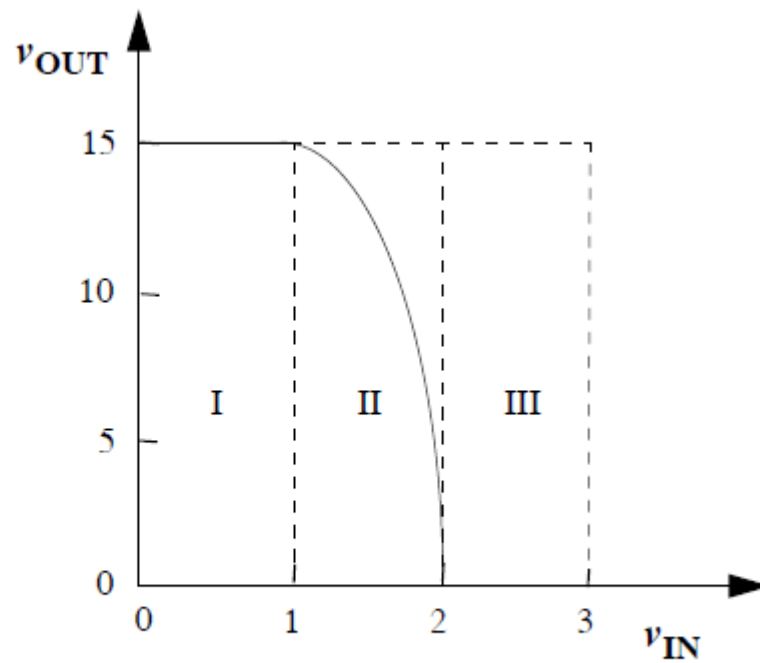- d) Region I is the open switch region, where  $v_{OUT} = V_S = 15$ . Region II is the saturation region, where  $v_{OUT}$  drops according to  $V_S - \frac{KR}{2}(v_{IN} - V_T)^2$ . The MOSFET enters the closed-switch region when  $v_{IN} = V_{IN_{cr}} = 2$ . In this region,  $v_{OUT} = 0$ .



ANS:: (b)  $V_{IN_T} = \sqrt{\frac{2V_S}{KR}} + V_T$

**Problem 7.14** Figure 7.28 shows a MOSFET amplifier driving a load resistor  $R_E$ . The MOSFET operates in saturation and is characterized by parameters  $K$  and  $V_T$ . Determine  $v_{OUT}$  versus  $v_{IN}$  for the circuit shown.

Solution:

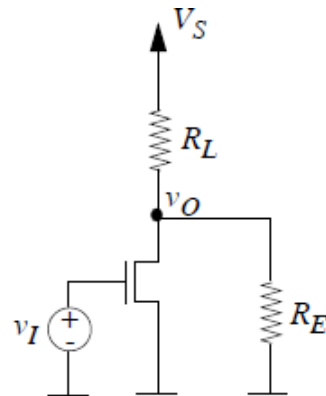


Figure 7.28:

First of all, assume that the circuit is in saturation. Call the three currents as follows: through resistor  $R_L$ :  $I_1$ , through the MOSFET:  $I_2$ , and through resistor  $R_E$ :  $I_3$ . All three of them point from higher voltage to lower, so therefore  $I_1 = I_2 + I_3$ . This is shown in Figure 7.29.

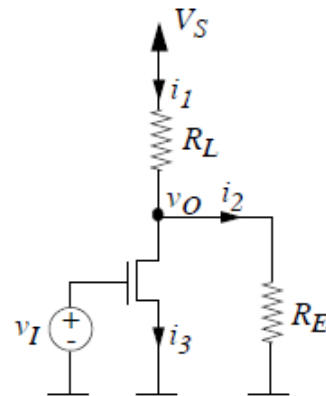


Figure 7.29:

The three currents can be determined in terms of  $v_{IN}$ ,  $v_{OUT}$ , and MOSFET parameters:

$$\begin{aligned} v_{OUT} &= I_3 R_E, \\ V_S - I_1 R_L &= v_{OUT}, \\ I_2 &= \frac{K}{2} (v_{IN} - V_T)^2. \end{aligned}$$

Substituting this into the KCL equation and solving for  $v_{OUT}$ , we get

$$v_{OUT} = \frac{V_S - \frac{KR_L}{2}(v_{IN} - V_T)^2}{1 + \frac{R_L}{R_E}} = \frac{2V_S R_E - KR_E R_L (v_{IN} - V_T)^2}{2(R_L + R_E)}.$$

However, this only applies for when the MOSFET is in saturation. We must find the range of  $v_{IN}$  for which this holds valid. The boundary between saturation and cutoff is merely  $v_{IN} \geq V_T$ . The boundary between saturation and triode can be found as follows.

$$\frac{2V_S R_E - R_E R_L K (v_{IN} - V_T)^2}{2(R_L + R_E)} \geq v_{IN} - V_T.$$

Solving this for  $v_{IN}$ , one gets the following boundary conditions for saturation:

$$V_T \leq v_{IN} \leq V_T + \frac{R_L + R_E}{KR_L R_E} + \sqrt{\frac{1}{K^2} \left( \frac{1}{R_L} + \frac{1}{R_E} \right)^2 + \frac{2V_S}{KR_L}}.$$

For the cutoff region, we can find the output voltage through a simple voltage divider relation, since no current flows through the MOSFET:

$$v_{OUT} = V_S \frac{R_E}{R_E + R_L}.$$

The voltage transfer characteristic for triode region will not be considered for this problem.

$$\text{ANS:: } v_{OUT} = \frac{2V_S R_E - KR_E R_L (v_{IN} - V_T)^2}{2(R_L + R_E)}$$

**Problem 7.17** Determine  $v_O$  versus  $v_I$  for the circuit shown in Figure 7.34. Assume that the MOSFET operates in saturation and is characterized by the parameters  $K$  and  $V_T$ .

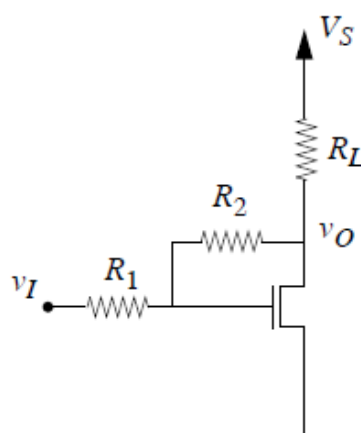


Figure 7.34:

Solution:

First of all, define  $v_G$  to be the gate voltage. Also, define three currents  $i_1$ ,  $i_2$ , and  $i_3$  to be the currents flowing through  $R_L$ ,  $R_2$ , and the MOSFET, respectively. Define  $i_3$  to be flowing towards ground, and let  $i_1 + i_2 = i_3$ . This is shown in Figure 7.35.

The gate voltage can be found through a voltage divider rule since no current flows from between  $R_1$  and  $R_2$  to the gate.

$$v_G = \frac{R_2}{R_1 + R_2} v_{IN} + \frac{R_1}{R_1 + R_2} v_{OUT}$$

In cutoff, the output voltage and the input voltage are related by a voltage divider rule:

$$v_{OUT} = \frac{V_S(R_1 + R_2) + V_{IN}R_L}{R_1 + R_2 + R_L}$$

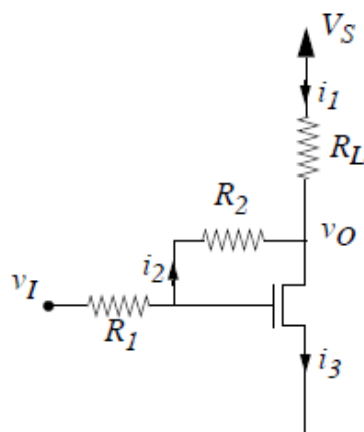


Figure 7.35:

In saturation, we have an extra current to worry about. We substitute into our original KCL equation to get

$$\frac{V_S - v_{\text{OUT}}}{R_L} + \frac{v_{\text{IN}} - v_{\text{OUT}}}{R_L} = \frac{K}{2} \left( \frac{R_2}{R_1 + R_2} v_{\text{IN}} + \frac{R_1}{R_1 + R_2} v_{\text{OUT}} - V_T \right)^2$$

We can solve this for  $v_{\text{OUT}}$ , but it ends up being quite monstrous. Let  $R_T = R_1 + R_2$ .

$$v_{\text{OUT}} = \frac{R_2 R_T V_T}{R_1^2} - \frac{R_2 v_{\text{IN}}}{R_1} - \frac{R_T^2}{K R_L R_1} - \frac{R_T}{K R_1^2} + \frac{\sqrt{L + M + N}}{2 K R_L R_1},$$

with the following subexpressions:

$$L = R_T^2 (R_T + R_L)^2,$$

$$M = K^2 R_L^2 R_T^2 V_T (R_1 - R_2) (2v_{\text{IN}} R_1 - V_T R_T),$$

$$N = 2K (V_S R_L R_1^2 R_T^2 - V_T R_1 R_2 R_T^2 (R_1 + R_2 + R_L) + v_{\text{IN}} R_L R_1 R_T^2 (R_L + R_2)).$$

The boundaries for which the device is in saturation can be found by evaluating  $v_G \geq V_T$  and  $v_{\text{OUT}} \geq v_G - v_T$ . This evaluation is even more complicated than the previous equation, since  $v_G$  is given in terms of  $v_{\text{OUT}}$ , and needs to be put in terms of  $v_{\text{IN}}$ . In terms of both  $v_{\text{IN}}$  and  $v_{\text{OUT}}$ , the boundary conditions are derived much more easily.

Between saturation and cutoff:

$$\frac{R_2}{R_1 + R_2} v_{\text{IN}} + \frac{R_1}{R_1 + R_2} v_{\text{OUT}} \geq V_T$$

Between saturation and triode:

$$v_{\text{OUT}} \geq v_{\text{IN}} - \frac{R_1 + R_2}{R_2} v_T$$

**Problem 7.19** Consider the compound three terminal device formed by connecting two BJTs in the configuration shown in Figure 7.37. The three terminals are labeled  $C'$ ,  $B'$  and  $E'$ . The two BJTs are identical, each with  $\beta = 100$ . Assume that each of the BJTs operates in the active region.


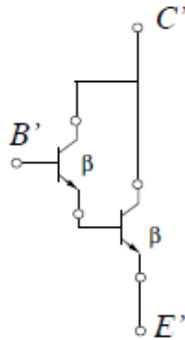


Figure 7.37:

- Draw the active-region equivalent circuit of the compound BJT by replacing each of the BJTs by the piecewise linear model shown in Exercise 7.8. Clearly label the  $C'$ ,  $B'$  and  $E'$  terminals.
- In the configuration shown, the compound device behaves like a BJT. Determine the value of the current gain  $\beta'$  for this compound BJT.
- When the base current  $i_{B'} > 0$ , determine the voltage between the  $B'$  and  $E'$  terminals.

**Solution:**

a)

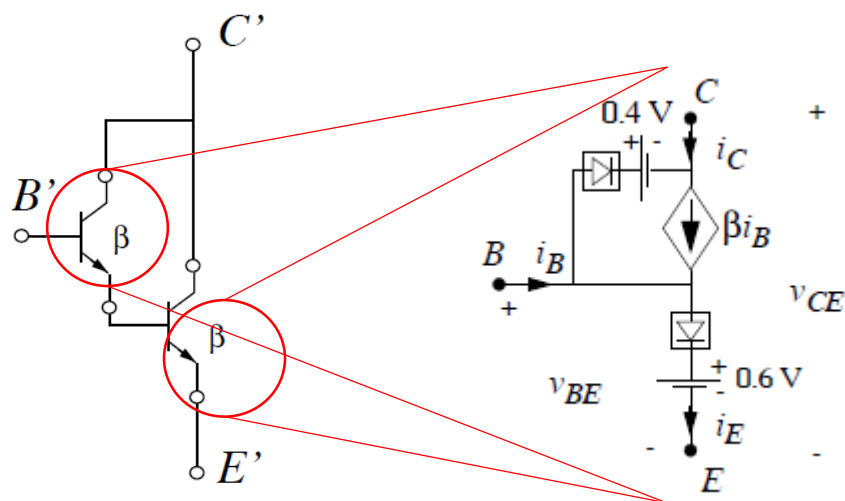

b) The current gain of the new device is given by

$$\beta' = (\beta + 2)\beta$$

c) When the base current  $i_{B'} > 0$ , both transistors are in their active region. In this situation, the voltage between the  $B'$  and  $E'$  terminals is 1.2V.

ANS:: (b)  $\beta' = (\beta + 2)\beta$  (c) 1.2V