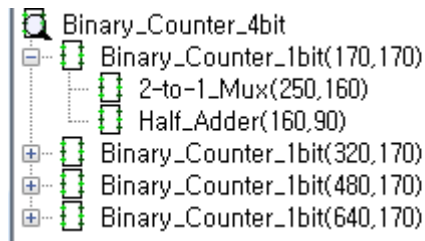


## Homework #2.

### 010.133 Digital Computer Concept and Practice

**Due Date: 11:59PM, April 10, 2013**

1. Make a circuit of 4-bit binary counter using logisim. Your circuit should follow the following restrictions.
  - Multiplexer should be built with tristate buffers(controlled buffer)
  - You may use the built-in D Flip-Flops
  - Half-adder should be built with logic gates.
  - There should be 4 input pins(inc, load, clock, i0~i3) and 1 output pin(o0~o3)
  - Hierarchical tree should look like **Figure1**



**Figure 1**

2. Using 2 4-bit binary counters, make a 8-bit binary counter. Your circuit should follow the following restrictions.
  - You can use built-in 4-bit binary counter of logisim, or you can use the circuit of your own.
  - There should be 4 input pins(inc, load, clock, i0~i7) and 1 output pin(o0~o7)
3. Submit a report for your circuit. Your report should include the followings.
  - Submit a full log of your 4-bit binary counter. Your log should show the counting operation and the operation of load input.
  - Justify that your 8-bit binary counter works correctly.

### Submission

- ① The logisim circuit file name should be "HW#2\_StudentID\_NAME.circ"
- ② The report file name should be "HW#2\_StudentID\_NAME.pdf"
- ③ It's ok to transform from .docx or .hwp to .pdf
- ④ Send email to TA([dccpta@aces.snu.ac.kr](mailto:dccpta@aces.snu.ac.kr)) with attached files.