

Logic Circuits II


010.133
Digital Computer Concept and Practice
Spring 2013

Lecture 04

Arithmetic Unit


- Integer addition and subtraction
- Two's complement representation

S_1	S_0	Y	$C_{in} = 0$	$C_{in} = 1$
0	0	$00 \cdots 0$	$F = A$	$F = A + 1$
0	1	B	$F = A + B$	$F = A + B + 1$
1	0	B'	$F = A + B'$	$F = A + B' + 1$
1	1	$11 \cdots 1$	$F = A - 1$	$F = A$

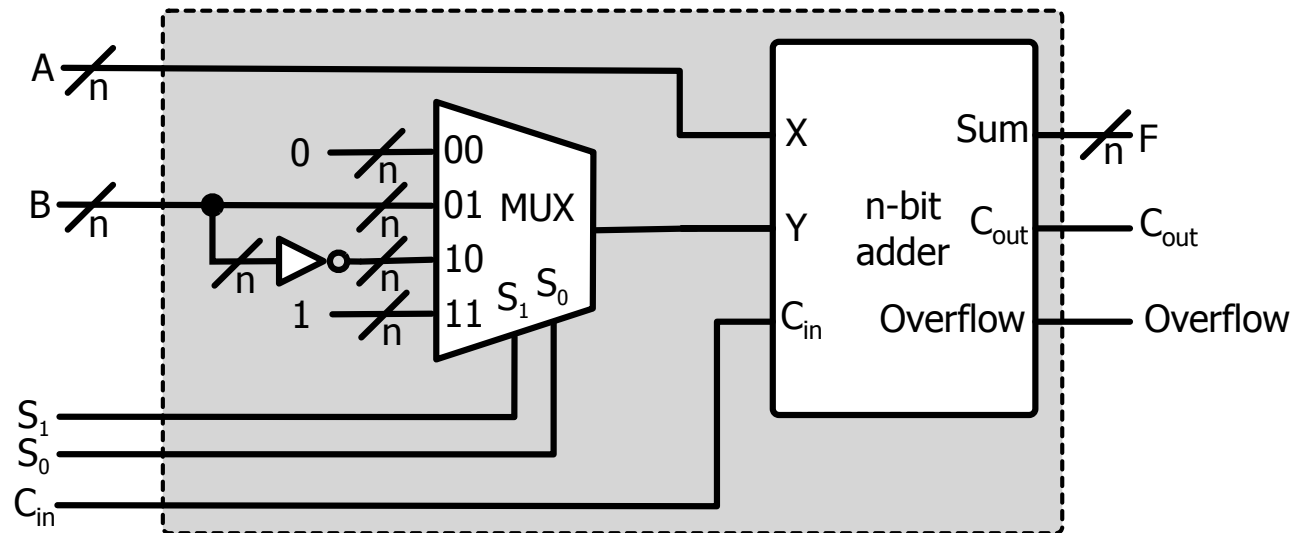


- Bitwise OR, AND, XOR, and NOT

S_1	S_0	output	operation
0	0	$F = A \vee B$	OR
0	1	$F = A \wedge B$	AND
1	0	$F = A \oplus B$	XOR
1	1	$F = A'$	NOT

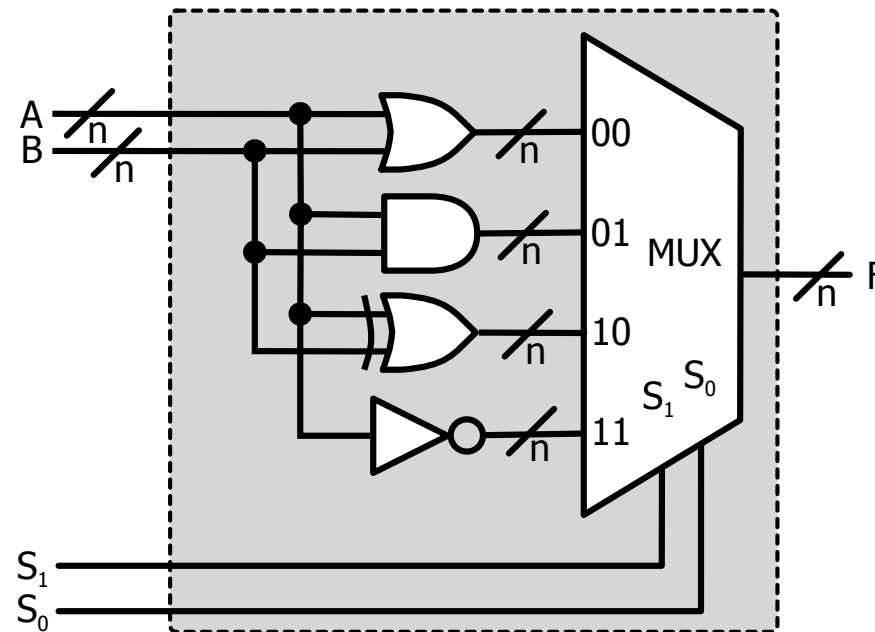

- Arithmetic unit + logic unit


S ₂	S ₁	S ₀	C _{in}	Operation
0	0	0	0	$F = A$
0	0	0	1	$F = A + 1$
0	0	1	0	$F = A + B$
0	0	1	1	$F = A + B + 1$
0	1	0	0	$F = A + B'$
0	1	0	1	$F = A + B' + 1$
0	1	1	0	$F = A - 1$
0	1	1	1	$F = A$
1	0	0	X	$F = A \vee B$
1	0	1	X	$F = A \wedge B$
1	1	0	X	$F = A \oplus B$
1	1	1	X	$F = A'$

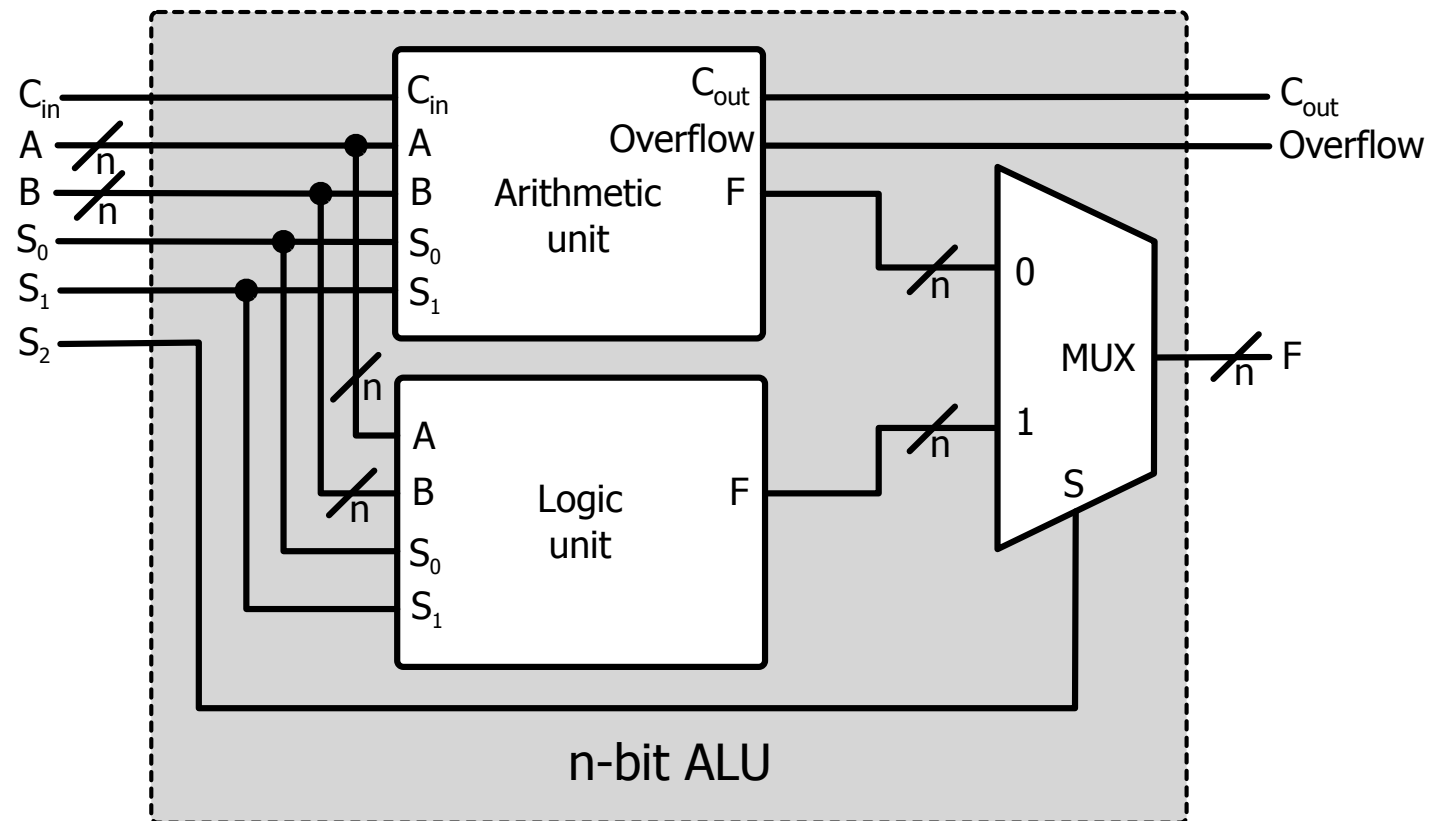


ALU in a Broader Sense

- ALU + shifter

FS ₄	FS ₃	FS ₂	FS ₁	FS ₀	Operation
0	0	0	0	0	$F = A$
0	0	0	0	1	$F = A + 1$
0	0	0	1	0	$F = A + B$
0	0	0	1	1	$F = A + B + 1$
0	0	1	0	0	$F = A + B'$
0	0	1	0	1	$F = A + B' + 1$
0	0	1	1	0	$F = A - 1$
0	0	1	1	1	$F = A$
0	1	0	0	X	$F = A \vee B$
0	1	0	1	X	$F = A \wedge B$
0	1	1	0	X	$F = A \oplus B$
0	1	1	1	X	$F = A'$
1	0	0	X	X	$F = B$
1	0	1	0	X	$F = \text{logical shift right } B$
1	0	1	1	X	$F = \text{arithmetic shift right } B$
1	1	0	X	X	$F = \text{shift left } B$
1	1	1	X	X	$F = B$

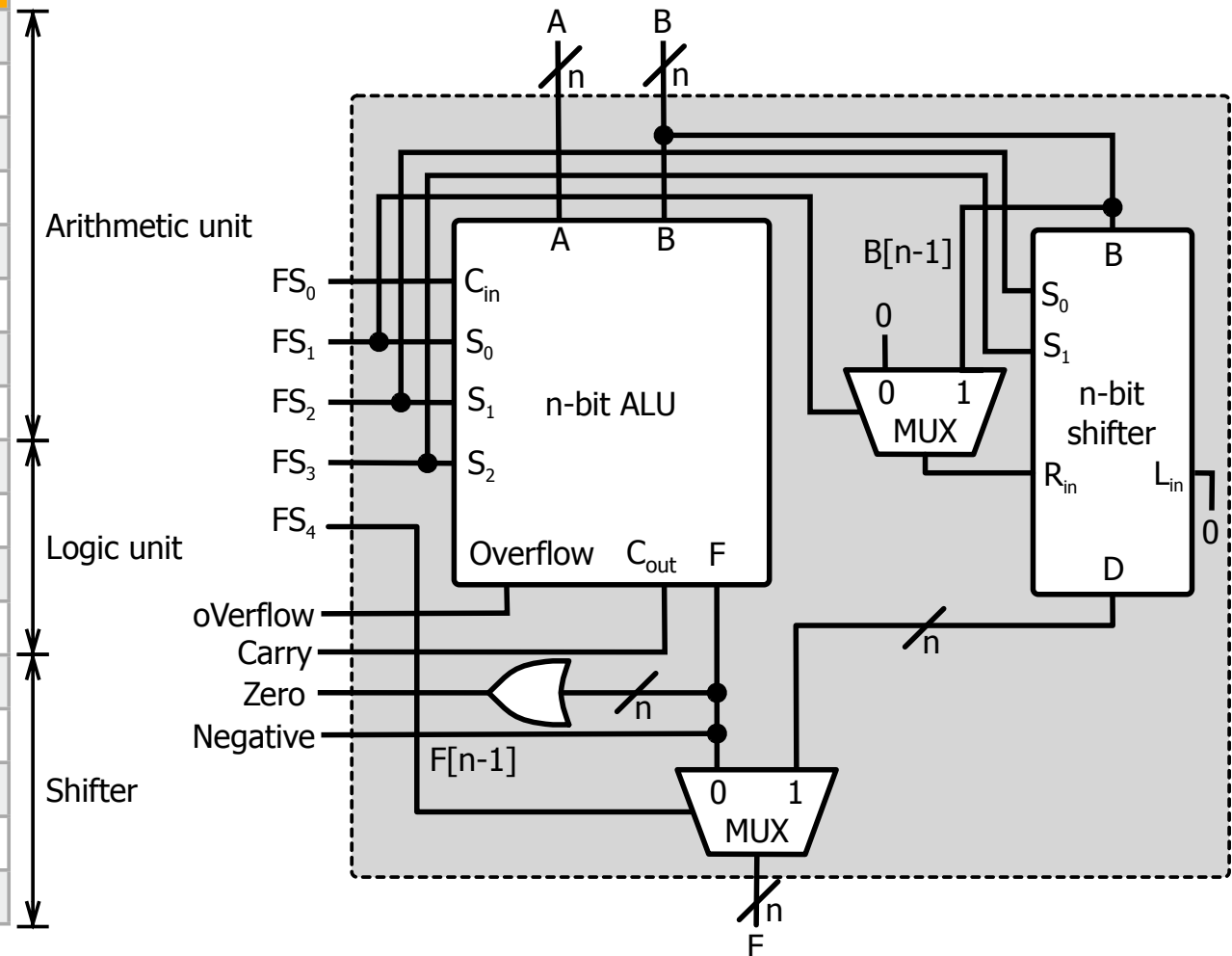

ALU Symbol

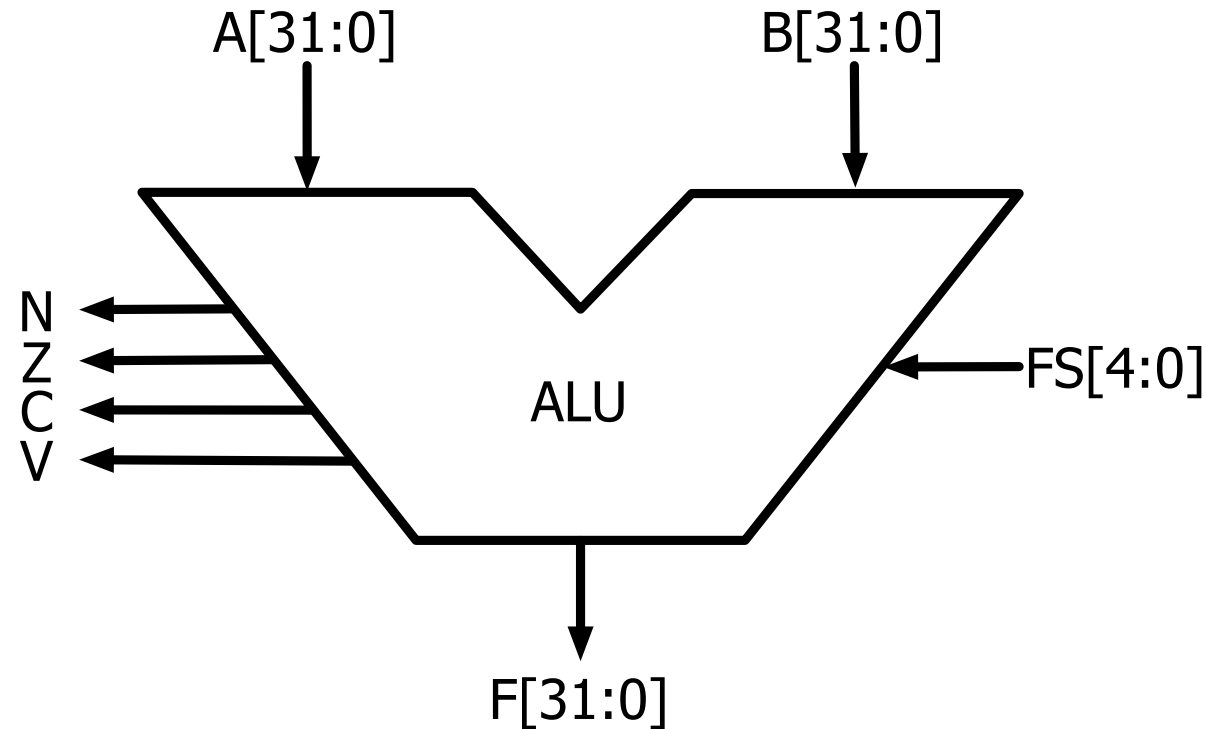


Combinational Logic vs. Sequential Logic

- The outputs of a combinational logic circuit
 - Totally dependent on the current input values and determined by combining the input values using Boolean operations
- The outputs of a sequential logic circuit
 - Depend not only on the current input values but also on the past inputs
 - Logic gates + memory
 - Outputs are a function of the current input values and the data stored in memory
 - A function of time
 - States



Clock

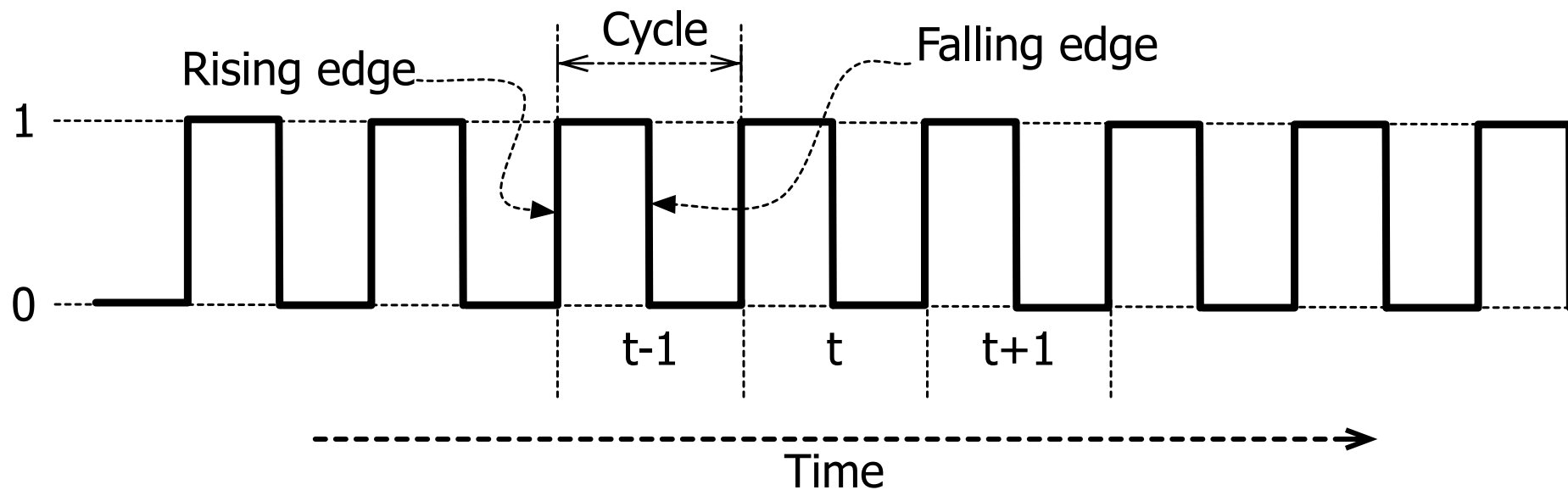- The clock signal is simultaneously broadcast to every circuit component
- Every operation in the circuit must be completed inside a clock cycle




- Also known as propagation delay
- The time delay between the changes when an input change causes an output change

The D Flip-flop


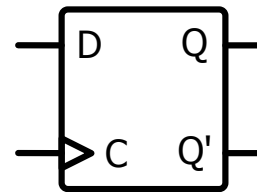
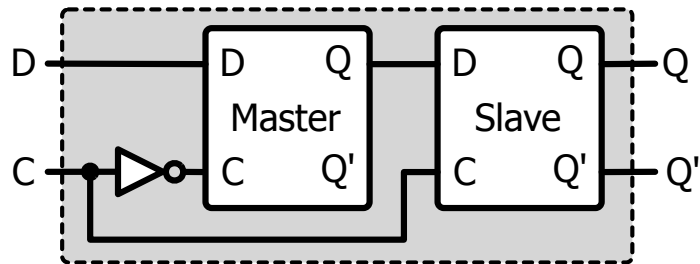


Asynchronous inputs:
preset and clear

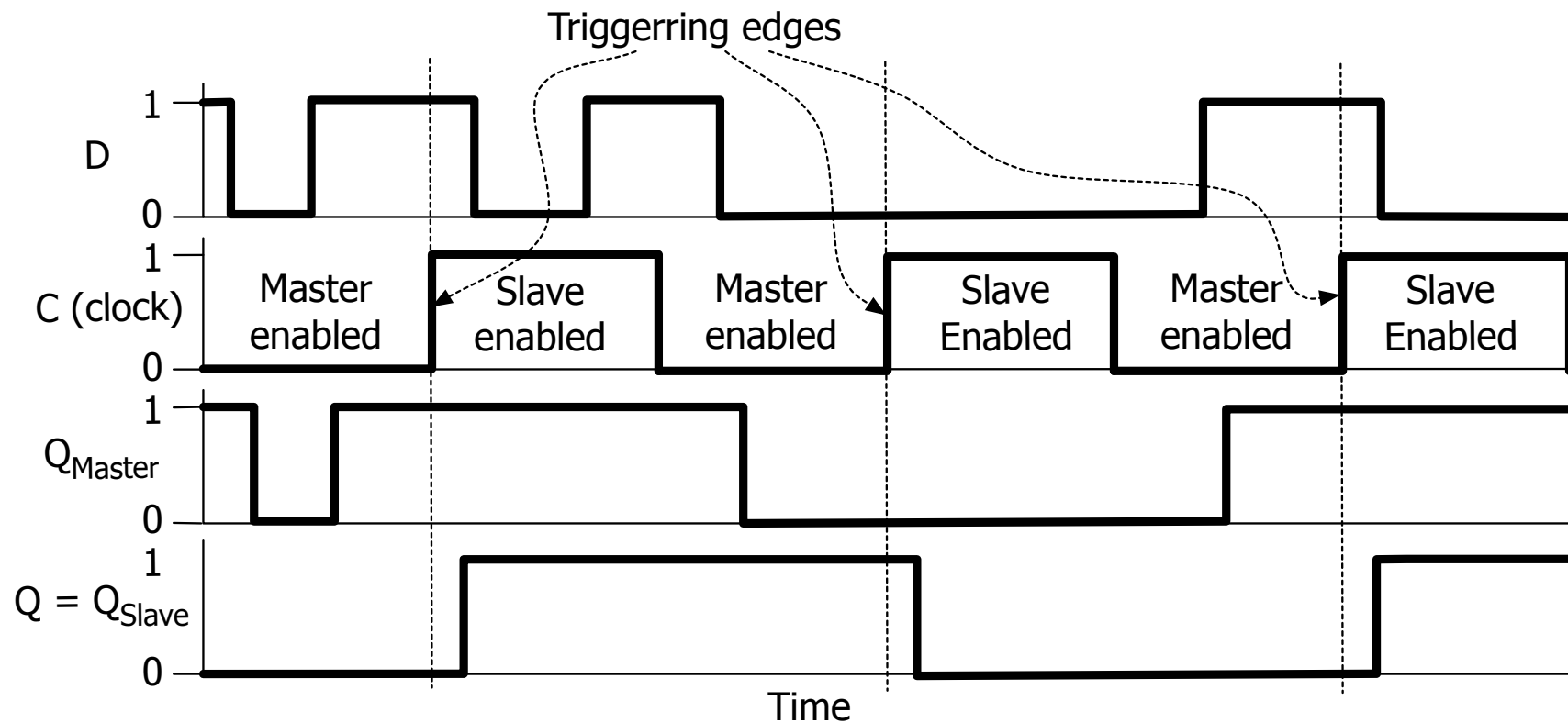



Registers

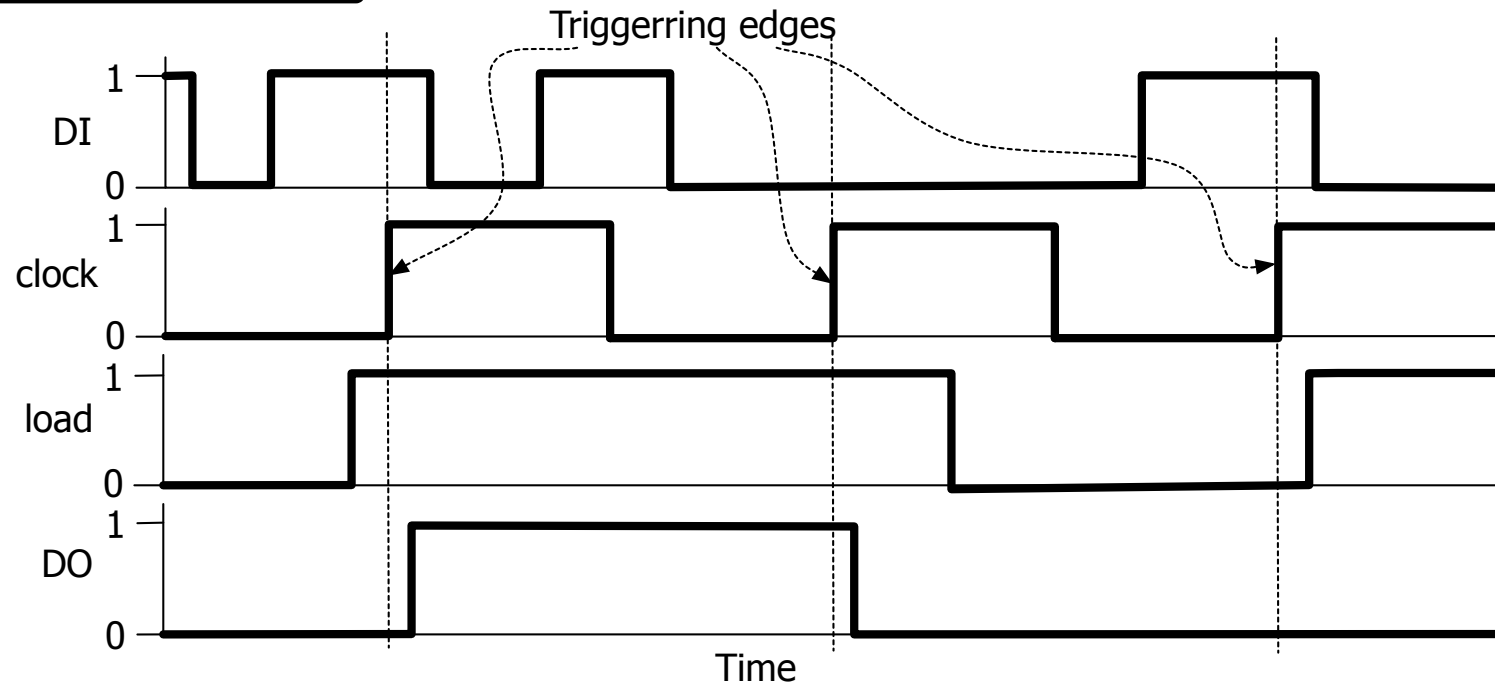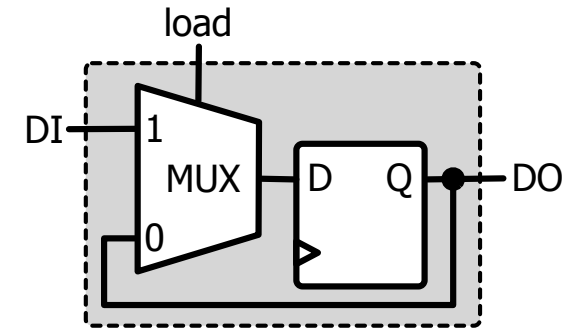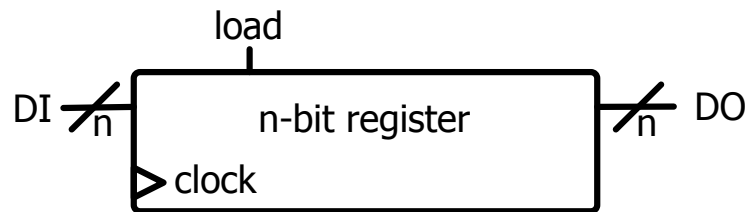- A register is a storage device that can store binary information over time
 - It is a collection of one or more flip-flops





- An n -bit counter is an n -bit register that goes through a predetermined sequence of states upon the application of the clock signal
- A counter that follows the binary number sequence is called a binary counter

Binary Counters (contd.)

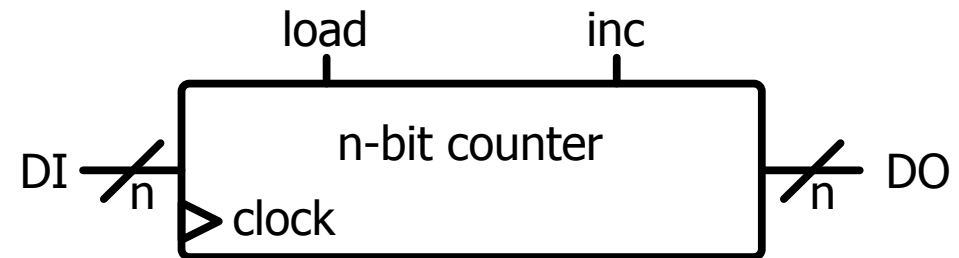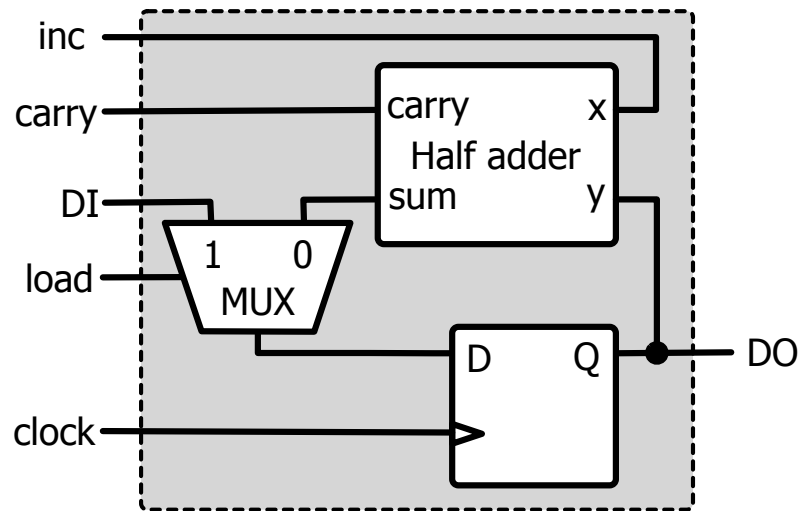


Binary Counters (contd.)

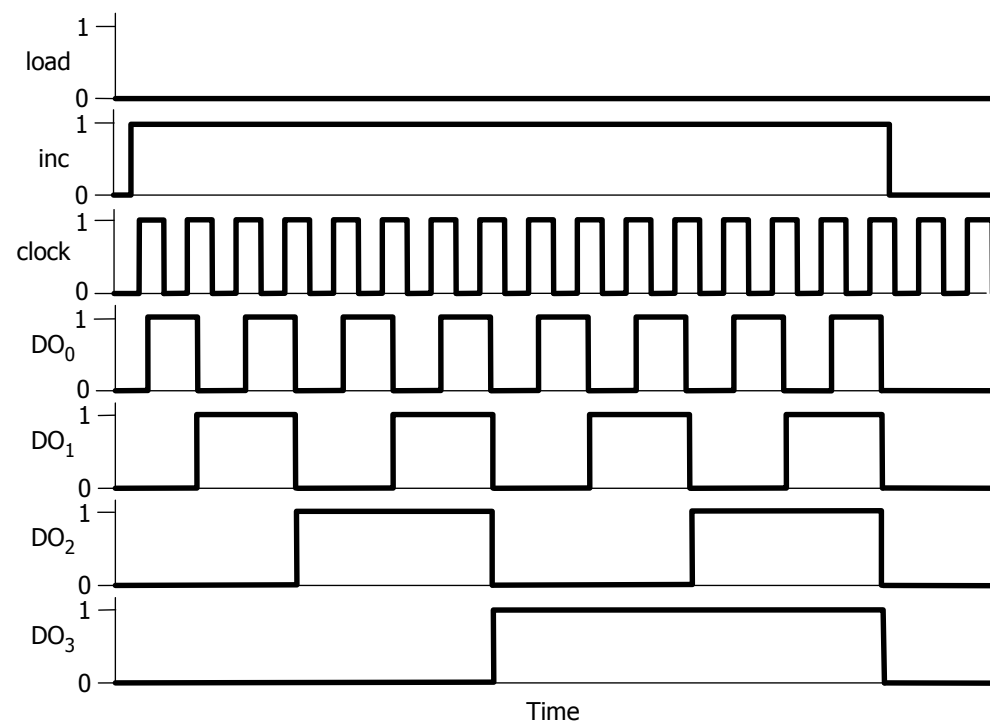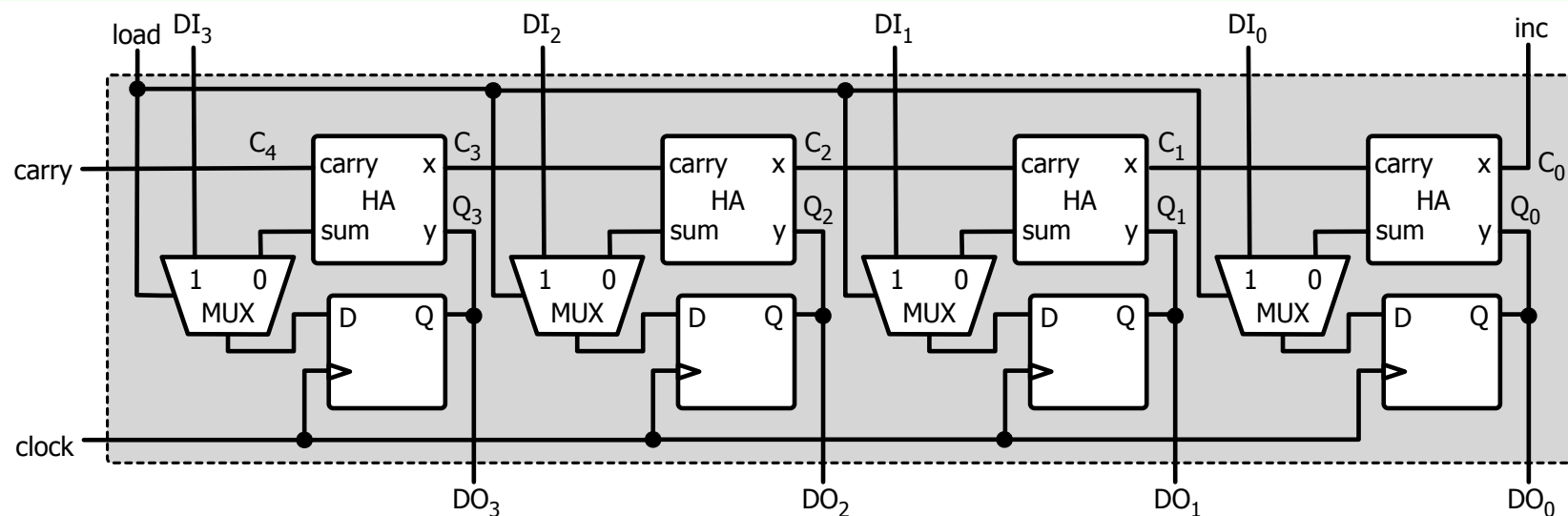

Register Files



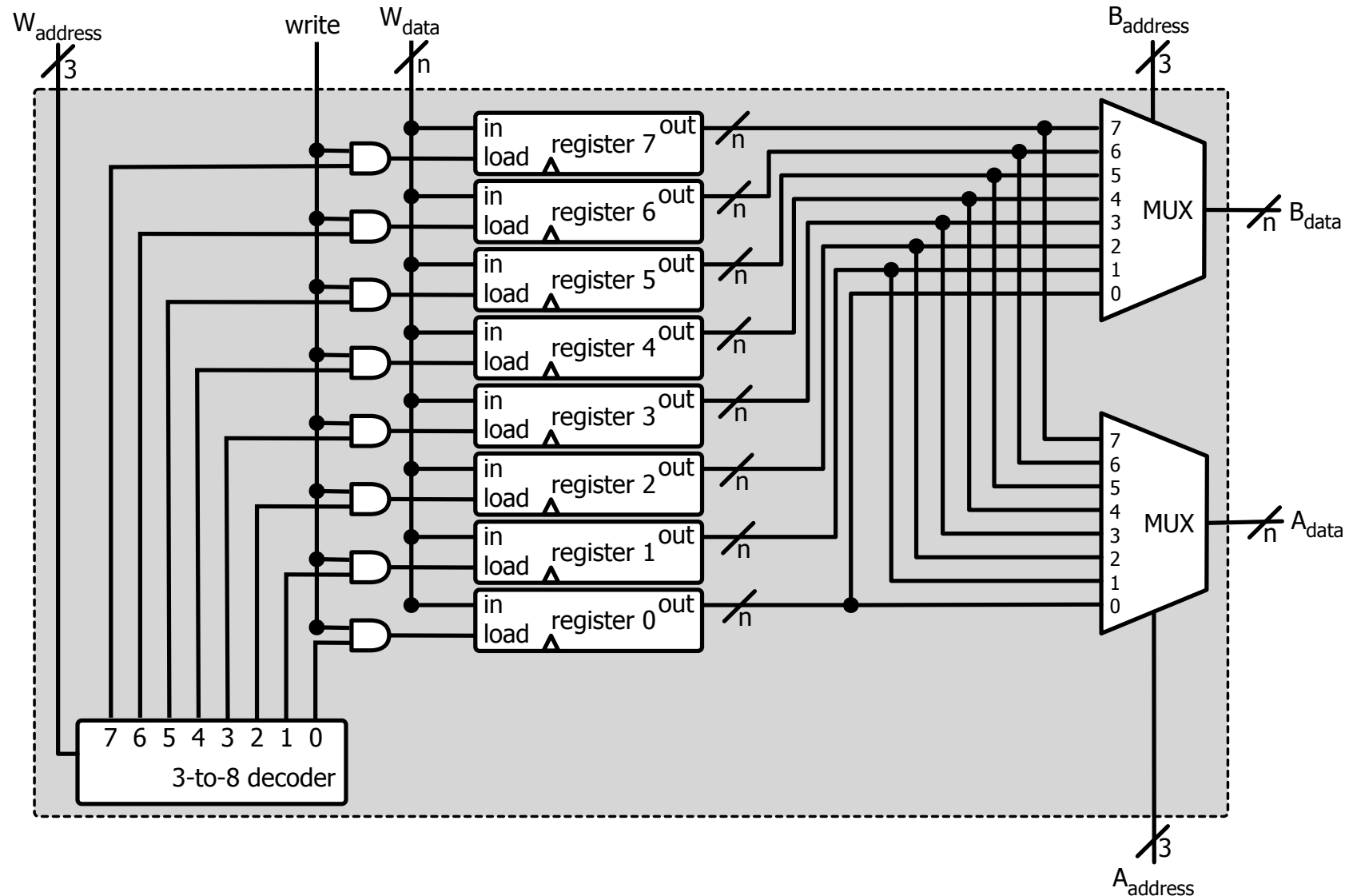
- A register file is an array of registers in a CPU



Tristate Buffers





- Also known as tristate drivers
- A third state, called a high-impedance state and denoted as Hi – Z, in addition to 0 and 1

E	D	O
0	X	Hi-Z
1	0	0
1	1	0

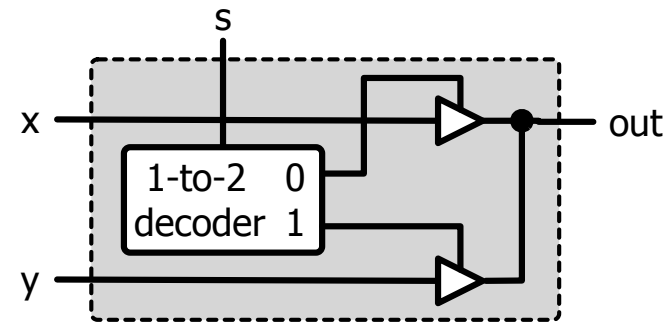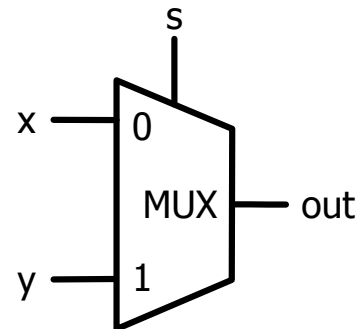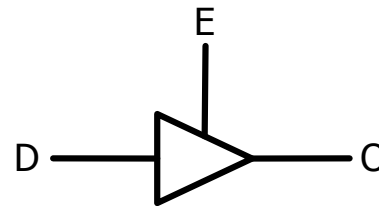


- Random access memory
- A word is a unit of information stored to and read from memory
- Able to access randomly chosen words regardless of the order in which they are accessed
- Thought as an array of 2^m w- bit registers + some access circuits to transfer information from/into it
 - Each word has a unique address


Memory Cell

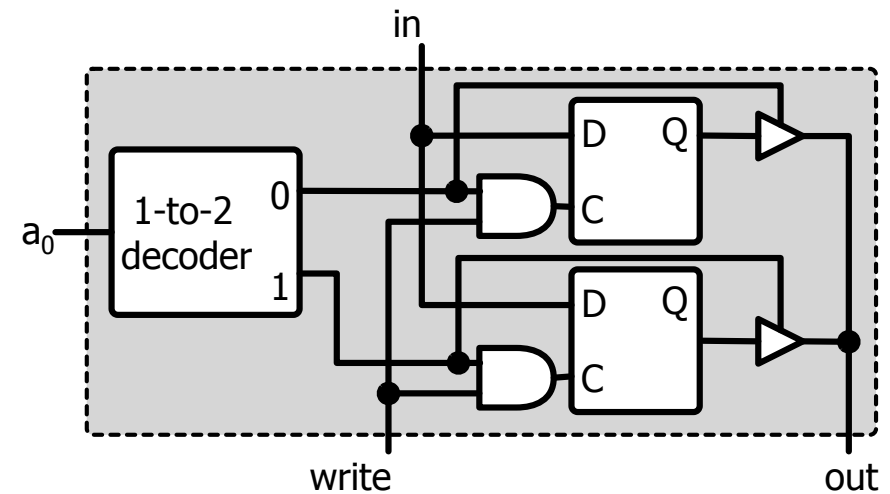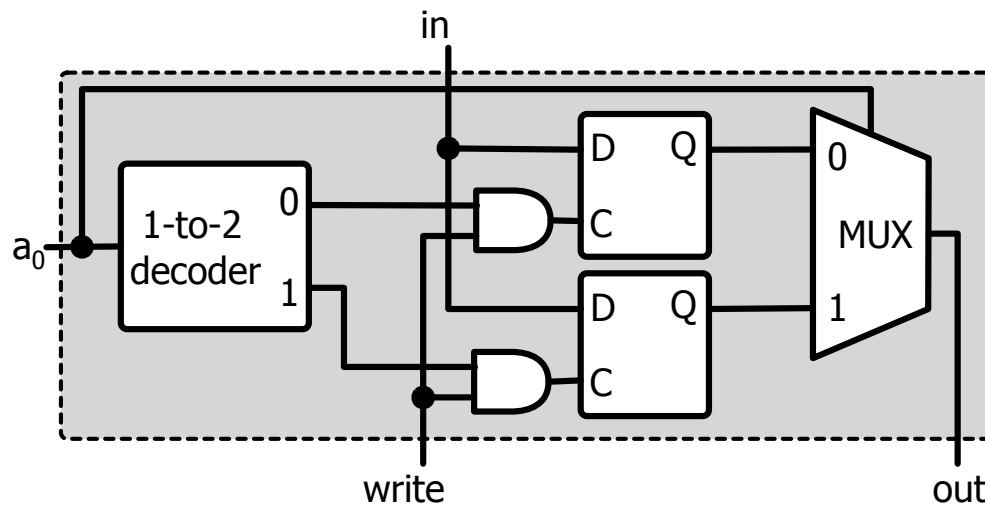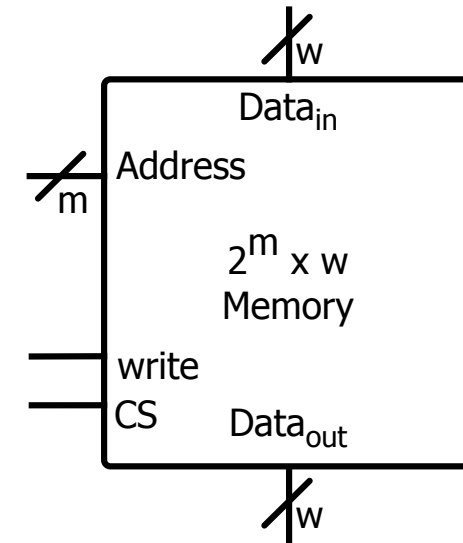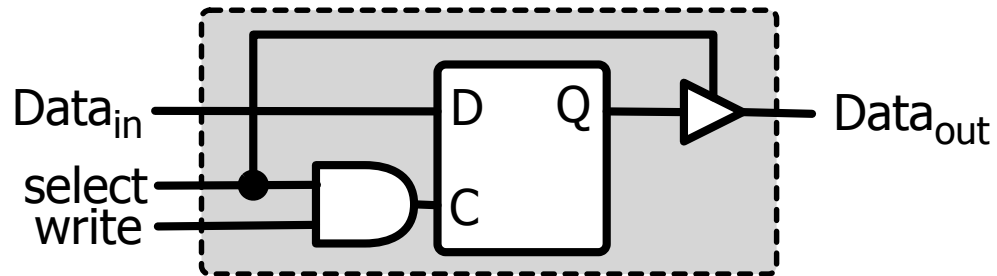

4 × 4 RAM

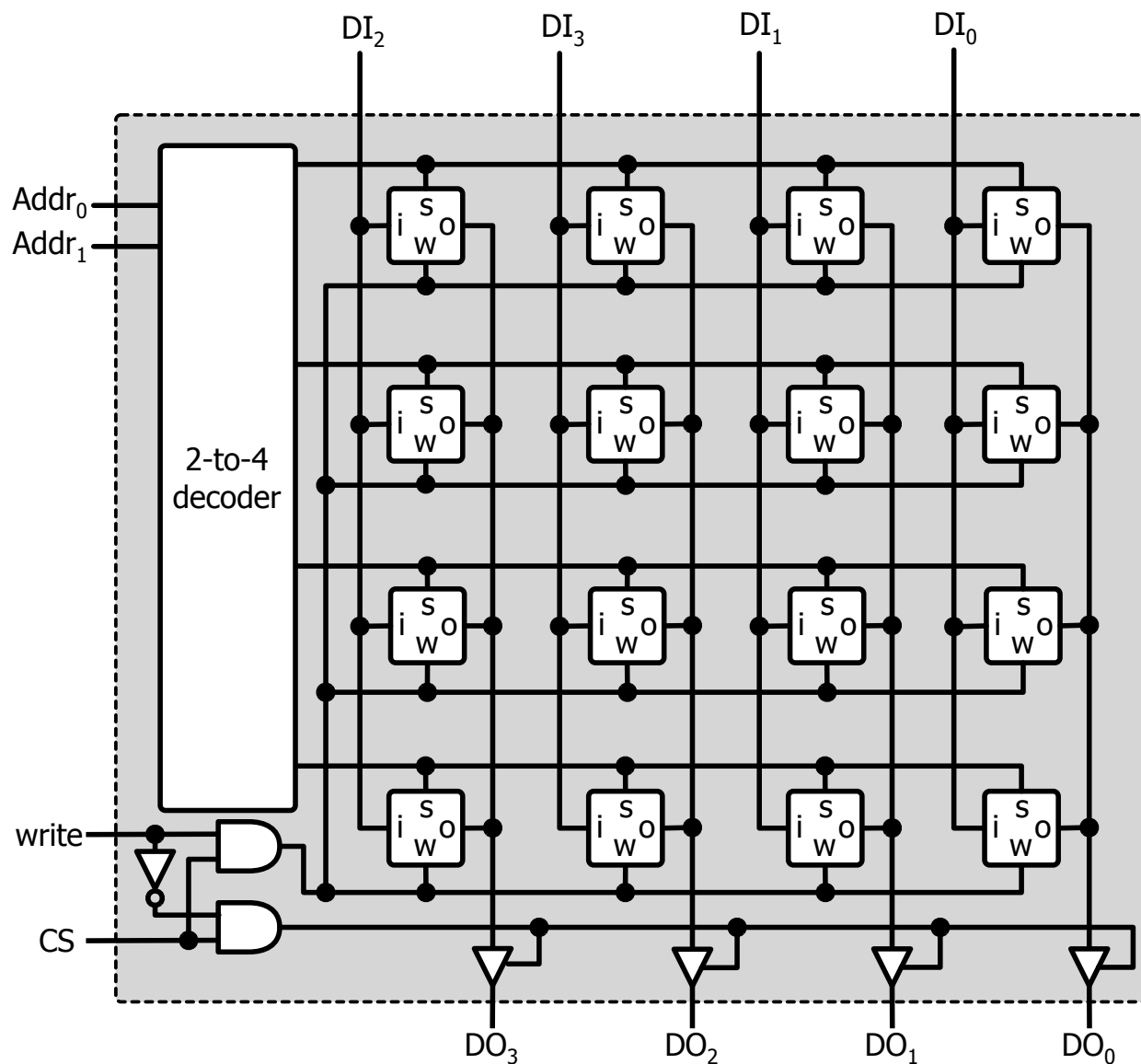

Building a RAM with Bigger Words

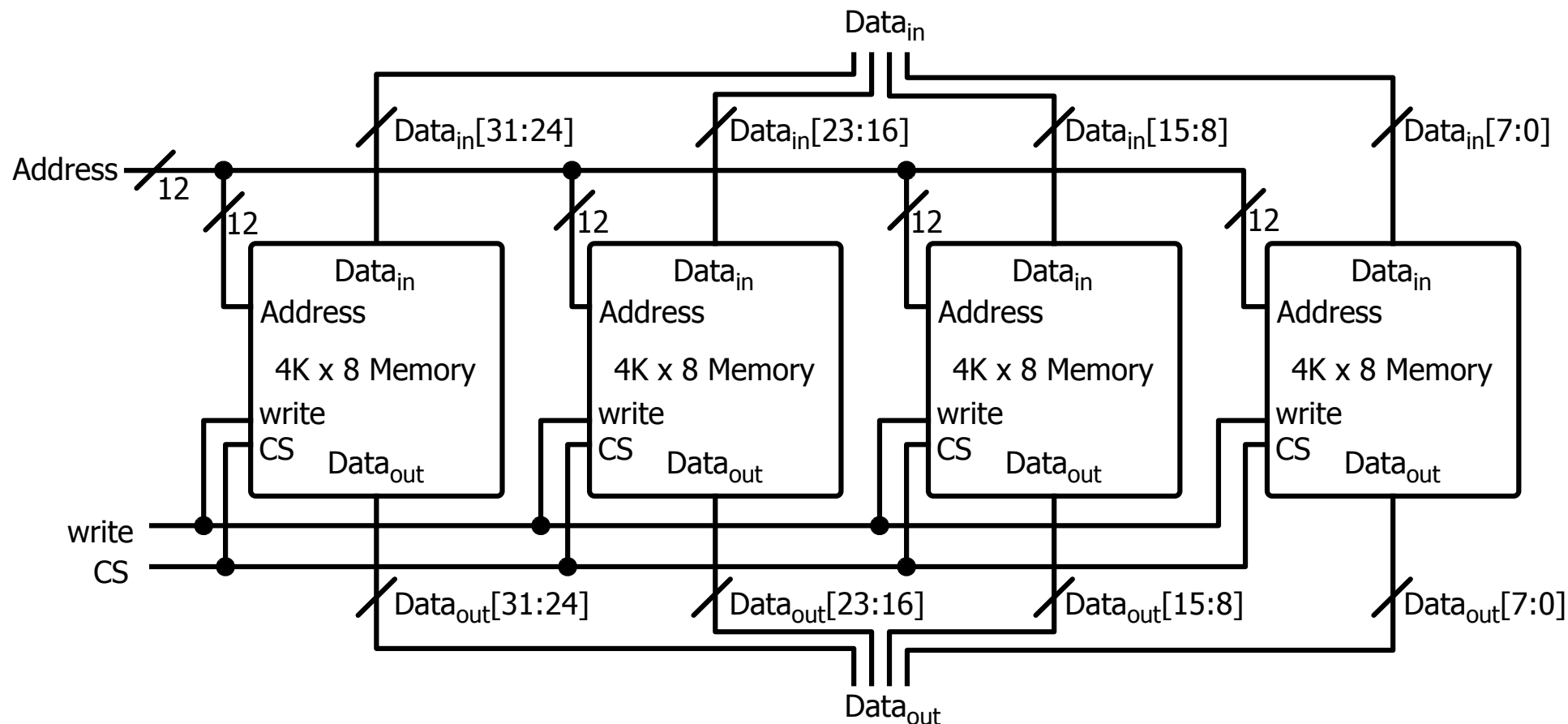

Building a RAM with More Words

