

# Digital Logic Design

4190.201

2014 Spring Semester

## 6. Case Studies in Combinational Logic Design

**Naehyuck Chang**  
**Dept. of CSE**  
**Seoul National University**  
**[naehyuck@snu.ac.kr](mailto:naehyuck@snu.ac.kr)**



# Combinational logic design case studies


- General design procedure
- Case studies
  - BCD to 7-segment display controller
  - logical function unit
  - process line controller
  - calendar subsystem
- Arithmetic circuits
  - integer representations
  - addition/subtraction
  - arithmetic/logic units

# General design procedure for combinational logic

- Step 1. Understand the problem
  - What is the circuit supposed to do?
  - Write down inputs (data, control) and outputs
  - Draw block diagram or other picture
- Step 2. Formulate the problem using a suitable design representation
  - Truth table or waveform diagram are typical
  - May require encoding of symbolic inputs and outputs
- Step 3. Choose implementation target
  - ROM, PAL, PLA
  - Mux, decoder and OR-gate
  - Discrete gates
- Step 4. Follow implementation procedure
  - K-maps for two-level, multi-level
  - Design tools and hardware description language (e.g., Verilog)
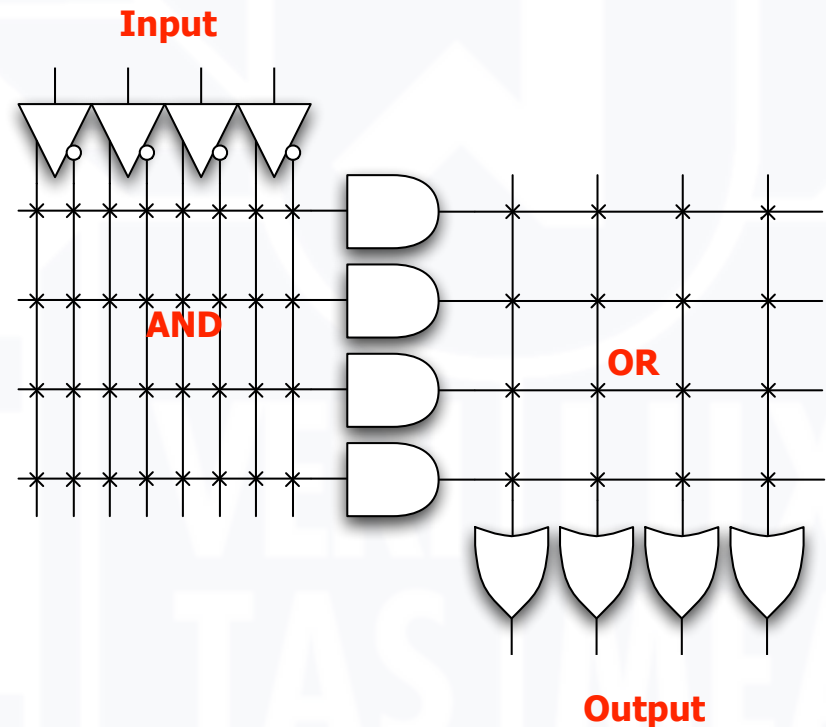
# Comparison among ROM, PLA and PAL


- Two-level implementation
  - Same speed regardless of the Boolean function as far as it can be fit
    - Fixed delay
  - Programmable logic device
- Organization
  - AND plane
  - OR plane
- Programmable AND plane
  - Generate selective product terms
- Fixed AND plane
  - Generate all the product terms
- Programmable OR plane
  - OR generated product terms selectively
- Fixed AND plane
  - OR all the generated product terms



# Comparison among ROM, PLA and PAL

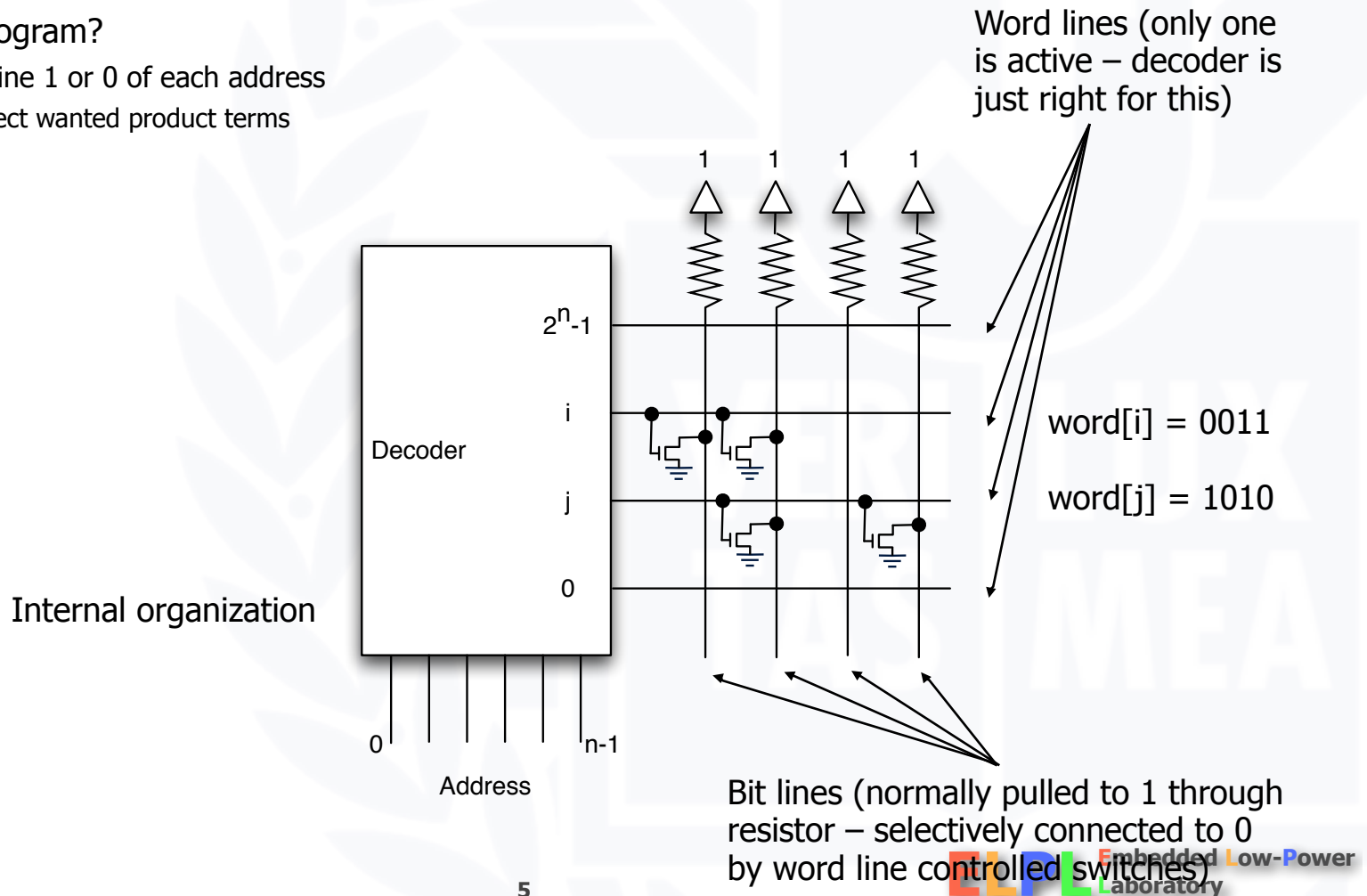
## ROM

- Fixed AND plane
- Programmable OR plane
- How to program?
  - Determine 1 or 0 of each address
  - Select wanted product terms


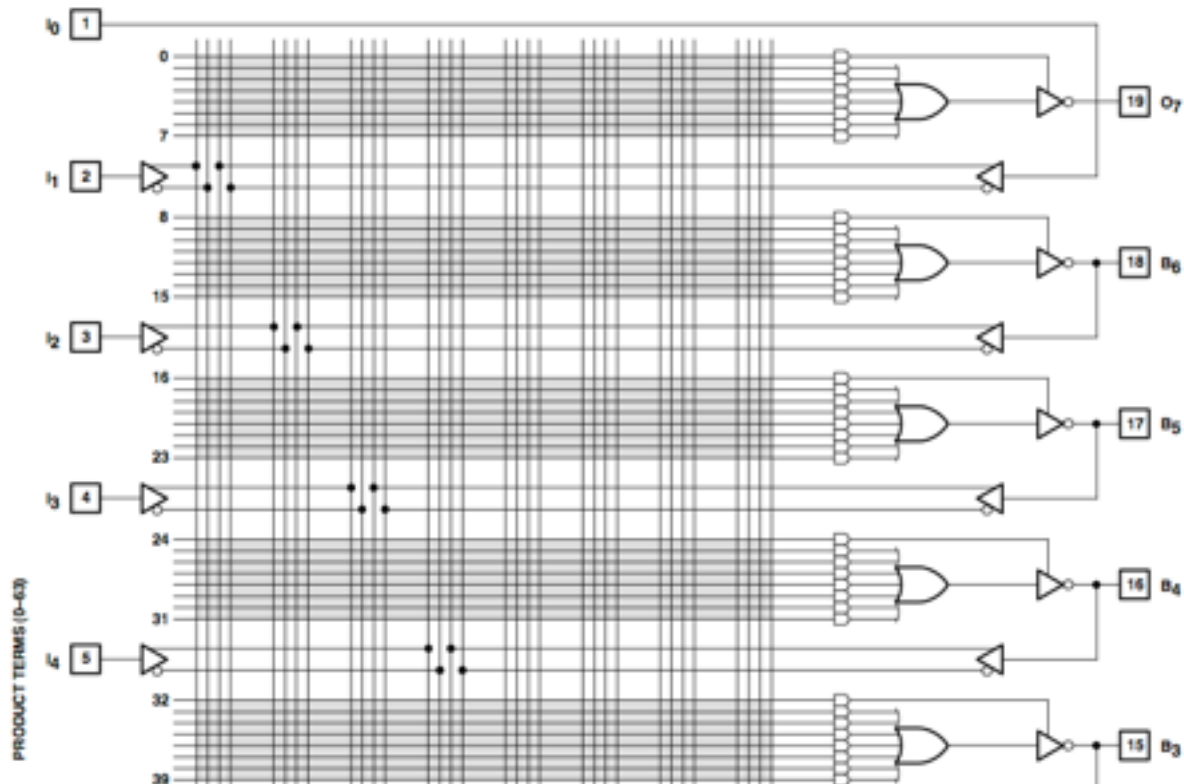
# Comparison among ROM, PLA and PAL


- PAL
  - Programmable AND plane
  - Fixed OR plane
  - How to program?
    - Generate wanted product terms



# Comparison among ROM, PLA and PAL


 
## PLA

- Programmable AND plane
- Programmable OR plane
- How to program?
  - Generate wanted product terms
  - Select wanted product terms


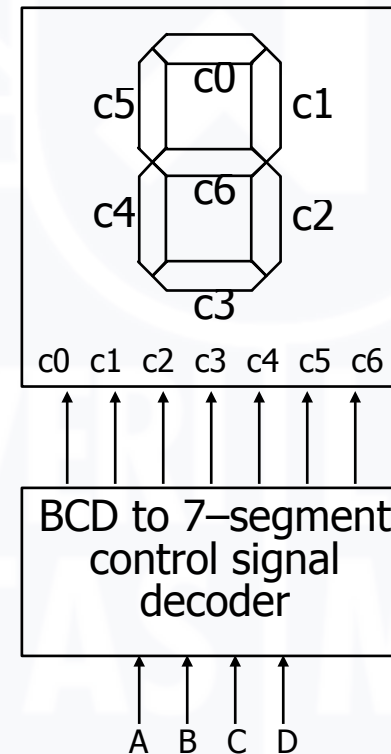 
# BCD to 7-segment display controller

- Understanding the problem
  - input is a 4 bit bcd digit (A, B, C, D)
  - output is the control signals for the display (7 outputs C0 – C6)
- Block diagram





# Formalize the problem

- Truth table
  - show don't cares
- Choose implementation target
  - if ROM, we are done
  - don't cares imply PAL/PLA may be attractive
- Follow implementation procedure
  - minimization using K-maps

A	B	C	D	C0	C1	C2	C3	C4	C5	C6
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	0	0	1	1
1	0	1	—	—	—	—	—	—	—	—
1	1	—	—	—	—	—	—	—	—	—

- 💡 15 unique product terms when minimized individually

# Implementation as minimized S-o-P (cont'd)

- Can do better
  - 9 unique product terms (instead of 15)
  - share terms among outputs
  - each output not necessarily in minimized form


		A			
C2		1	1	X	1
		1	1	X	1
C		1	1	X	X
		0	1	X	X
		B			

		A			
C2		1	1	X	1
		1	1	X	1
C		1	1	X	X
		0	1	X	X
		B			

$$\begin{aligned}
 C0 &= A + B D + C + B' D' \\
 C1 &= C' D' + C D + B' \\
 C2 &= B + C' + D \\
 C3 &= B' D' + C D' + B C' D + B' C \\
 C4 &= B' D' + C D' \\
 C5 &= A + C' D' + B D' + B C' \\
 C6 &= A + C D' + B C' + B' C
 \end{aligned}$$

$$\begin{aligned}
 C0 &= B C' D + C D + B' D' + B C D' + A \\
 C1 &= B' D + C' D' + C D + B' D' \\
 C2 &= B' D + B C' D + C' D' + C D + B C D' \\
 C3 &= B C' D + B' D + B' D' + B C D' \\
 C4 &= B' D' + B C D' \\
 C5 &= B C' D + C' D' + A + B C D' \\
 C6 &= B' C + B C' + B C D' + A
 \end{aligned}$$

# PLA implementation

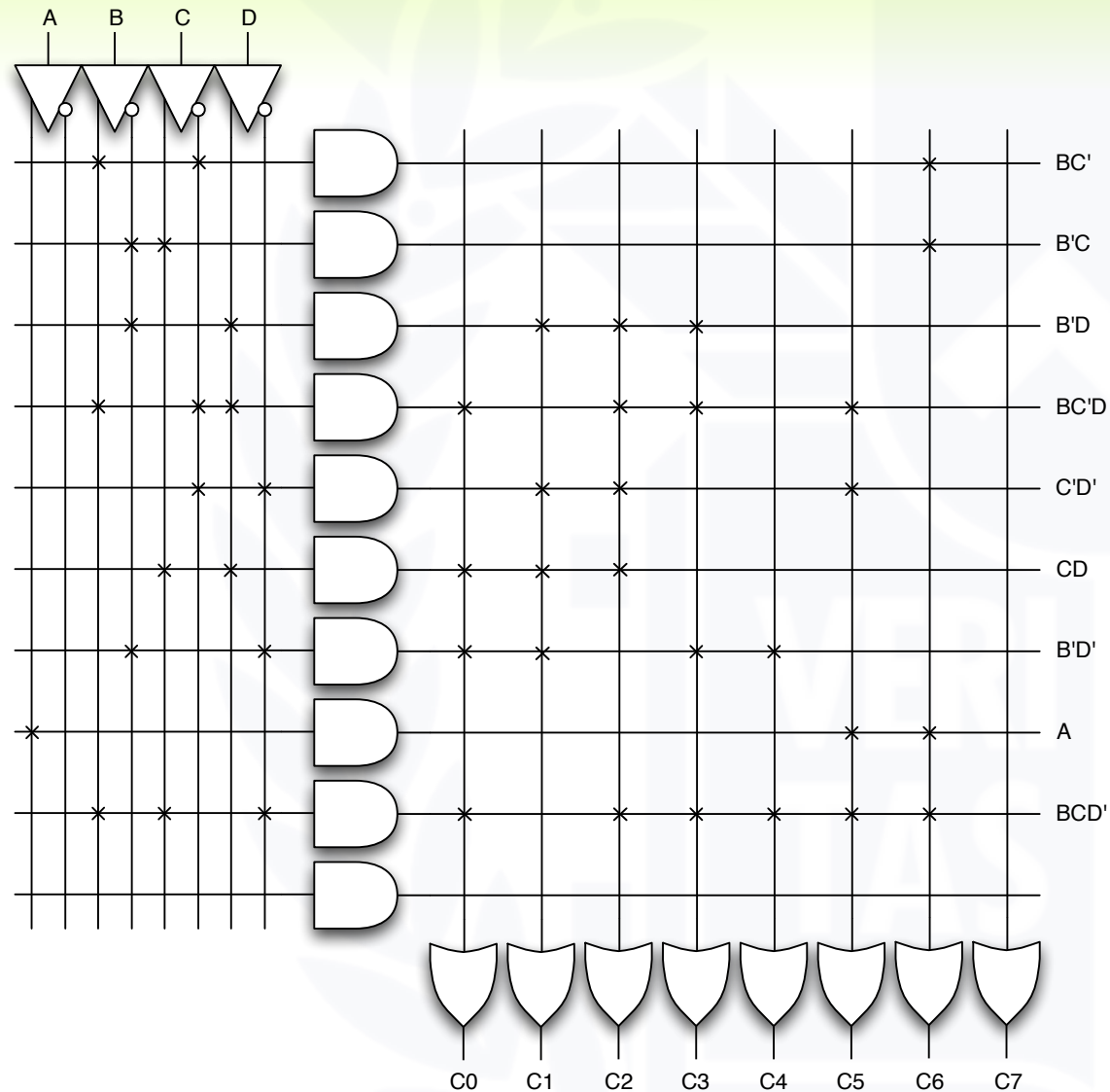

# PAL implementation vs. Discrete gate implementation

- Limit of 4 product terms per output
  - Decomposition of functions with larger number of terms
  - Do not share terms in PAL anyway (although there are some with some shared terms)

$$C2 = B + C' + D$$

$$C2 = B' D + B C' D + C' D' + C D + B C D'$$

$$C2 = B' D + B C' D + C' D' + W$$

$$W = C D + B C D'$$

need another input and another output

- Decompose into multi-level logic (hopefully with CAD support)
  - Find common sub-expressions among functions

$$C0 = C3 + A' B X' + A D Y$$

$$C1 = Y + A' C5' + C' D' C6$$

$$C2 = C5 + A' B' D + A' C D$$

$$C3 = C4 + B D C5 + A' B' X'$$

$$C4 = D' Y + A' C D'$$

$$C5 = C' C4 + A Y + A' B X$$

$$C6 = A C4 + C C5 + C4' C5 + A' B' C$$

$$X = C' + D'$$

$$Y = B' C'$$

# Logical function unit

- Multi-purpose function block
  - 3 control inputs to specify operation to perform on operands
  - 2 data inputs for operands
  - 1 output of the same bit-width as operands


C0	C1	C2	Function	Comments
0	0	0	1	always 1
0	0	1	$A + B$	logical OR
0	1	0	$(A \bullet B)'$	logical NAND
0	1	1	$A \text{ xor } B$	logical xor
1	0	0	$A \text{ xnor } B$	logical xnor
1	0	1	$A \bullet B$	logical AND
1	1	0	$(A + B)'$	logical NOR
1	1	1	0	always 0

3 control inputs: C0, C1, C2  
2 data inputs: A, B  
1 output: F

# Formalize the problem

C0	C1	C2	A	B	F
0	0	0	0	0	1
0	0	0	0	1	1
0	0	0	1	0	1
0	0	0	1	1	1
0	0	1	0	0	0
0	0	1	0	1	1
0	0	1	1	0	1
0	0	1	1	1	1
0	1	0	0	0	1
0	1	0	0	1	1
0	1	0	1	0	1
0	1	0	1	1	0
0	1	1	0	0	0
0	1	1	0	1	1
0	1	1	1	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	0	0	1	0
1	0	0	1	0	0
1	0	0	1	1	1
1	0	1	0	0	0
1	0	1	0	1	0
1	0	1	1	0	0
1	0	1	1	1	1
1	1	0	0	0	1
1	1	0	0	1	0
1	1	0	1	0	0
1	1	0	1	1	0
1	1	1	0	0	0
1	1	1	0	1	0
1	1	1	1	0	0
1	1	1	1	1	0

 
Choose implementation technology  
5-variable K-map to discrete gates  
multiplexor implementation




# 74LS247

## SN54/74LS247 • SN54/74LS248 • SN54/74LS249

SN54/74LS247  
(TOP VIEW)

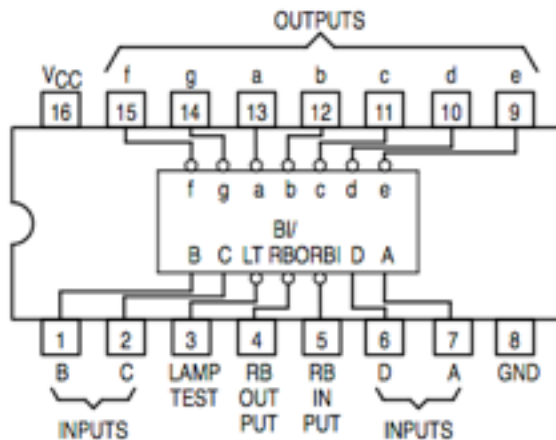

SN54/74LS248  
SN54/74LS259  
(TOP VIEW)

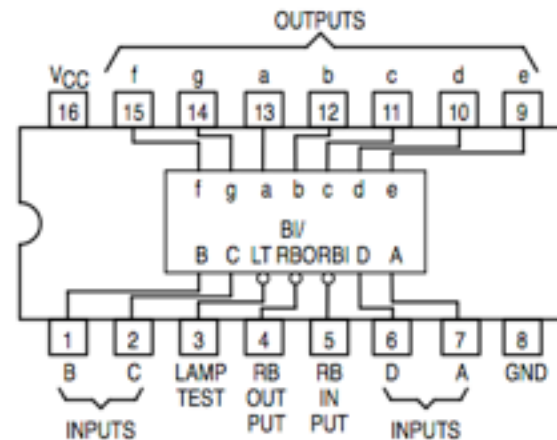




# Production line control

- Rods of varying length ( $\pm 10\%$ ) travel on conveyor belt
  - mechanical arm pushes rods within spec ( $\pm 5\%$ ) to one side
  - second arm pushes rods too long to other side
  - rods that are too short stay on belt
  - 3 light barriers (light source + photocell) as sensors
  - design combinational logic to activate the arms
- Understanding the problem
  - inputs are three sensors
  - outputs are two arm control signals
  - assume sensor reads "1" when tripped, "0" otherwise
  - call sensors A, B, C
 
# Sketch of problem

- Position of sensors
  - A to B distance = specification - 5%
  - A to C distance = specification + 5%



# Formalize the problem

- Truth table
  - Show don't cares

A	B	C	Function
0	0	0	do nothing
0	0	1	do nothing
0	1	0	do nothing
0	1	1	do nothing
1	0	0	too short
1	0	1	don't care
1	1	0	in spec
1	1	1	too long

Logic implementation now straightforward  
just use three 3-input AND gates

"too short" =  $AB'C'$   
(only first sensor tripped)

"in spec" =  $A B C'$   
(first two sensors tripped)

"too long" =  $A B C$   
(all three sensors tripped)


# Calendar subsystem

- Determine number of days in a month (to control watch display)
  - used in controlling the display of a wrist-watch LCD screen
  - inputs: month, leap year flag
  - outputs: number of days
- Use software implementation to help understand the problem

```
integer number_of_days ( month, leap_year_flag)
{
    switch (month) {
        case 1: return (31);
        case 2: if (leap_year_flag == 1)
                  then return (29)
                  else return (28);
        case 3: return (31);
        case 4: return (30);
        case 5: return (31);
        case 6: return (30);
        case 7: return (31);
        case 8: return (31);
        case 9: return (30);
        case 10: return (31);
        case 11: return (30);
        case 12: return (31);
        default: return (0);
    }
}
```
 
# Formalize the problem

- Encoding:
  - binary number for month: 4 bits
  - 4 wires for 28, 29, 30, and 31  
one-hot – only one true at any time
- Block diagram:



month	leap	28	29	30	31
0000	–	–	–	–	–
0001	–	0	0	0	1
0010	0	1	0	0	0
0010	1	0	1	0	0
0011	–	0	0	0	1
0100	–	0	0	1	0
0101	–	0	0	0	1
0110	–	0	0	1	0
0111	–	0	0	0	1
1000	–	0	0	0	1
1001	–	0	0	1	0
1010	–	0	0	0	1
1011	–	0	0	1	0
1100	–	0	0	0	1
1101	–	–	–	–	–
111–	–	–	–	–	–

# Choose implementation target and perform mapping

- Discrete gates

- $28 = m8' m4' m2 m1' \text{ leap}'$

- $29 = m8' m4' m2 m1' \text{ leap}$

- $30 = m8' m4 m1' + m8 m1$

- $31 = m8' m1 + m8 m1'$

- Can translate to S-o-P or P-o-S

month	leap	28	29	30	31
0000	—	—	—	—	—
0001	—	0	0	0	1
0010	0	1	0	0	0
0010	1	0	1	0	0
0011	—	0	0	0	1
0100	—	0	0	1	0
0101	—	0	0	0	1
0110	—	0	0	1	0
0111	—	0	0	0	1
1000	—	0	0	0	1
1001	—	0	0	1	0
1010	—	0	0	0	1
1011	—	0	0	1	0
1100	—	0	0	0	1
1101	—	—	—	—	—
111—	—	—	—	—	—

# Leap year flag

- Determine value of leap year flag given the year
  - For years after 1582 (Gregorian calendar reformation),
  - leap years are all the years divisible by 4,
  - except that years divisible by 100 are not leap years,
  - but years divisible by 400 are leap years.
- Encoding the year:
  - binary – easy for divisible by 4,  
but difficult for 100 and 400 (not powers of 2)
  - BCD – easy for 100,  
but more difficult for 4, what about 400?
- Parts:
  - construct a circuit that determines if the year is divisible by 4
  - construct a circuit that determines if the year is divisible by 100
  - construct a circuit that determines if the year is divisible by 400
  - combine the results of the previous three steps to yield the leap year flag

# Activity: divisible-by-4 circuit

- BCD coded year
  - YM8 YM4 YM2 YM1 – YH8 YH4 YH2 YH1 – YT8 YT4 YT2 YT1 – YO8 YO4 YO2 YO1
- Only need to look at low-order two digits of the year  
all years ending in 00, 04, 08, 12, 16, 20, etc. are divisible by 4
  - if tens digit is even, then divisible by 4 if ones digit is 0, 4, or 8
  - if tens digit is odd, then divisible by 4 if the ones digit is 2 or 6.
- Translates into the following Boolean expression  
(where YT1 is the year's tens digit low-order bit,  
YO8 is the high-order bit of year's ones digit, etc.):
  - $YT1' (YO8' YO4' YO2' YO1' + YO8' YO4 YO2' YO1' + YO8 YO4' YO2' YO1' )$   
 $+ YT1 (YO8' YO4' YO2 YO1' + YO8' YO4 YO2 YO1' )$
- Digits with values of 10 to 15 will never occur, simplify further to yield:
  - $YT1' YO2' YO1' + YT1 YO2 YO1'$



# Divisible-by-100 and divisible-by-400 circuits


- Divisible-by-100 just requires checking that all bits of two low-order digits are all 0:
  - $YT8' YT4' YT2' YT1' \bullet YO8' YO4' YO2' YO1'$
- Divisible-by-400 combines the divisible-by-4 (applied to the thousands and hundreds digits) and divisible-by-100 circuits
  - $(YM1' YH2' YH1' + YM1 YH2 YH1') \bullet (YT8' YT4' YT2' YT1' \bullet YO8' YO4' YO2' YO1')$

# Combining to determine leap year flag

- Label results of previous three circuits: D4, D100, and D400

$$\begin{aligned}\text{leap\_year\_flag} &= D4 (D100 \bullet D400')' \\ &= D4 \bullet D100' + D4 \bullet D400 \\ &= D4 \bullet D100' + D400\end{aligned}$$

# Implementation of leap year flag

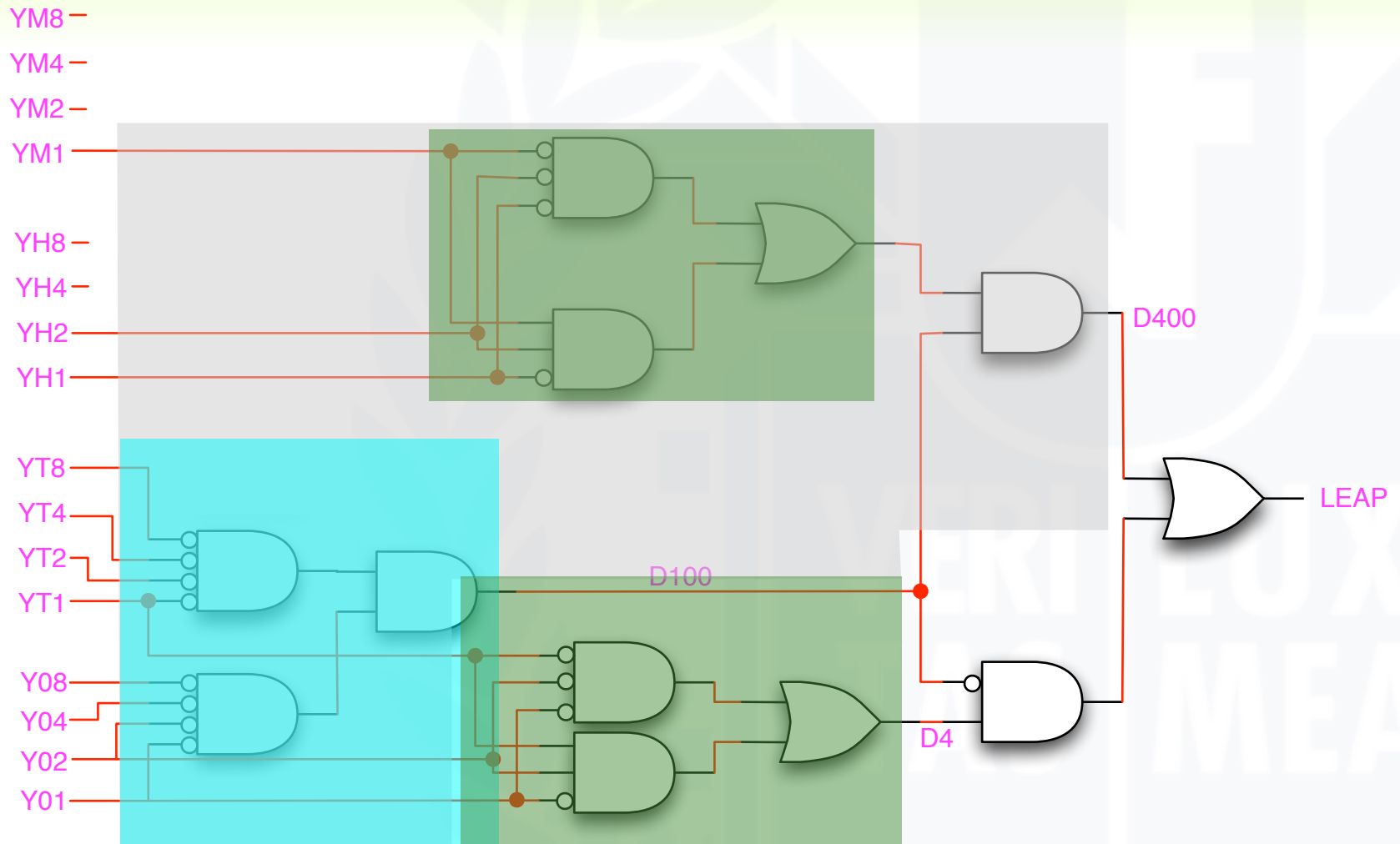

# Arithmetic circuits

- Excellent examples of combinational logic design
- Time vs. space trade-offs
  - doing things fast may require more logic and thus more space
  - example: carry lookahead logic
- Arithmetic and logic units
  - general-purpose building blocks
  - critical components of processor datapaths
  - used within most computer instructions

# Number systems


- Representation of positive numbers is the same in most systems
- Major differences are in how negative numbers are represented
- Representation of negative numbers come in three major schemes
  - sign and magnitude
  - 1s complement
  - 2s complement
- Assumptions
  - we'll assume a 4 bit machine word
  - 16 different values can be represented
  - roughly half are positive, half are negative

# Sign and magnitude

- One bit dedicate to sign (positive or negative)
  - sign: 0 = positive (or zero), 1 = negative
- Rest represent the absolute value or magnitude
  - three low order bits: 0 (000) thru 7 (111)
- Range for n bits
  - $\pm 2^{n-1} - 1$  (two representations for 0)
- Cumbersome addition/subtraction
  - must compare magnitudes to determine sign of result

0 100 = + 4

1 100 = - 4

 

# 1s complement

- If N is a positive number, then the negative of N (its 1s complement or N' ) is  $N' = (2^n - 1) - N$
- Example: 1s complement of 7

$$\begin{array}{rcl} 2^4 & = & 10000 \\ 1 & = & 00001 \\ \hline 2^4 - 1 & = & 1111 \\ 7 & = & 0111 \\ \hline & & 1000 \end{array} = -7 \text{ in 1s complement form}$$


- Shortcut: simply compute bit-wise complement ( 0111 -> 1000 )

# 1s complement (cont'd)

- Subtraction implemented by 1s complement and then addition
- Two representations of 0
  - causes some complexities in addition
- High-order bit can act as sign bit

0 100 = + 4

1 011 = - 4

 




# 2s complement

- 1s complement with negative numbers shifted one position clockwise
  - only one representation for 0
  - one more negative number than positive numbers
  - high-order bit can act as sign bit

0 100 = + 4

1 100 = - 4

 

# 2s complement (cont'd)

- If  $N$  is a positive number, then the negative of  $N$  (its 2s complement or  $N^*$ ) is  $N^* = 2^n - N$

- Example: 2s complement of 7

$$\begin{array}{rcl} & 4 & \\ 2^4 & = & 10000 \\ \text{subtract } 7 & = & \underline{0111} \\ & & 1001 = \text{repr. of } -7 \end{array}$$

- Example: 2s complement of  $-7$

$$\begin{array}{rcl} & 4 & \\ 2^4 & = & 10000 \\ \text{subtract } -7 & = & \underline{1001} \\ & & 0111 = \text{repr. of } 7 \end{array}$$

- Shortcut: 2s complement = bit-wise complement + 1

- 0111  $\rightarrow$  1000 + 1  $\rightarrow$  1001 (representation of  $-7$ )
- 1001  $\rightarrow$  0110 + 1  $\rightarrow$  0111 (representation of 7)

# 2s complement addition and subtraction

- Simple addition and subtraction
  - simple scheme makes 2s complement the virtually unanimous choice for integer number systems in computers

$$\begin{array}{r} 4 \quad 0100 \\ + 3 \quad 0011 \\ \hline 7 \quad 0111 \end{array}$$

$$\begin{array}{r} -4 \quad 1100 \\ + (-3) \quad 1101 \\ \hline -7 \quad 11001 \end{array}$$

$$\begin{array}{r} 4 \quad 0100 \\ - 3 \quad 1101 \\ \hline 1 \quad 10001 \end{array}$$

$$\begin{array}{r} -4 \quad 1100 \\ + 3 \quad 0011 \\ \hline -1 \quad 1111 \end{array}$$

# Why can the carry-out be ignored?

- Can't ignore it completely
  - Needed to check for overflow (see next two slides)
- When there is no overflow, carry-out may be true but can be ignored

–  $M + N$  when  $N > M$ :

$$M^* + N = (2^n - M) + N = 2^n + (N - M)$$

ignoring carry-out is just like subtracting  $2^n$


–  $M + -N$  where  $N + M \leq 2^n - 1$

$$(-M) + (-N) = M^* + N^* = (2^n - M) + (2^n - N) = 2^n - (M + N) + 2^n$$


ignoring the carry, it is just the 2s complement representation for  $-(M + N)$
 
# Overflow in 2s complement addition/subtraction

- Overflow conditions
  - add two positive numbers to get a negative number
  - add two negative numbers to get a positive number



$$5 + 3 = -8$$

 

$$-7 - 2 = +7$$

# Overflow conditions

- Overflow when carry into sign bit position is not equal to carry-out

$$\begin{array}{r}
 5 \\
 - 3 \\
 \hline
 -8
 \end{array}$$

overflow

$$\begin{array}{r}
 0111 \\
 0101 \\
 \hline
 0011 \\
 1000
 \end{array}$$

$$\begin{array}{r}
 -7 \\
 -2 \\
 \hline
 7
 \end{array}$$

overflow

$$\begin{array}{r}
 1000 \\
 1001 \\
 \hline
 1110 \\
 10111
 \end{array}$$

$$\begin{array}{r}
 5 \\
 - 2 \\
 \hline
 7
 \end{array}$$

no overflow

$$\begin{array}{r}
 0000 \\
 0101 \\
 \hline
 0010 \\
 0111
 \end{array}$$

$$\begin{array}{r}
 -3 \\
 -5 \\
 \hline
 -8
 \end{array}$$

no overflow

$$\begin{array}{r}
 1111 \\
 1101 \\
 \hline
 1011 \\
 11000
 \end{array}$$

# Circuits for binary addition

- Half adder (add 2 1-bit numbers)
  - $\text{Sum} = A_i' B_i + A_i B_i' = A_i \text{ xor } B_i$
  - $\text{Cout} = A_i B_i$
- Full adder (carry-in to cascade for multi-bit adders)
  - $\text{Sum} = C_i \text{ xor } A \text{ xor } B$
  - $\text{Cout} = B C_i + A C_i + A B = C_i (A + B) + A B$


Ai	Bi	Sum	Cout
0	0	0	0
0	1	1	0
1	0	1	0
1	1	1	1

Ai	Bi	Cin	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

# Full adder implementations

- Standard approach


- 6 gates
- 2 XORs, 2 ANDs, 2 ORs

 

- Alternative implementation

- 5 gates
- Half adder is an XOR gate and AND gate
- 2 XORs, 2 ANDs, 1 OR

 
$$\text{Cout} = A B + \text{Cin} (A \text{ xor } B) = A B + B \text{Cin} + A \text{Cin}$$






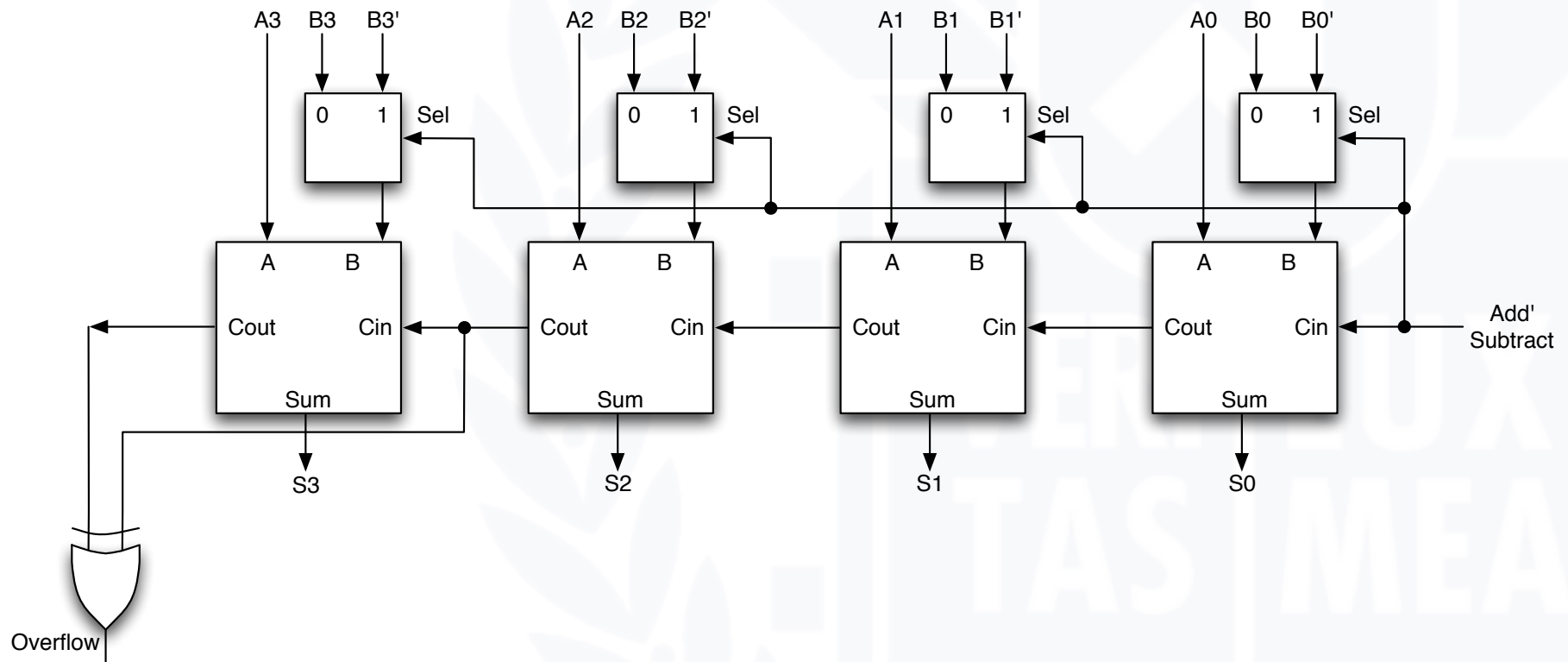
# Adder/subtractor

- Use an adder to do subtraction thanks to 2s complement representation
  - $A - B = A + (-B) = A + B' + 1$
  - Control signal selects B or 2s complement of B



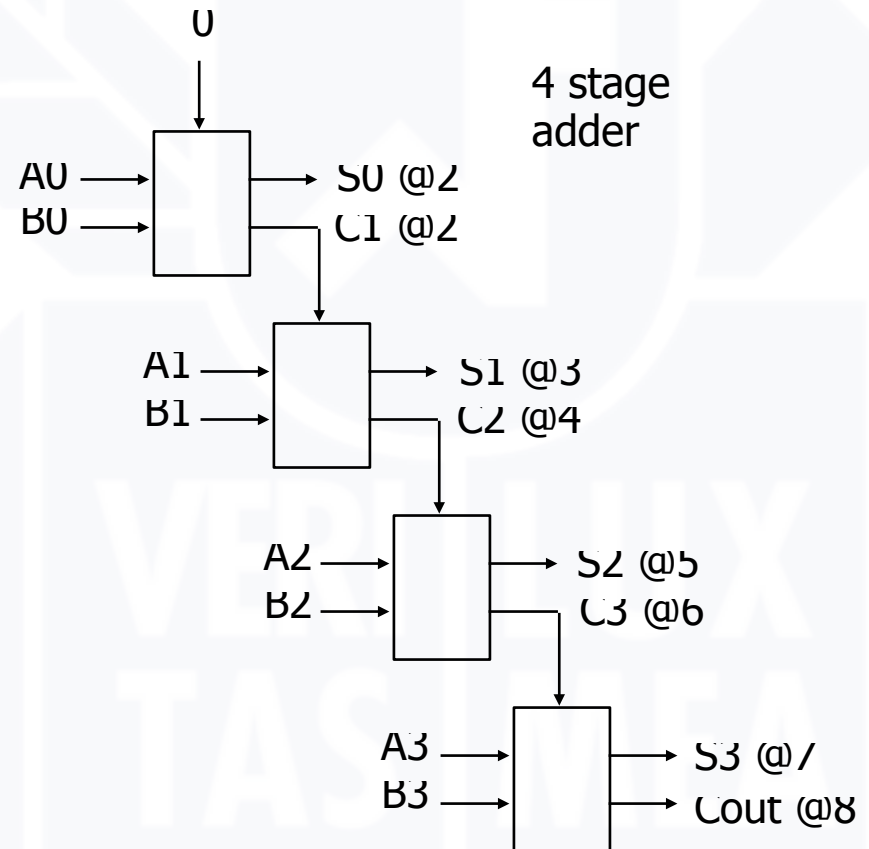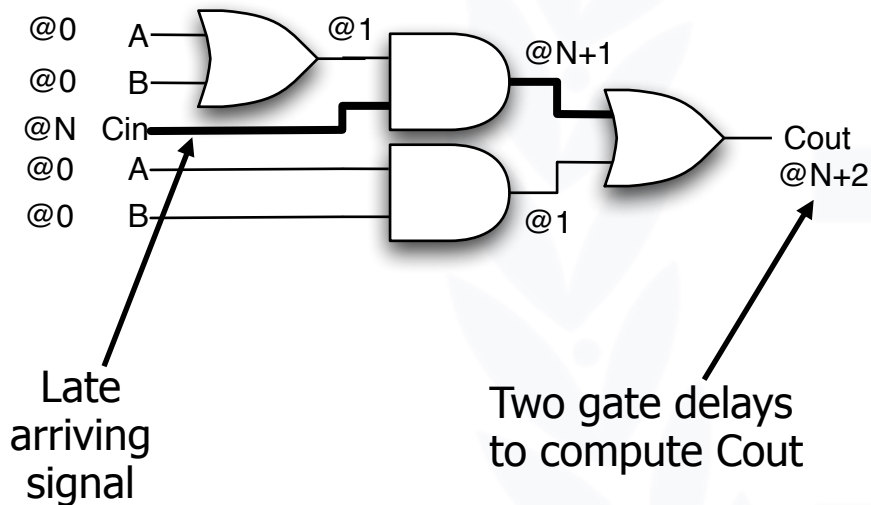
# Ripple-carry adders

- Critical delay
  - The propagation of carry from low to high order stages


 
# Ripple-carry adders (cont'd)

- Critical delay
  - the propagation of carry from low to high order stages
  - 1111 + 0001 is the worst case addition
  - carry must propagate through all bits



# Carry-lookahead logic






- Carry generate:  $G_i = A_i B_i$ 
  - Must generate carry when  $A = B = 1$
- Carry propagate:  $P_i = A_i \text{ xor } B_i$ 
  - Carry-in will equal carry-out here
- Sum and Cout can be re-expressed in terms of generate/propagate:
  - $S_i = A_i \text{ xor } B_i \text{ xor } C_i$   
 $= P_i \text{ xor } C_i$
  - $C_{i+1} = A_i B_i + A_i C_i + B_i C_i$   
 $= A_i B_i + C_i (A_i + B_i)$   
 $= A_i B_i + C_i (A_i \text{ xor } B_i)$   
 $= G_i + C_i P_i$

# Carry-lookahead logic (cont'd)

- Re-express the carry logic as follows:
  - $C_1 = G_0 + P_0 C_0$
  - $C_2 = G_1 + P_1 C_1 = G_1 + P_1 G_0 + P_1 P_0 C_0$
  - $C_3 = G_2 + P_2 C_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$
  - $C_4 = G_3 + P_3 C_3 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0$
- Each of the carry equations can be implemented with two-level logic
  - All inputs are now directly derived from data inputs and not from intermediate carries
  - This allows computation of all sum outputs to proceed in parallel
     
# Carry-lookahead implementation



- Adder with propagate and generate outputs



Increasingly complex  
logic for carries

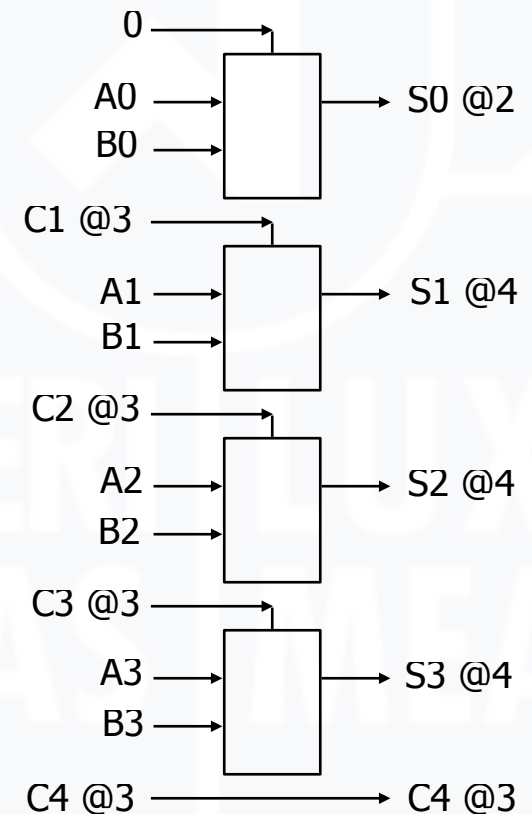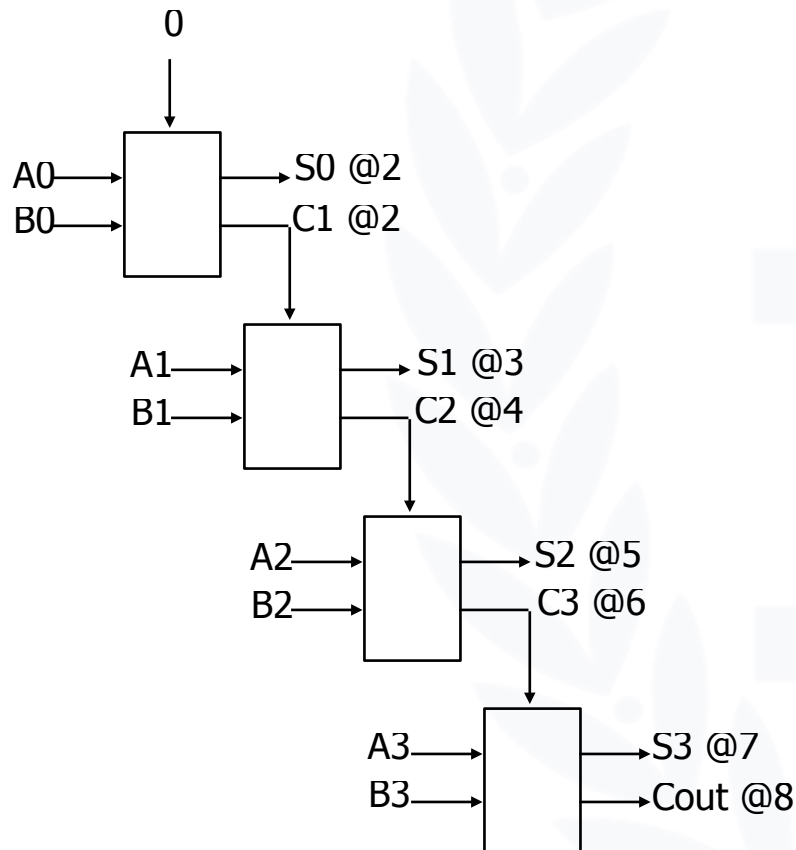
# Carry-lookahead implementation (cont'd)

- Carry-lookahead logic generates individual carries
  - sums computed much more quickly in parallel
  - however, cost of carry logic increases with more stages


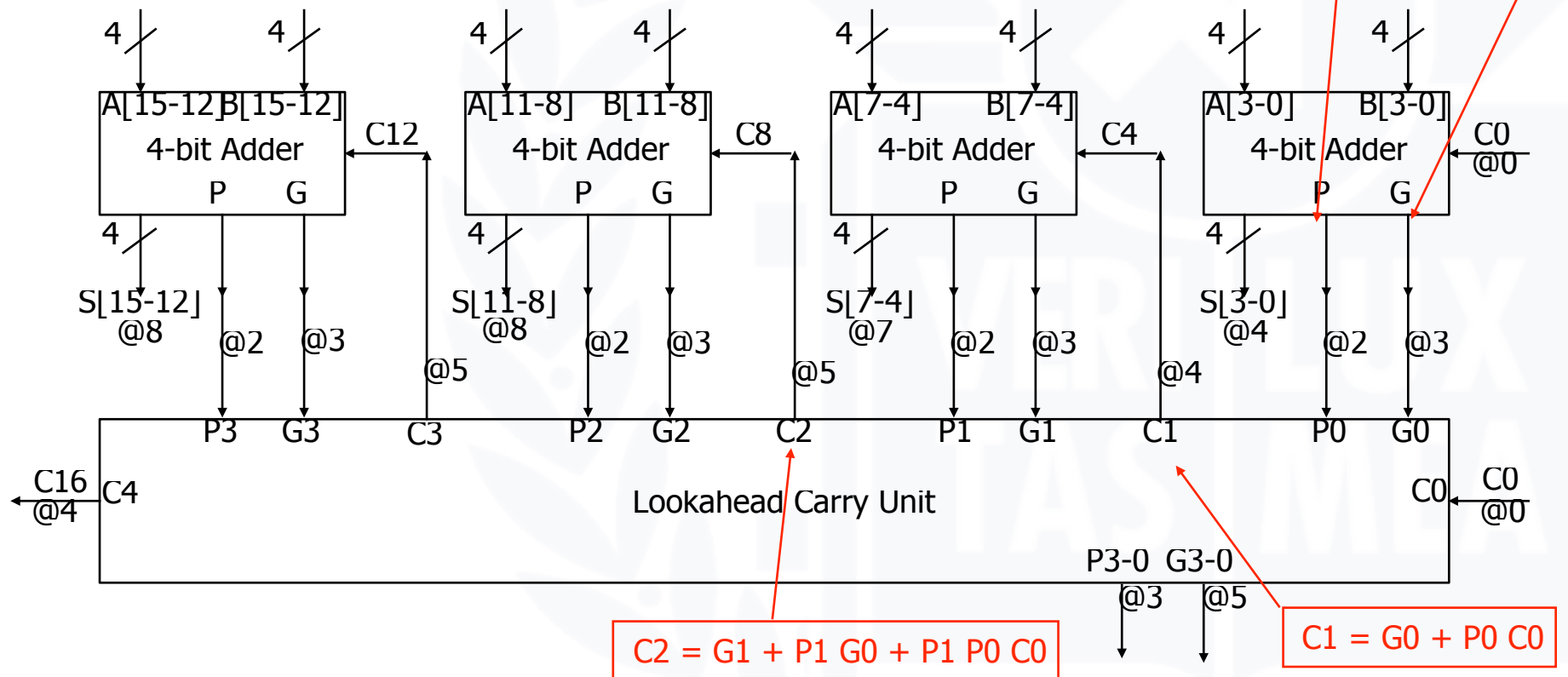
# Carry-lookahead adder with cascaded carry-lookahead logic


- Carry-lookahead adder
  - 4 four-bit adders with internal carry lookahead
  - second level carry lookahead unit extends lookahead to 16 bits




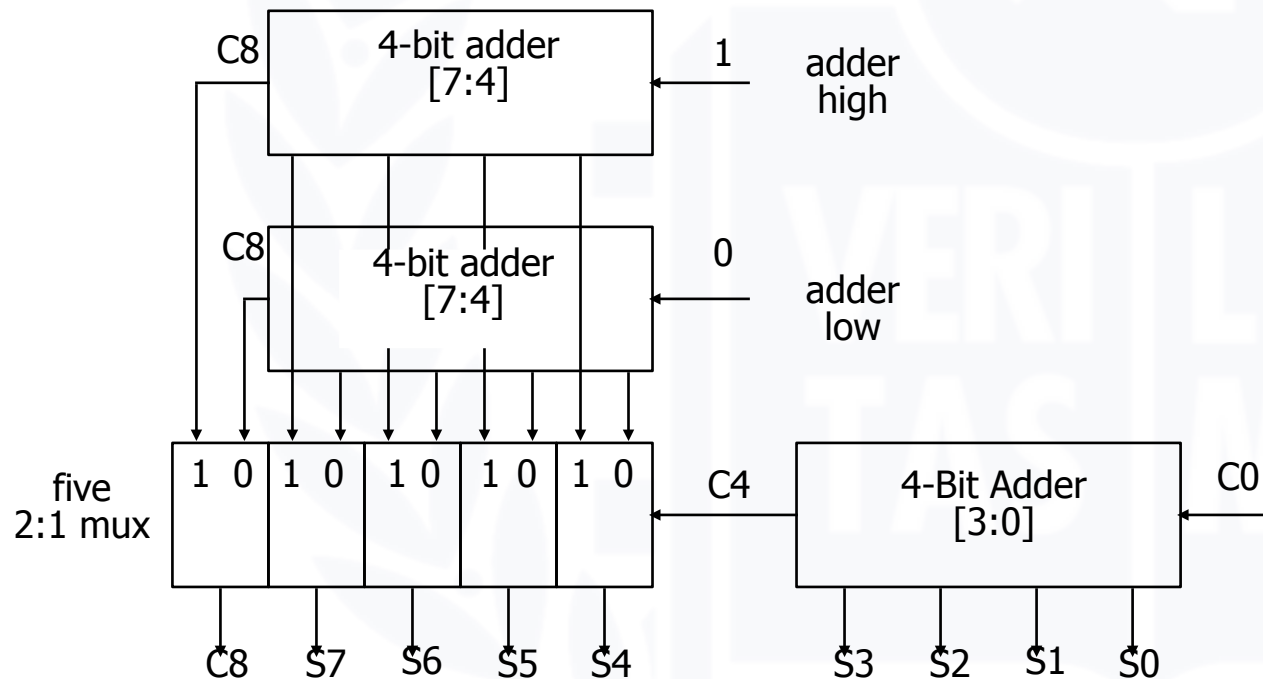
# Carry-select adder

- Redundant hardware to make carry calculation go faster
  - compute two high-order sums in parallel while waiting for carry-in
  - one assuming carry-in is 0 and another assuming carry-in is 1
  - select correct result once carry-in is finally computed



# Arithmetic logic unit design specification

**M = 0, logical bitwise operations**

<b>S1</b>	<b>S0</b>	<b>Function</b>	<b>Comment</b>
<b>0</b>	<b>0</b>	<b><math>F_i = A_i</math></b>	<b>input <math>A_i</math> transferred to output</b>
<b>0</b>	<b>1</b>	<b><math>F_i = \text{not } A_i</math></b>	<b>complement of <math>A_i</math> transferred to output</b>
<b>1</b>	<b>0</b>	<b><math>F_i = A_i \text{ xor } B_i</math></b>	<b>compute XOR of <math>A_i, B_i</math></b>
<b>1</b>	<b>1</b>	<b><math>F_i = A_i \text{ xnor } B_i</math></b>	<b>compute XNOR of <math>A_i, B_i</math></b>

**M = 1, C0 = 0, arithmetic operations**

<b>0</b>	<b>0</b>	<b><math>F = A</math></b>	<b>input A passed to output</b>
<b>0</b>	<b>1</b>	<b><math>F = \text{not } A</math></b>	<b>complement of A passed to output</b>
<b>1</b>	<b>0</b>	<b><math>F = A \text{ plus } B</math></b>	<b>sum of A and B</b>
<b>1</b>	<b>1</b>	<b><math>F = (\text{not } A) \text{ plus } B</math></b>	<b>sum of B and complement of A</b>

**M = 1, C0 = 1, arithmetic operations**

<b>0</b>	<b>0</b>	<b><math>F = A \text{ plus } 1</math></b>	<b>increment A</b>
<b>0</b>	<b>1</b>	<b><math>F = (\text{not } A) \text{ plus } 1</math></b>	<b>twos complement of A</b>
<b>1</b>	<b>0</b>	<b><math>F = A \text{ plus } B \text{ plus } 1</math></b>	<b>increment sum of A and B</b>
<b>1</b>	<b>1</b>	<b><math>F = (\text{not } A) \text{ plus } B \text{ plus } 1</math></b>	<b>B minus A</b>

**logical and arithmetic operations**  
**not all operations appear useful, but "fall out" of internal logic**


# Arithmetic logic unit design (cont'd)

## Sample ALU – truth table

M	S1	S0	Ci	Ai	Bi	Fi	Ci+1
0	0	0	X	0	X	0	X
			X	1	X	1	X
		1	X	0	X	1	X
			X	1	X	0	X
		0	X	0	0	0	X
			X	0	1	1	X
	1	0	X	1	0	1	X
			X	1	1	0	X
		1	X	0	0	1	X
			X	0	1	0	X
		1	X	1	0	0	X
			X	1	1	1	X
1	0	0	0	0	X	0	X
			0	1	X	1	X
		1	0	0	X	1	X
			0	1	X	0	X
		0	0	0	0	0	0
			0	0	1	1	0
	1	0	0	1	0	1	0
			0	1	1	0	1
		1	0	0	0	1	0
			0	0	1	0	1
		1	0	1	0	0	0
			0	1	1	1	0
1	0	0	1	0	X	1	0
			1	1	X	0	1
		1	1	0	X	1	0
			1	1	X	0	1
		0	1	0	0	1	0
			1	0	1	0	1
	1	0	1	1	0	0	1
			1	1	1	1	1
		1	1	0	0	1	1
			1	0	1	0	1
		1	1	1	0	1	0
			1	1	1	1	0
51			1	1	1	0	1
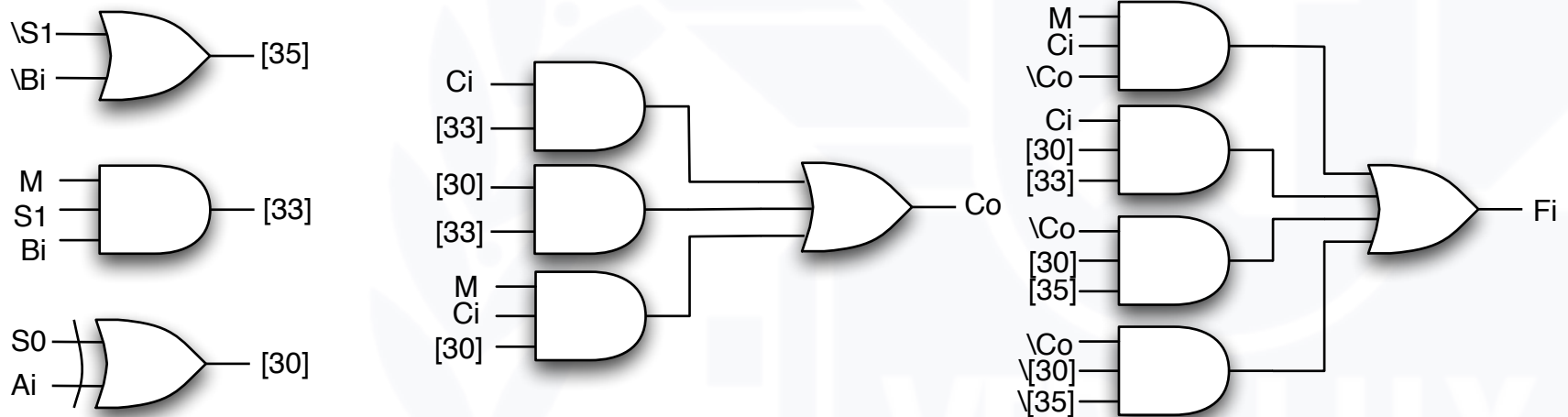
# Arithmetic logic unit design (cont'd)


- Sample ALU – multi-level discrete gate logic implementation



12 gates
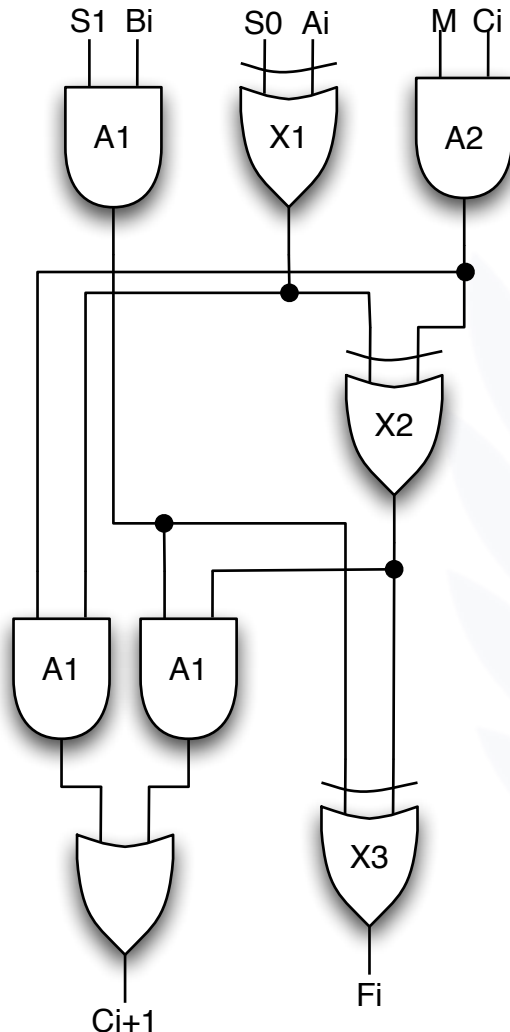
## Arithmetic logic unit design (cont'd)

Sample ALU – clever multi-level implementation



## First-level gates

use  $S_0$  to complement  $A_i$

$S0 = 0$  causes gate X1 to pass  $A_i$

$S0 = 1$  causes gate X1 to pass  $A_i'$

use S1 to block Bi

S1 = 0 causes gate A1 to make Bi go forward as 0  
(don't want Bi for operations with just A)

S1 = 1 causes gate A1 to pass Bi

use  $M$  to block  $C_i$

M = 0 causes gate A2 to make Ci go forward as 0 (don't want Ci for logical operations)

M = 1 causes gate A2 to pass Ci

## Other gates

for  $M=0$  (logical operations,  $C_i$  is ignored)

$$F_i = S1 \oplus B_i \text{ xor } (S0 \text{ xor } A_i)$$
$$= S1'S0' ( A_i ) + S1'S0 ( A_i' ) +$$
$$S_1 S_0' (A_i' B_i' + A_i' \bar{B}_i) + S_1 S_0 (A_i' B_i' + A_i B_i)$$

for  $M=1$  (arithmetic operations)

$$F_i = S_1 \oplus B_i \oplus ((S_0 \oplus A_i) \oplus C_i) =$$
$$C_{i+1} = C_i (S_0 \text{ xor } A_i) + S_1 B_i ( (S_0 \text{ xor } A_i) \text{ xor } C_i ) =$$

just a full adder with inputs  $S_0 \oplus A_i$ ,  $S_1 B_i$ , and  $C_i$

# Summary for examples of combinational logic

- Combinational logic design process
  - formalize problem: encodings, truth-table, equations
  - choose implementation technology (ROM, PAL, PLA, discrete gates)
  - implement by following the design procedure for that technology
- Binary number representation
  - positive numbers the same
  - difference is in how negative numbers are represented
  - 2s complement easiest to handle: one representation for zero, slightly complicated complementation, simple addition
- Circuits for binary addition
  - basic half-adder and full-adder
  - carry lookahead logic
  - carry-select
- ALU Design
  - specification, implementation