

Digital Logic Design

4190.201

2014 Spring Semester

10. Sequential Logic Technology

Naehyuck Chang
Dept. of CSE
Seoul National University
naehyuck@snu.ac.kr




Sequential logic implementation

- Implementation
 - Random logic gates and FFs
 - Programmable logic devices (PAL with FFs)
- Design procedure
 - State diagrams
 - Design
 - Verification (branch condition)
 - Reduction (implicant chart or raw matching)
 - State transition table
 - State assignment
 - Tight encoding for random logic
 - One-hot for FPGA
 - Output-based for PLD
 - Next state functions
 - Input synchronization

Median filter FSM

 - Remove single 0s between two 1s (output = NS3)



I	PS1	PS2	PS3	NS1	NS2	NS3
0	0	0	0	0	0	0
0	0	0	1	0	0	0
0	0	1	0	0	0	1
0	0	1	1	0	0	1
0	1	0	0	0	1	0
0	1	0	1	X	X	X
0	1	1	0	0	1	1
0	1	1	1	0	1	1
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	1	1	1
1	0	1	1	1	1	1
1	1	0	0	1	1	0
1	1	0	1	X	X	X
1	1	1	0	1	1	1
1	1	1	1	1	1	1

Median filter FSM (cont'd)

- Realized using the standard procedure and individual FFs and gates

I	PS1	PS2	PS3	NS1	NS2	NS3
0	0	0	0	0	0	0
0	0	0	1	0	0	0
0	0	1	0	0	0	1
0	0	1	1	0	0	1
0	1	0	0	0	1	0
0	1	0	1	X	X	X
0	1	1	0	0	1	1
0	1	1	1	0	1	1
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	1	1	1
1	0	1	1	1	1	1
1	1	0	0	1	1	0
1	1	0	1	X	X	X
1	1	1	0	1	1	1
1	1	1	1	1	1	1

NS1 = Reset' (I)



NS2 = Reset' (PS1 + PS2 I)

NS3 = Reset' PS2

O = PS3


Median filter FSM (cont'd)

  - But it looks like a shift register if you look at it right



Median filter FSM (cont'd)

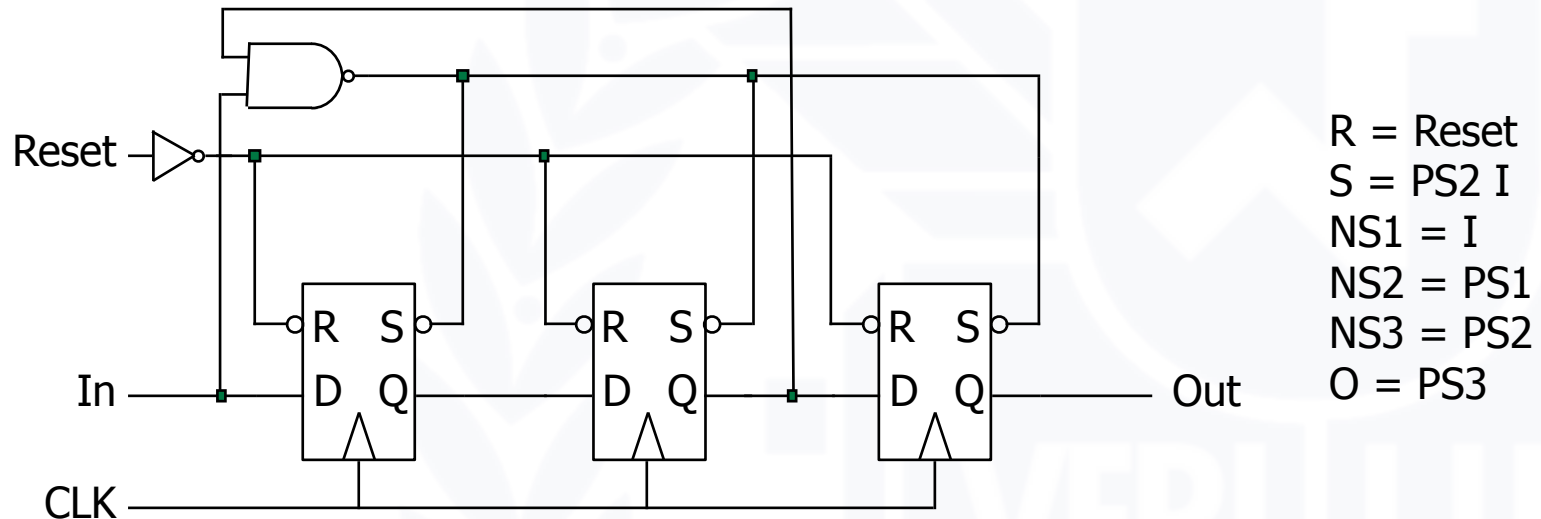
- An alternate implementation with S/R FFs
- Personally I do not recommend this!



- 💡 The set input (S) does the median filter function by making the next state 111 whenever the input is 1 and PS2 is 1 (1 input to state x1x)

FSM implementation with a shift register

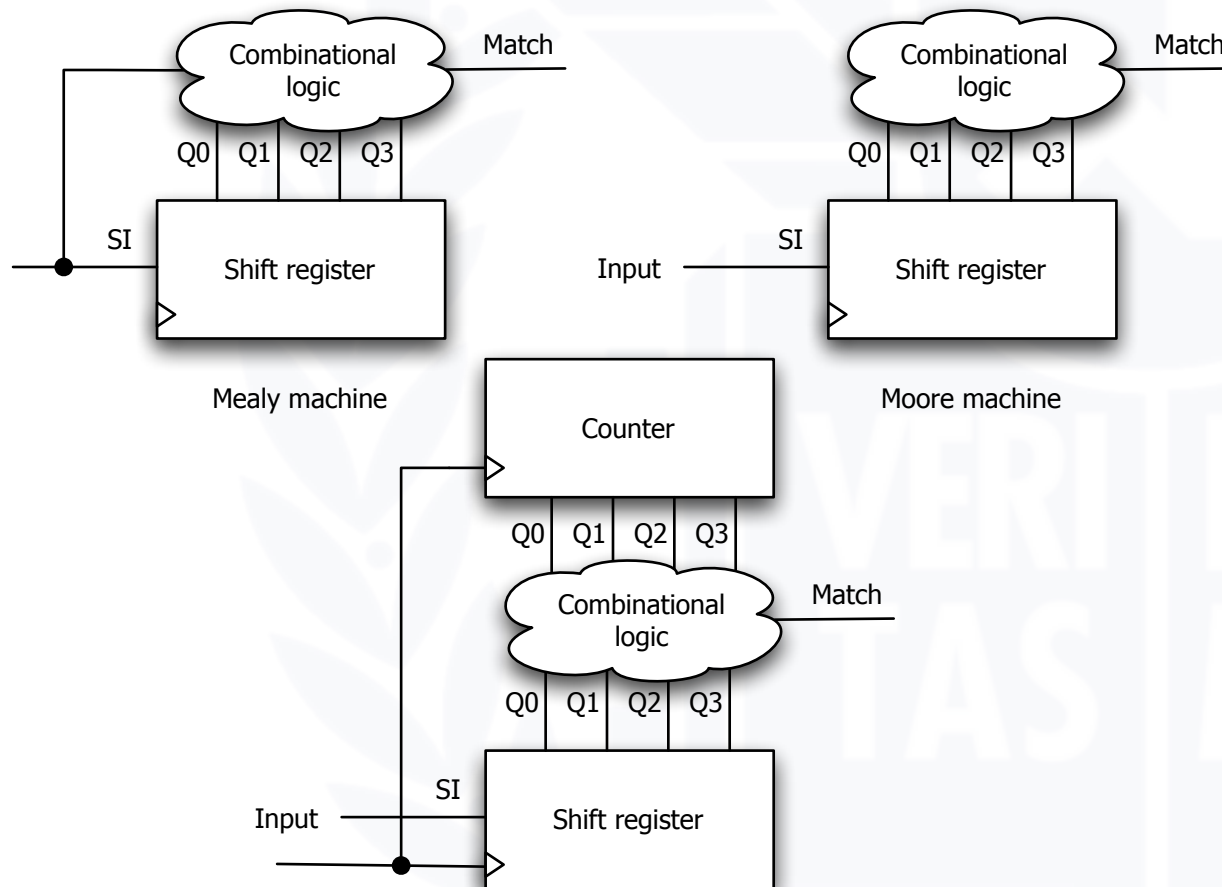- String recognizer
 - Good candidate for a shift register implementation




FSM implementation with a counter

- Three functions of a counter
 - Count
 - Reset
 - Jump
- State machine implementation with a counter
 - Next state function
 - Count (CNT), Reset (R) and Load (LD)
- Sequencer

Input/Current State								Next State				Output							
I0	I1	I2	I3	Q	Q	Q	Q	Q	Q	Q	Q	LD*	R*	EN*	A	B	C	D	E


FSM implementation with a ROM

 - PS + FSM input
- Address input
- NS
- Data output
- Input synchronization is applied here
- Both Moore and Mealy machines can be implemented
- Advantage and disadvantages?
 - Same to the combinational logic implementation with a ROM



FSM implementation using PALs

 - Programmable logic building block for sequential logic
 - Aacro-cell: FF + logic
 - D-FF
 - Two-level logic capability like PAL (e.g., 8 product terms)




Vending machine example (Moore PLD mapping)

D0 = $\text{reset}'(Q0'N + Q0N' + Q1N + Q1D)$


D1 = $\text{reset}'(Q1 + D + Q0N)$

OPEN = $Q1Q0$

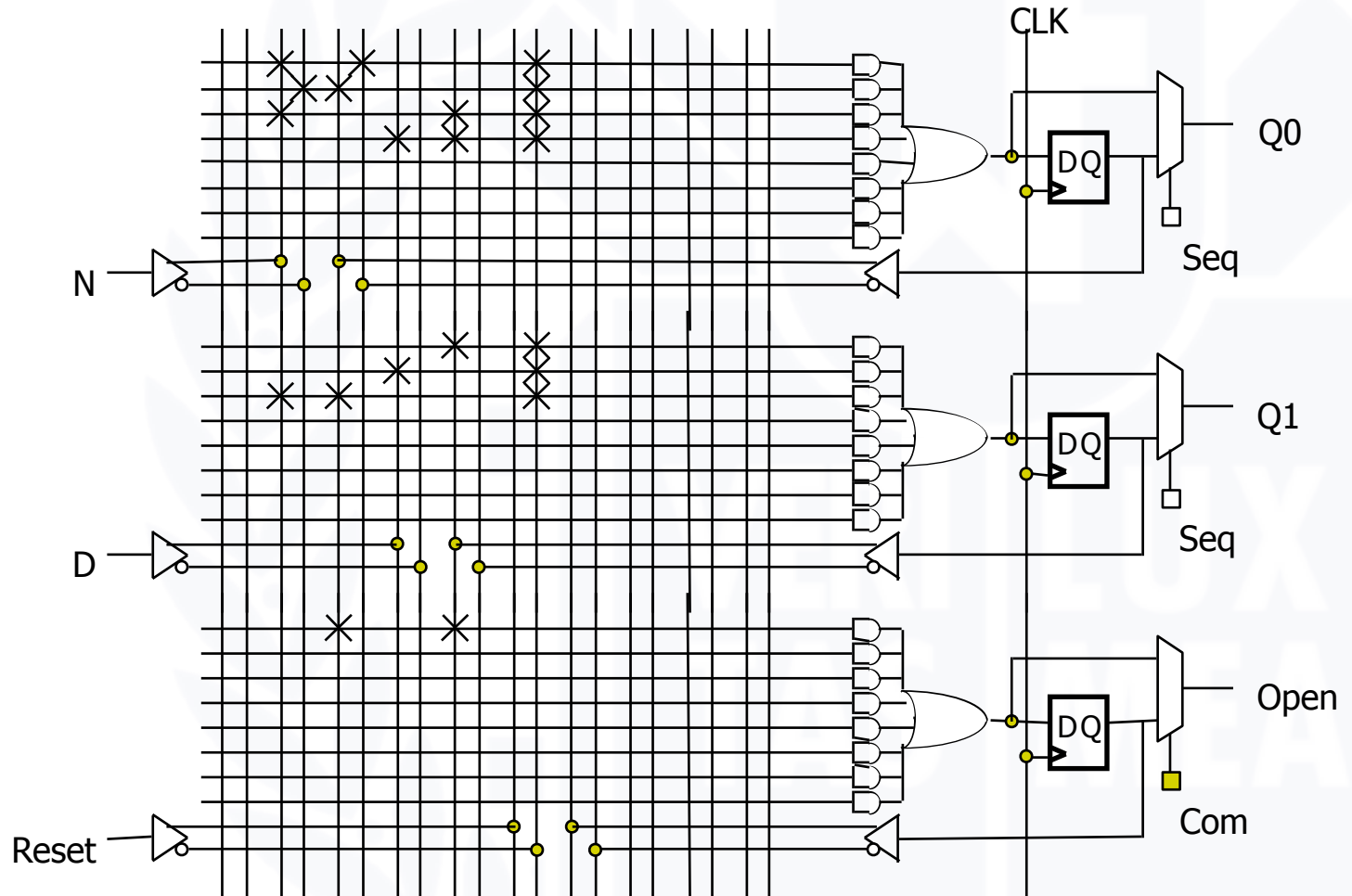

Vending machine (synch. Mealy PLD mapping)

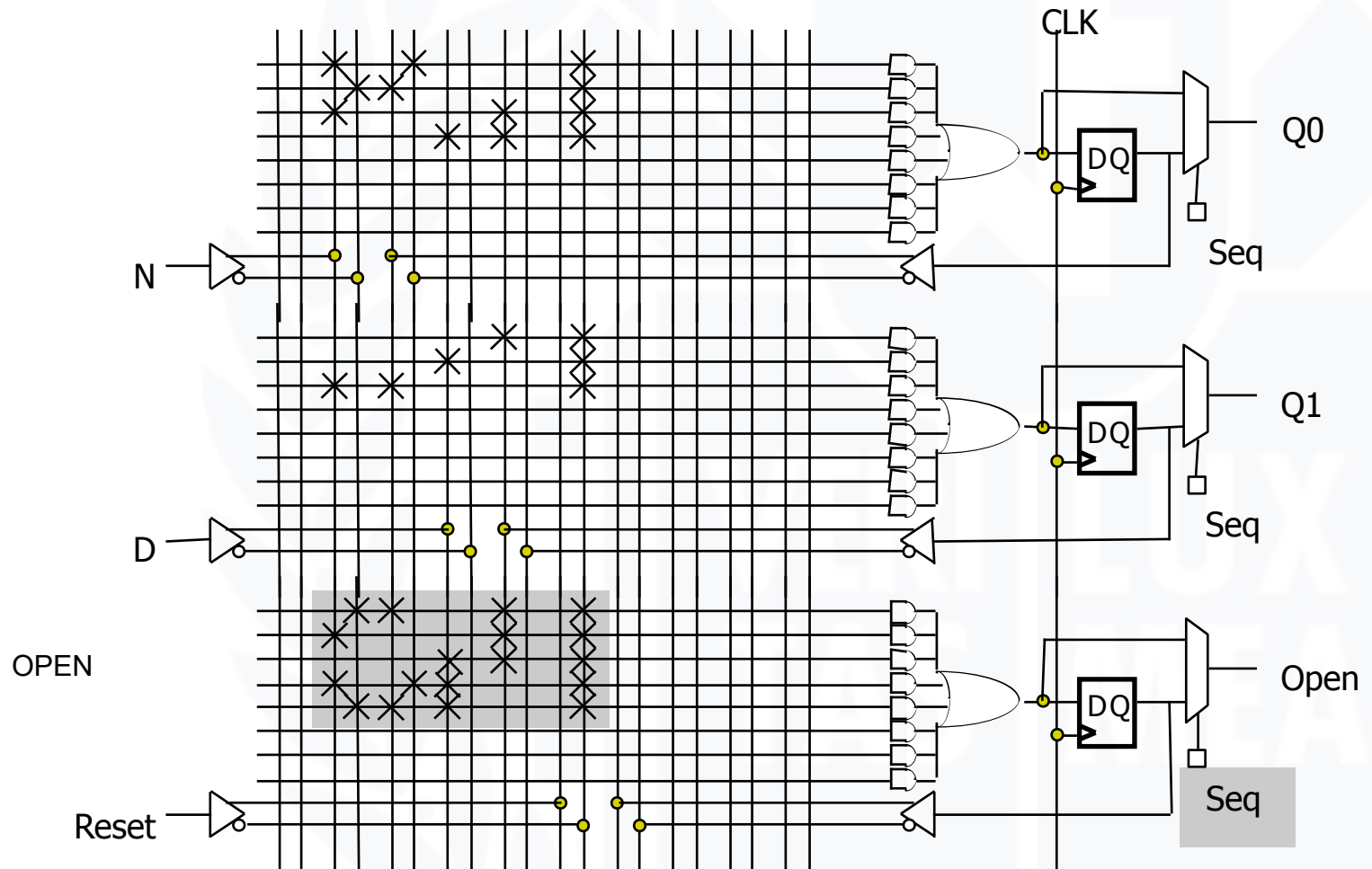
$$\text{OPEN} = \text{reset}'(Q1Q0N' + Q1N + Q1D + Q0'ND + Q0N'D)$$



22V10 PAL


- Combinational logic elements (SoP)
- Sequential logic elements (D-FFs)
- Up to 10 outputs
- Up to 10 FFs
- Up to 22 inputs

Functional Logic Diagram for PALC22V10D

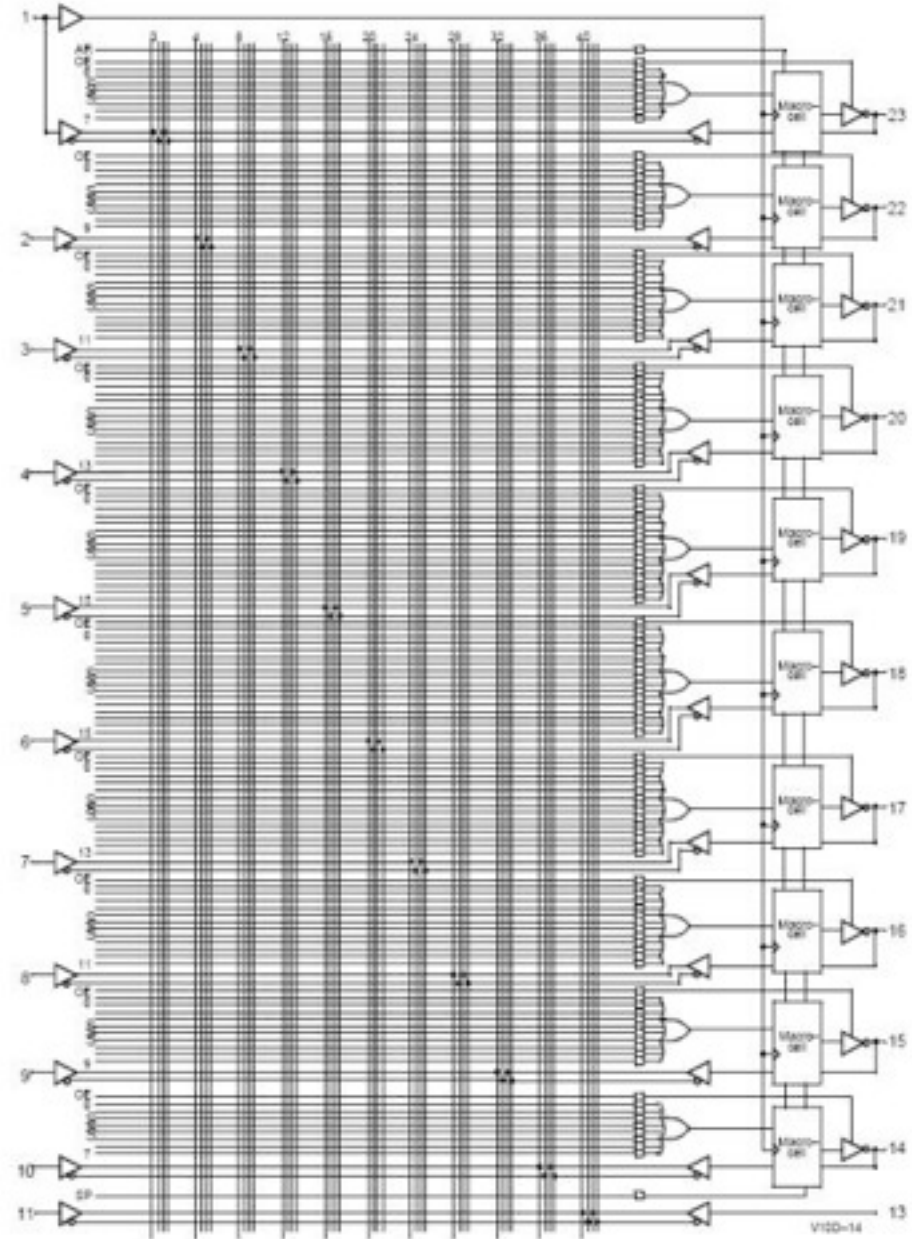


22V10 PAL macro cell

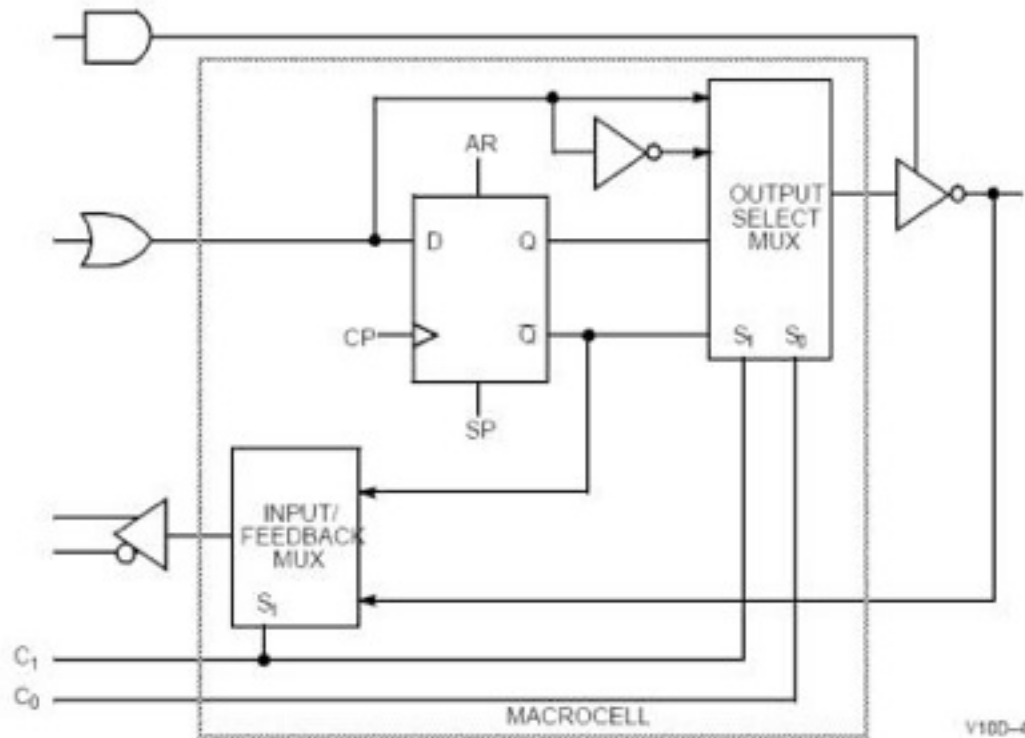- Sequential logic element + output/input selection




FSM implementation with an FPGA

Altera MAX 3000 CPLD architecture

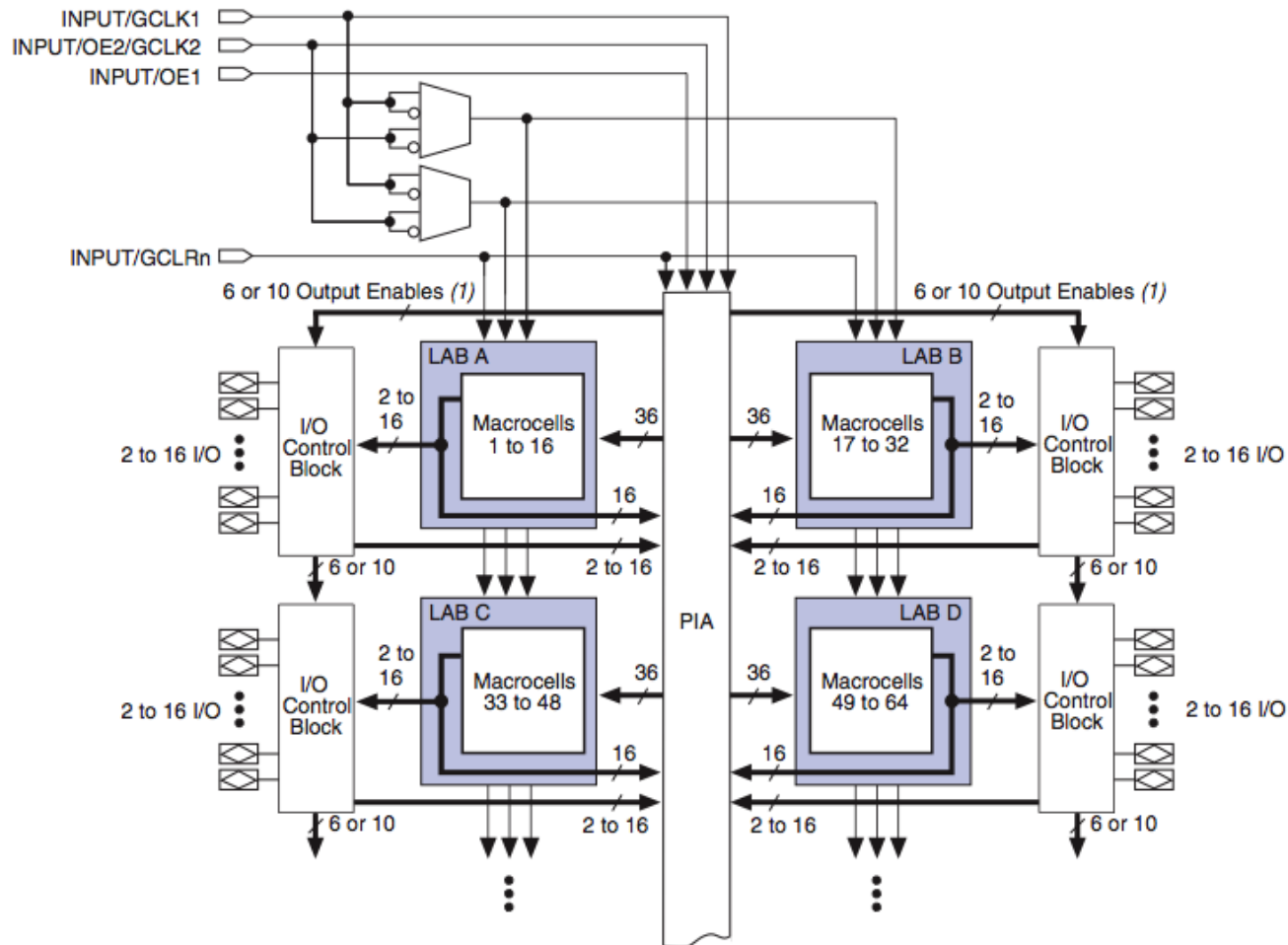


FSM implementation with an FPGA

- Altera MAX 3000 CPLD macrocell

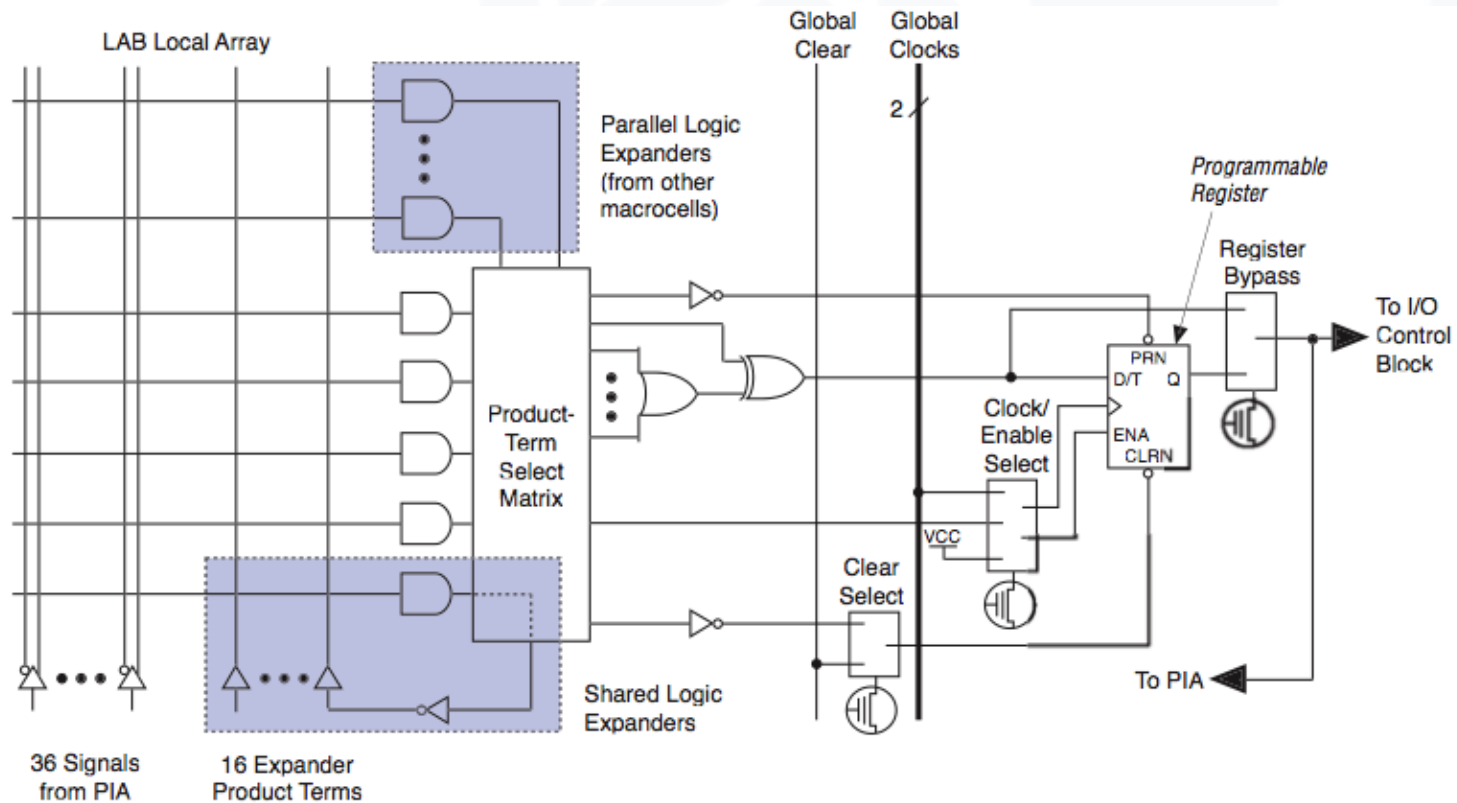

- Xilinx Vertex-5 slice

 


Example: traffic light controller

- A busy highway is intersected by a little used farmroad
- Detectors C sense the presence of cars waiting on the farmroad
 - With no car on farmroad, light remain green in highway direction
 - If vehicle on farmroad, highway lights go from Green to Yellow to Red, allowing the farmroad lights to become green
 - These stay green only as long as a farmroad car is detected but never longer than a set interval
 - When these are met, farm lights transition from Green to Yellow to Red, allowing highway to return to green
 - Even if farmroad vehicles are waiting, highway gets at least a set interval as green
- Assume you have an interval timer that generates:
 - A short time pulse (TS) and
 - A long time pulse (TL),
 - In response to a set (ST) signal.
 - TS is to be used for timing yellow lights and TL for green lights

Example: traffic light controller (cont')

- Highway/farm road intersection

 

Example: traffic light controller (cont')

- Tabulation of inputs and outputs


inputs	description	outputs	description
reset	place FSM in initial state	HG, HY, HR	assert green/yellow/red highway lights
C	detect vehicle on the farm road	FG, FY, FR	assert green/yellow/red highway lights
TS	short time interval expired	ST	start timing a short or long interval
TL	long time interval expired		

- Tabulation of unique states – some light configurations imply others

state	description
HG	highway green (farm road red)
HY	highway yellow (farm road red)
FG	farm road green (highway red)
FY	farm road yellow (highway red)

Example: traffic light controller (cont')

- State diagram

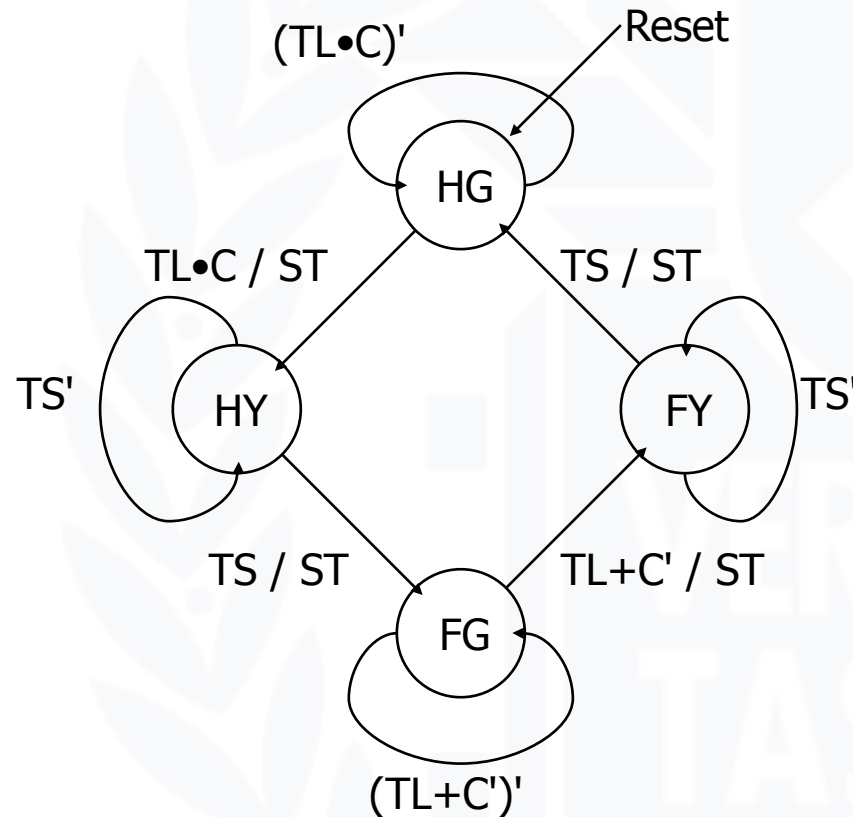

Example: traffic light controller (cont')

- Generate state table with symbolic states
- Consider state assignments

Output encoding – similar problem to state assignment
(Green = 00, Yellow = 01, Red = 10)

Inputs			Present State	Next State	Outputs		
C	TL	TS			ST	H	F
0	–	–	HG	HG	0	Green	Red
–	0	–	HG	HG	0	Green	Red
1	1	–	HG	HY	1	Green	Red
–	–	0	HY	HY	0	Yellow	Red
–	–	1	HY	FG	1	Yellow	Red
1	0	–	FG	FG	0	Red	Green
0	–	–	FG	FY	1	Red	Green
–	1	–	FG	FY	1	Red	Green
–	–	0	FY	FY	0	Red	Yellow
–	–	1	FY	HG	1	Red	Yellow

SA1:	HG = 00	HY = 01	FG = 11	FY = 10	
SA2:	HG = 00	HY = 10	FG = 01	FY = 11	
SA3:	HG = 0001	HY = 0010	FG = 0100	FY = 1000	(one-hot)

Logic for different state assignments

SA1

$$\begin{aligned}NS1 &= C \cdot TL' \cdot PS1 \cdot PS0 + TS \cdot PS1' \cdot PS0 + TS \cdot PS1 \cdot PS0' + C' \cdot PS1 \cdot PS0 + TL \cdot PS1 \cdot PS0 \\NS0 &= C \cdot TL \cdot PS1' \cdot PS0' + C \cdot TL' \cdot PS1 \cdot PS0 + PS1' \cdot PS0\end{aligned}$$

$$\begin{aligned}ST &= C \cdot TL \cdot PS1' \cdot PS0' + TS \cdot PS1' \cdot PS0 + TS \cdot PS1 \cdot PS0' + C' \cdot PS1 \cdot PS0 + TL \cdot PS1 \cdot PS0 \\H1 &= PS1 & H0 &= PS1' \cdot PS0 \\F1 &= PS1' & F0 &= PS1 \cdot PS0'\end{aligned}$$

SA2

$$\begin{aligned}NS1 &= C \cdot TL \cdot PS1' + TS' \cdot PS1 + C' \cdot PS1' \cdot PS0 \\NS0 &= TS \cdot PS1 \cdot PS0' + PS1' \cdot PS0 + TS' \cdot PS1 \cdot PS0\end{aligned}$$

$$\begin{aligned}ST &= C \cdot TL \cdot PS1' + C' \cdot PS1' \cdot PS0 + TS \cdot PS1 \\H1 &= PS0 & H0 &= PS1 \cdot PS0' \\F1 &= PS0' & F0 &= PS1 \cdot PS0\end{aligned}$$

SA3

$$\begin{aligned}NS3 &= C' \cdot PS2 + TL \cdot PS2 + TS' \cdot PS3 & NS2 &= TS \cdot PS1 + C \cdot TL' \cdot PS2 \\NS1 &= C \cdot TL \cdot PS0 + TS' \cdot PS1 & NS0 &= C' \cdot PS0 + TL' \cdot PS0 + TS \cdot PS3\end{aligned}$$

$$\begin{aligned}ST &= C \cdot TL \cdot PS0 + TS \cdot PS1 + C' \cdot PS2 + TL \cdot PS2 + TS \cdot PS3 \\H1 &= PS3 + PS2 & H0 &= PS1 \\F1 &= PS1 + PS0 & F0 &= PS3\end{aligned}$$

Sequential logic implementation summary

- Models for representing sequential circuits
 - Finite state machines and their state diagrams
 - Mealy, Moore, and synchronous Mealy machines
- Finite state machine design procedure
 - Deriving state diagram
 - Deriving state transition table
 - Assigning codes to states
 - Determining next state and output functions
 - Implementing combinational logic
- Implementation technologies
 - Random logic + FFs
 - PAL with FFs (programmable logic devices – PLDs)