

Digital Logic Design

4190.201

2014 Spring Semester

8. Finite State Machines

Naehyuck Chang
Dept. of CSE
Seoul National University
naehyuck@snu.ac.kr




Finite state machines

- Sequential circuits include
 - Primitive sequential elements (latches and FFs)
 - Combinational logic
- Models for representing sequential circuits
 - Finite-state machines (Moore and Mealy)
- Basic sequential circuits revisited
 - Shift registers
 - Counters
- Design procedure
 - State diagrams
 - State transition table
 - Next state functions
- Hardware description languages

What is state machine?

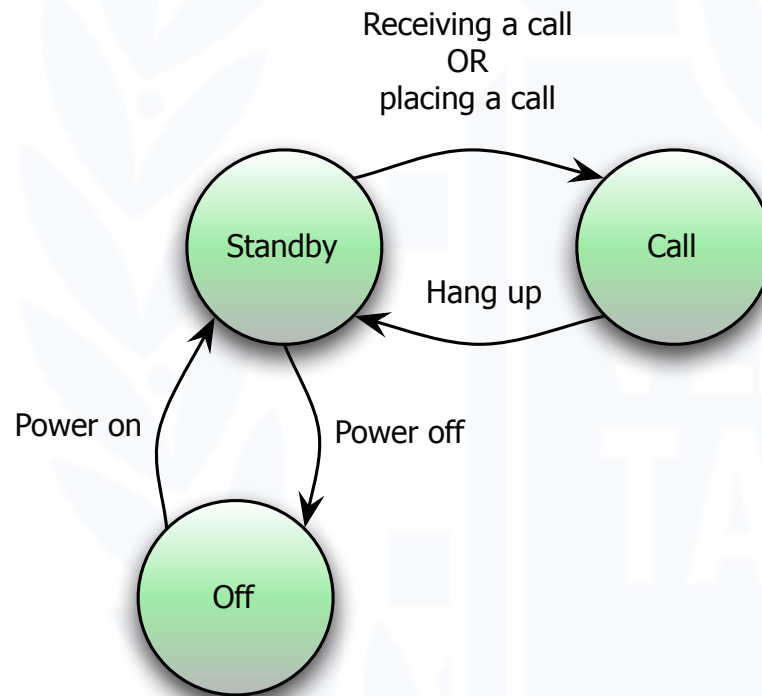- A state is a set of values measured at different parts of the circuit
 - RF amplifier is on/off, LCD is on/off, loudspeaker is on/off, etc.
- A state machine is a digital device that traverses through a predetermined sequence of states in an orderly fashion
- A synchronous state machine distinguishes state by the clock.




Finite state machines

- Asynchronous state machine
 - State transition occurs when an event occurs
 - Concept is natural
 - Hard and expensive to implement
 - Only one event occurs at a time
- Synchronous state machine
 - State transition occurs when a clock transition occurs
 - Concept is artificial
 - Easy and efficient to implement
 - More than two events may occur during a clock period
 - Appropriate priority is given
- Finite state machine
 - Number of states is finite


Finite state machines

 - Branch condition
- No overlapped condition
- No ambiguity




Finite state machines

 - Asynchronous state diagram
 - State machine remains forever in State 1 unless Start becomes active.




Finite state machines

 - Synchronous state machine
 - State transition has to be made in every clock cycle
 - The sum of branch conditions must to be 1
- We will deal with synchronous FSMs only




Finite state machines

 - Mealy model
 - Output is a function of the state and the input
- Moore model output
 - Output is a function of the state only




Moore model

 


Mealy model

Comparison of Mealy and Moore machines

Moore

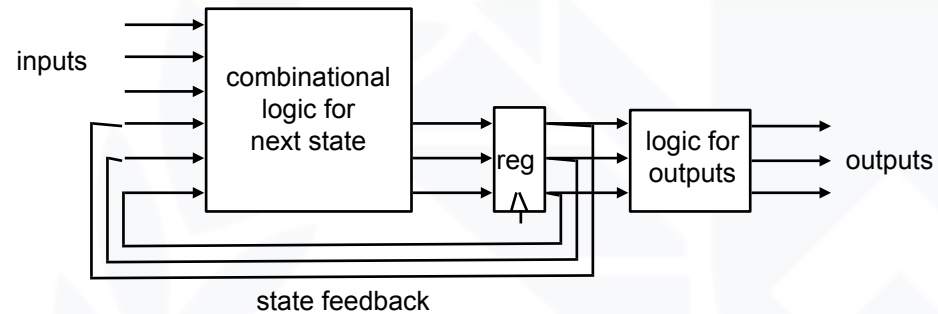


Mealy

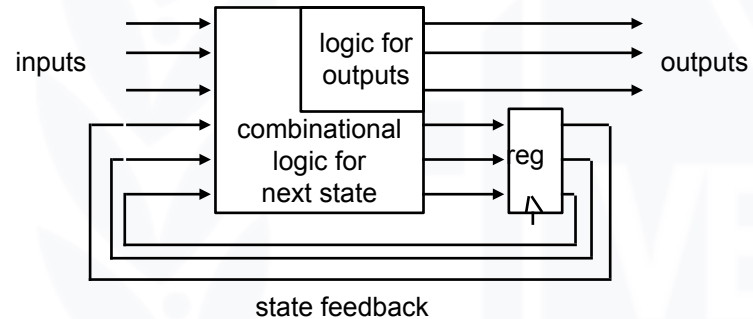



General state machine model

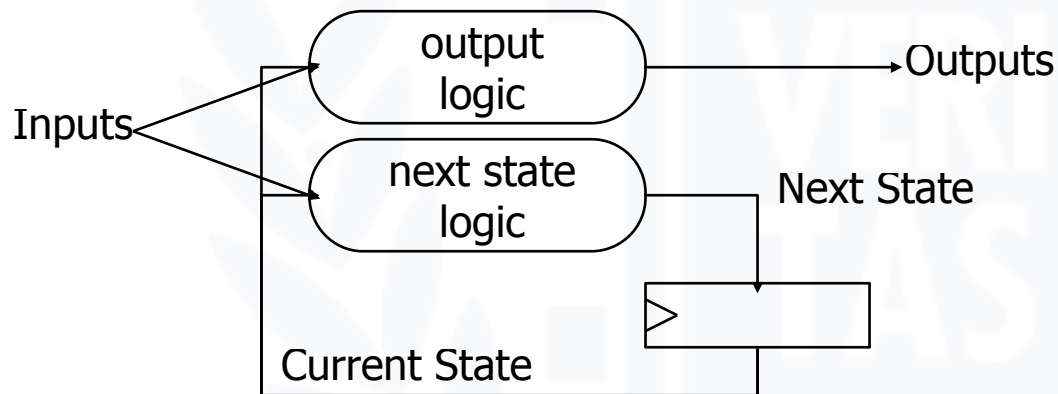- Values stored in registers represent the state of the circuit
- Combinational logic computes:
 - Next state
 - Function of current state and inputs
 - Outputs
 - Function of current state and inputs (Mealy machine)
 - Function of current state only (Moore machine)




State machine model (cont'd)

 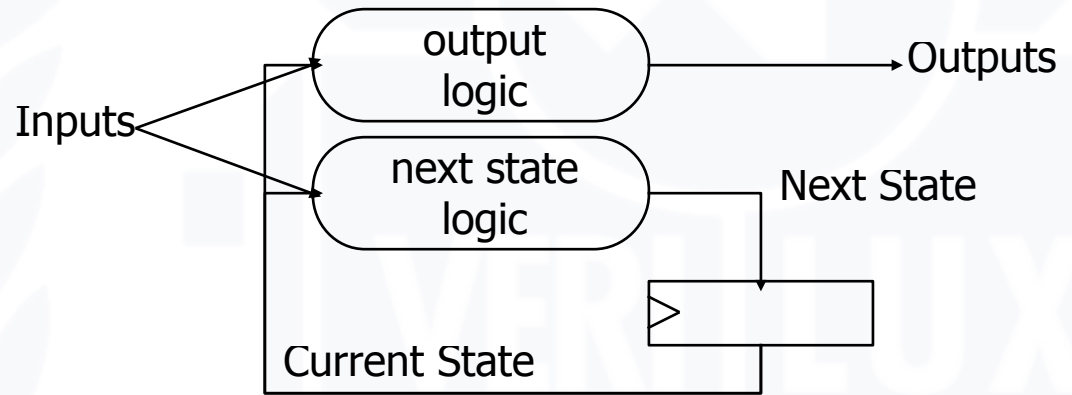- States: S_1, S_2, \dots, S_k
- Inputs: I_1, I_2, \dots, I_m
- Outputs: O_1, O_2, \dots, O_n
- Transition function: $F_s(S_i, I_j)$
- Output function: $F_o(S_i)$ or $F_o(S_i, I_j)$




Abstraction of state elements

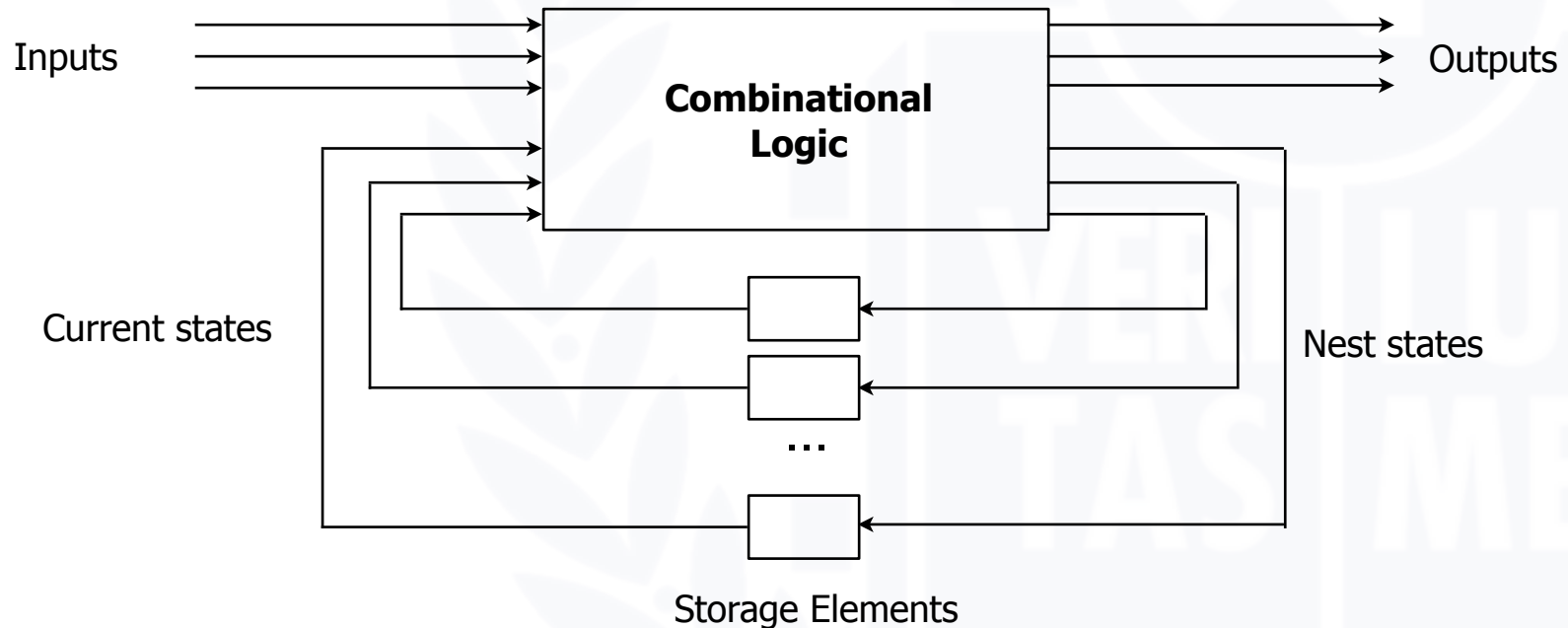- Divide circuit into combinational logic and state
- Feedback loops is isolated by FFs
 - Only the current state outputs affect the combination logic




Forms of sequential logic

 - Asynchronous sequential logic – state changes occur whenever state inputs change (elements may be simple wires or delay elements)
- Synchronous sequential logic – state changes occur in lock step across all storage elements (using a periodic waveform - the clock)



Asynchronous FSM

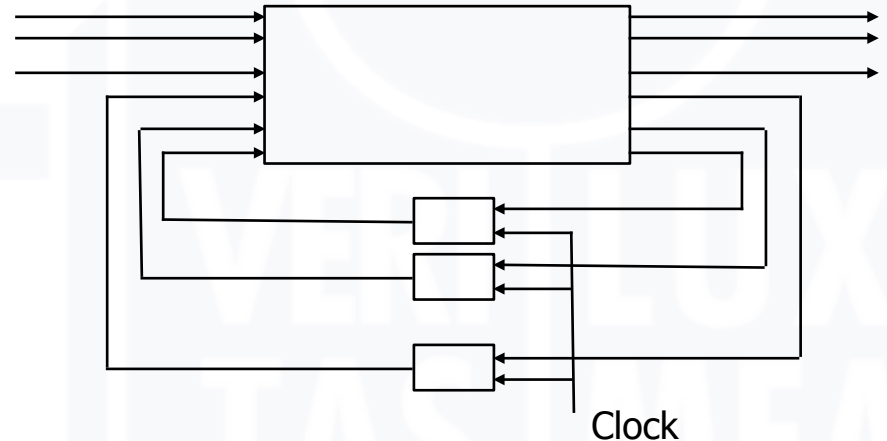


Synchronous FSM

FSM design procedure

- Start with counters
 - Simple because output is just state
 - Simple because no choice of next state based on input
- State diagram to state transition table
 - Tabular form of state diagram
 - Like a truth-table
- State encoding
 - Decide on representation of states
 - For counters it is simple: just its value
- Implementation
 - Flip-flop for each state bit
 - Combinational logic based on encoding

FSM design procedure: state diagram

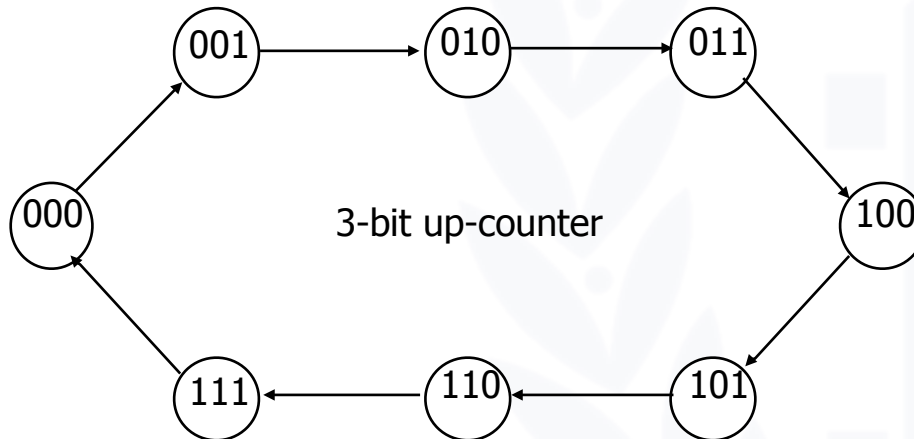- State transition table
 - Tabular form of state diagram
 - Like a truth-table (specify output for all input combinations)
 - Encoding of states: easy for counters – just use value



Present state		Next state	
0	000	001	1
1	001	010	2
2	010	011	3
3	011	100	4
4	100	101	5
5	101	110	6
6	110	111	7
7	111	000	0

FSM design procedure: state transition table

- Format of state transition table

Present State	Inputs	Next State	Outputs Generated
S0 – Sn	I0 – Im	S0 – Sn	O0 – Op

FSM design procedure: next state forming logic

- D flip-flop for each state bit
- Combinational logic based on encoding

C3	C2	C1	N3	N2	N1
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

$$N1 = C1'$$

$$N2 = C1C2' + C1'C2$$

$$= C1 \text{ xor } C2$$

$$N3 = C1C2C3' + C1'C3 + C2'C3$$

$$= (C1C2)C3' + (C1' + C2')C3$$

$$= (C1C2)C3' + (C1C2)'C3$$

$$= (C1C2) \text{ xor } C3$$

N3

			C3
	0	0	1
	0	1	1
C1	0	1	0
		C2	1

N2


			C3
	0	1	1
	0	0	0
C1	1	0	1
		C2	

N1

			C3
	1	1	1
	1	1	1
C1	0	0	0
		C2	

FSM design procedure: implementation

Implementation

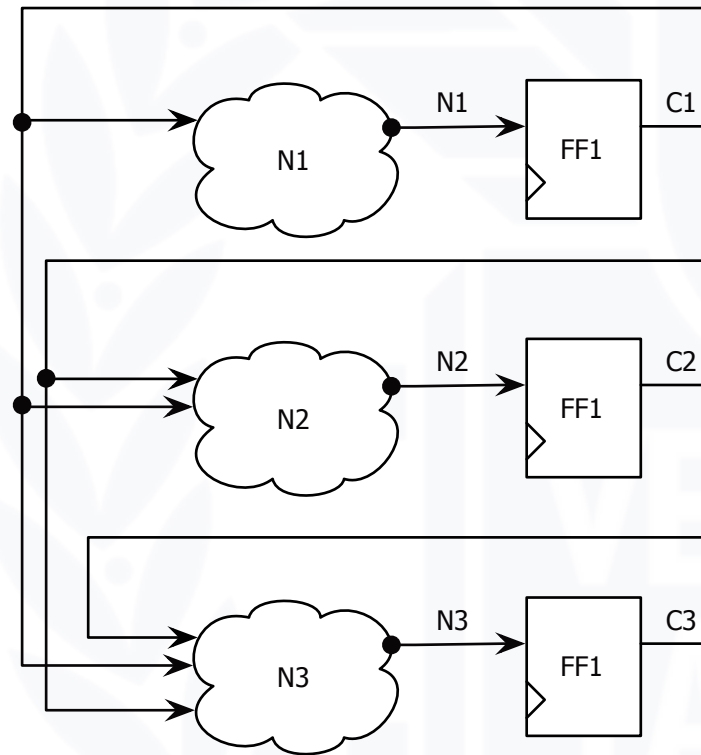


Quiz

- Design a clock-enable DFF with a primitive DFF
 - Draw a state transition diagram
 - Draw a state transition table
 - Derive the next state and output forming logics
 - Draw a schematic diagram


More FSM design examples

- Shift register
- Input determines next state

In	C1	C2	C3	N1	N2	N3
0	0	0	0	0	0	0
0	0	0	1	0	0	0
0	0	1	0	0	0	1
0	0	1	1	0	0	1
0	1	0	0	0	1	0
0	1	0	1	0	1	0
0	1	1	0	0	1	1
0	1	1	1	0	1	1
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	1	0	1
1	0	1	1	1	0	1
1	1	0	0	1	1	0
1	1	0	1	1	1	0
1	1	1	0	1	1	1
1	1	1	1	1	1	1

 


$N1 = In$
 $N2 = C1$
 $N3 = C2$

 


More FSM design examples

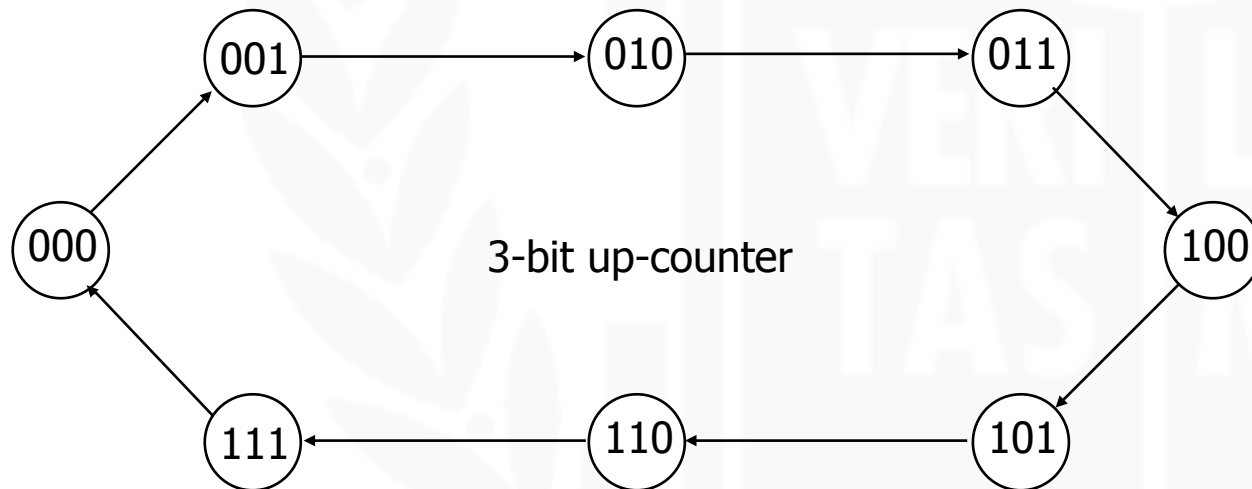- Counters
 - proceed through well-defined sequence of states in response to enable
- Many types of counters: binary, BCD, Gray-code
 - 3-bit up-counter: 000, 001, 010, 011, 100, 101, 110, 111, 000, ...
 - 3-bit down-counter: 111, 110, 101, 100, 011, 010, 001, 000, 111, ...





More FSM design examples

 - Counter
 - 3 flip-flops to hold state
 - Logic to compute next state
 - Clock signal controls when flip-flop memory can change
 - Wait long enough for combinational logic to compute new value
 - Don't wait too long as that is low performance



More FSM design examples

  - Self-starting counters
- Start-up states
 - At power-up, counter may be in an unused or invalid state
 - Designer must guarantee that it (eventually) enters a valid state
- Self-starting solution
 - Design counter so that invalid states eventually transition to a valid state
 - May limit exploitation of don't cares



More FSM design examples


- Re-deriving state transition table from don't care assignment

C+		C	
	0	0	0
	0	0	0
A	1	1	1
	B		

B+		C	
	1	1	0
	1	1	0
A	1	0	0
	B		


A+		C	
	0	1	0
	0	1	0
A	0	1	0
	B		

Present State			Next State		
C	B	A	C+	B+	A+
0	0	0	0	1	0
0	0	1	1	1	0
0	1	0	0	1	1
0	1	1	1	0	1
1	0	0	0	1	0
1	0	1	1	1	0
1	1	0	0	0	0
1	1	1	1	0	0

 

More FSM design examples

 - Complex counter
 - repeats 5 states in sequence
 - not a binary number representation
- Step 1: derive the state transition diagram
 - count sequence: 000, 010, 011, 101, 110
- Step 2: derive the state transition table from the state transition diagram



Present State			Next State		
C	B	A	C+	B+	A+
0	0	0	0	1	0
0	0	1	—	—	—
0	1	0	0	1	1
0	1	1	1	0	1
1	0	0	—	—	—
1	0	1	1	1	0
1	1	0	0	0	0
1	1	1	—	—	—

Note the don't care conditions that arise from the unused state codes

More FSM design examples

- Step 3: K-maps for next state functions

		C			
		0	0	0	X
A	C+	X	1	X	1
		B			

		C			
		1	1	0	X
A	B+	X	0	X	1
		B			

		C			
		0	1	0	X
A	A+	X	1	X	0
		B			


$$C+ \leq A$$

$$B+ \leq B' + A'C'$$


$$A+ \leq BC'$$

Comparison of Mealy and Moore machines


Moore

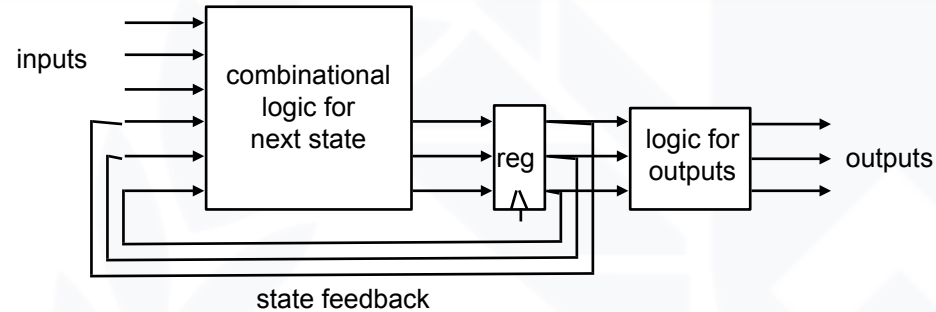

Mealy

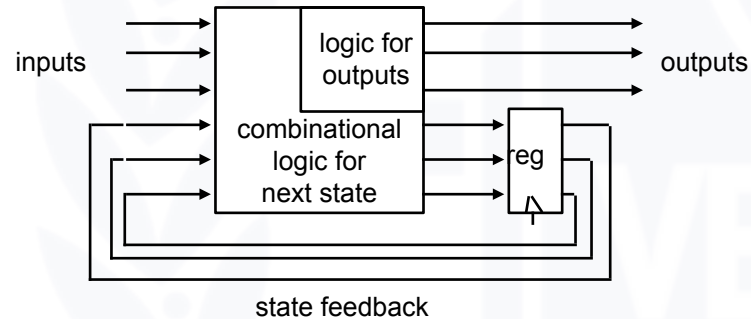


Synchronous Mealy

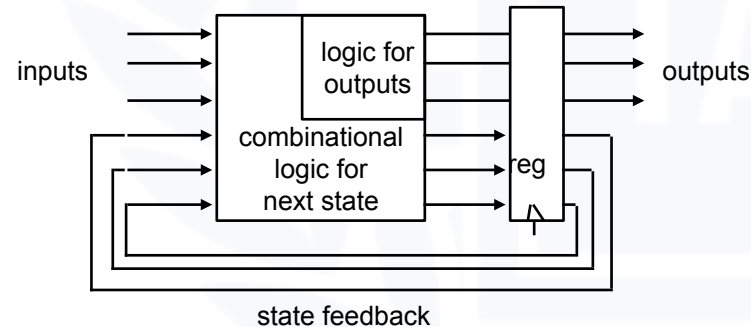

Comparison of Mealy and Moore machines

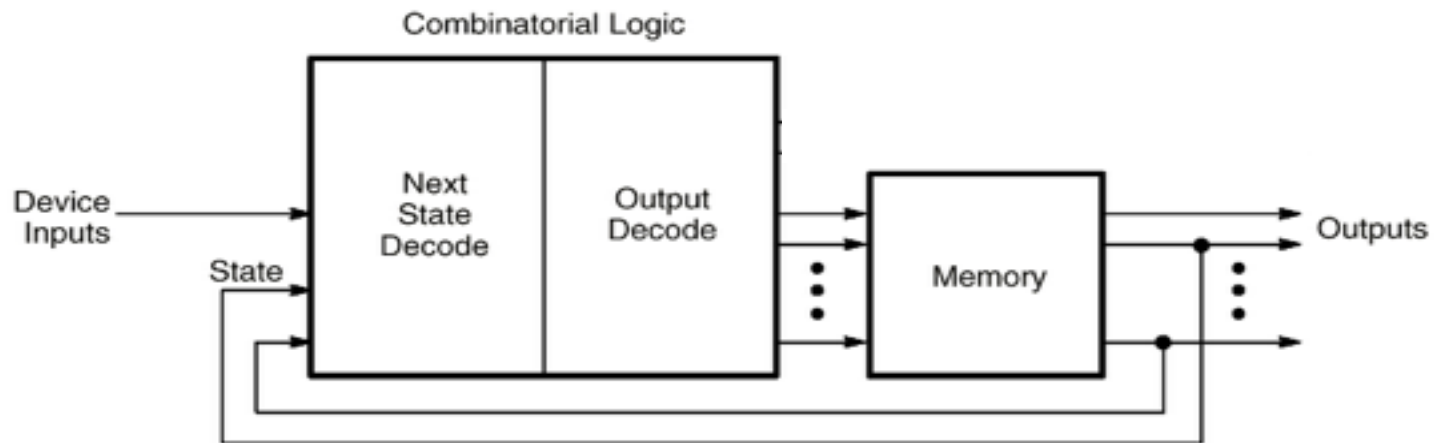- Basic model
 - Suitable for a single PAL implementation






Comparison of Mealy and Moore machines

- Mealy machines tend to have less states
 - Different outputs on arcs (n^2) rather than states (n)
- Moore machines are safer to use
 - Outputs change at clock edge (always one cycle later)
 - In Mealy machines, input change can cause output change as soon as logic is done – a big problem when two machines are interconnected – asynchronous feedback may occur if one isn't careful
- Mealy machines react faster to inputs
 - React in same cycle – don't need to wait for clock
 - In Moore machines, more logic may be necessary to decode state into outputs – more gate delays after clock edge


Mealy and Moore examples

   - Recognize $A, B = 0, 1$
 - Mealy or Moore?



Mealy and Moore examples (cont'd)

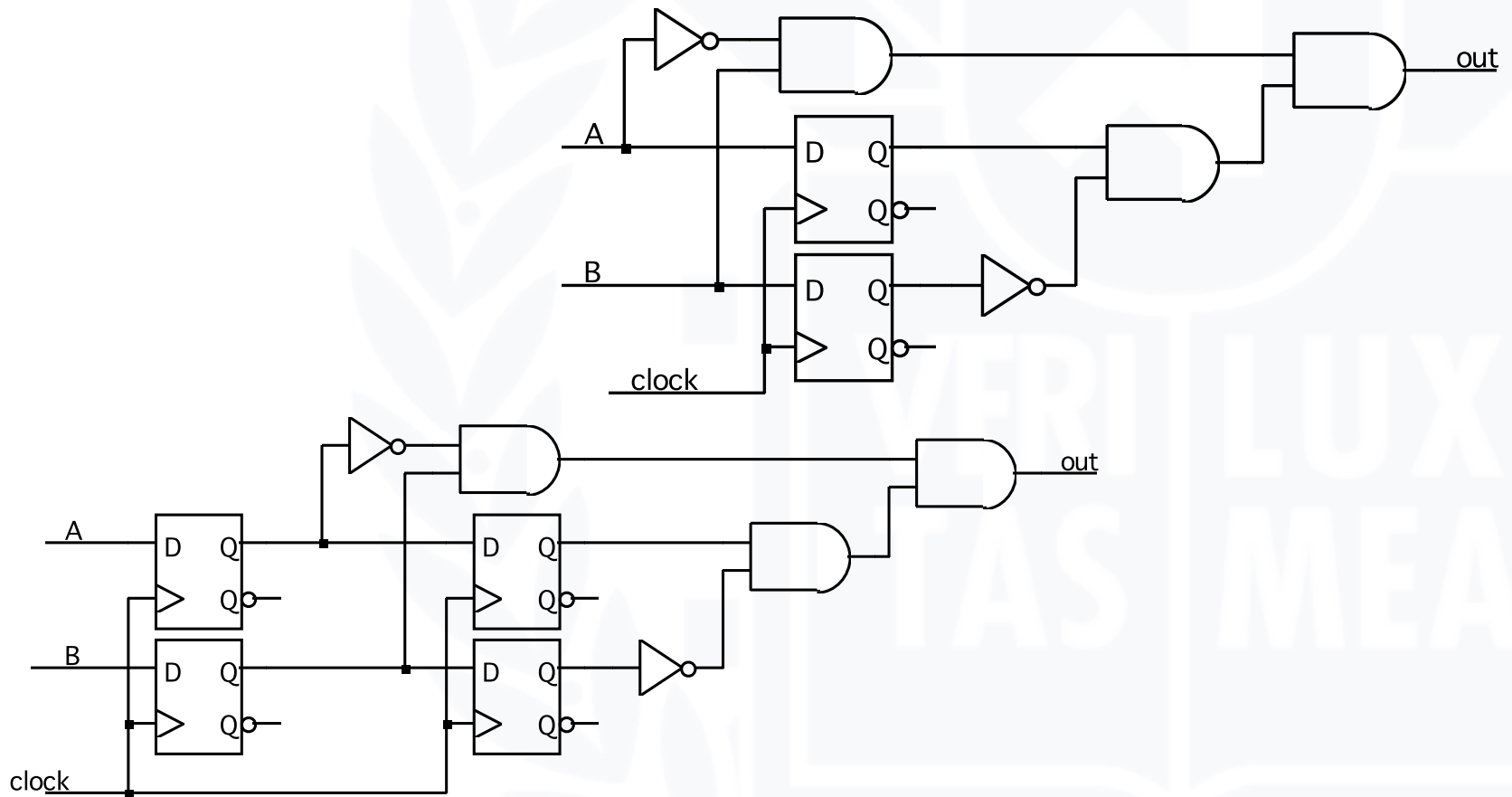- Recognize $A, B = 1, 0$ then $0, 1$
- Mealy or Moore?



State assignment


- State encoding
 - Identify each state by a unique name
- Non-redundant encoding
 - Binary encoding
 - Gray code encoding
- Redundant encoding
 - One-hot encoding
 - BCD encoding
 - Basic machine encoding

One-hot encoding

- Use of n -bit code for n states
 - S1: 0000000001
 - S2: 0000000010
 - S3: 0000000100
- Suitable for FPGA implementation
 - Use more FFs
 - Make the combination logic simpler
 - Less number of inputs
 - Even complicated FSM has limited number of previous states

Specifying outputs for a Moore machine

 
- Output is only function of state
 - Specify in state bubble in state diagram
 - Example: sequence detector for 01 or 10



reset	input	current state	next state	output
1	—	—	A	
0	0	A	B	0
0	1	A	C	0
0	0	B	B	0
0	1	B	D	0
0	0	C	E	0
0	1	C	C	0
0	0	D	E	1
0	1	D	C	1
0	0	E	B	1
0	1	E	D	1

Specifying outputs for a Mealy machine

 
- Output is function of state and inputs
 - Specify output on transition arc between states
 - Example: sequence detector for 01 or 10



reset	input	current state	next state	output
1	—	—	A	0
0	0	A	B	0
0	1	A	C	0
0	0	B	B	0
0	1	B	C	1
0	0	C	B	1
0	1	C	C	0


Registered Mealy machine (really Moore)

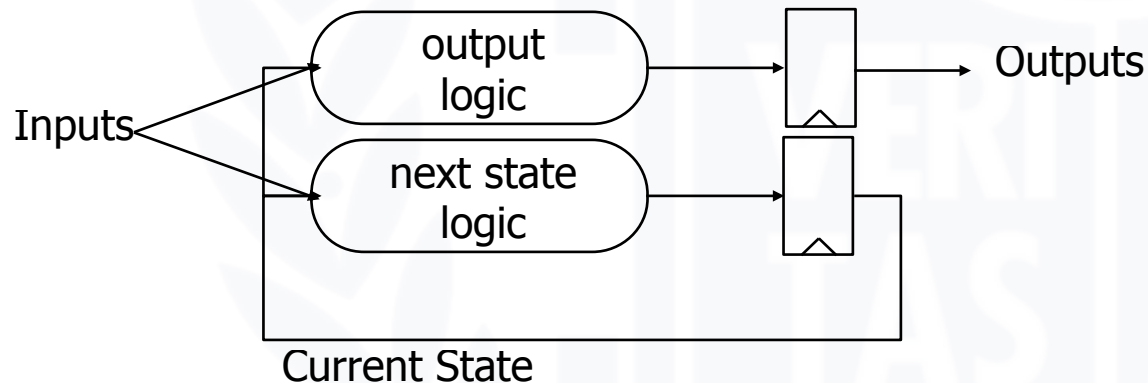- Synchronous (or registered) Mealy machine
 - Registered state AND outputs
 - Avoids 'glitchy' outputs
 - Easy to implement in PLDs
- Moore machine with no output decoding
 - Outputs computed on transition to next state rather than after entering
 - View outputs as expanded state vector




More complex example: vending machine

 - Release item after 15 cents are deposited
- Single coin slot for dimes, nickels
- No change




More complex example: vending machine

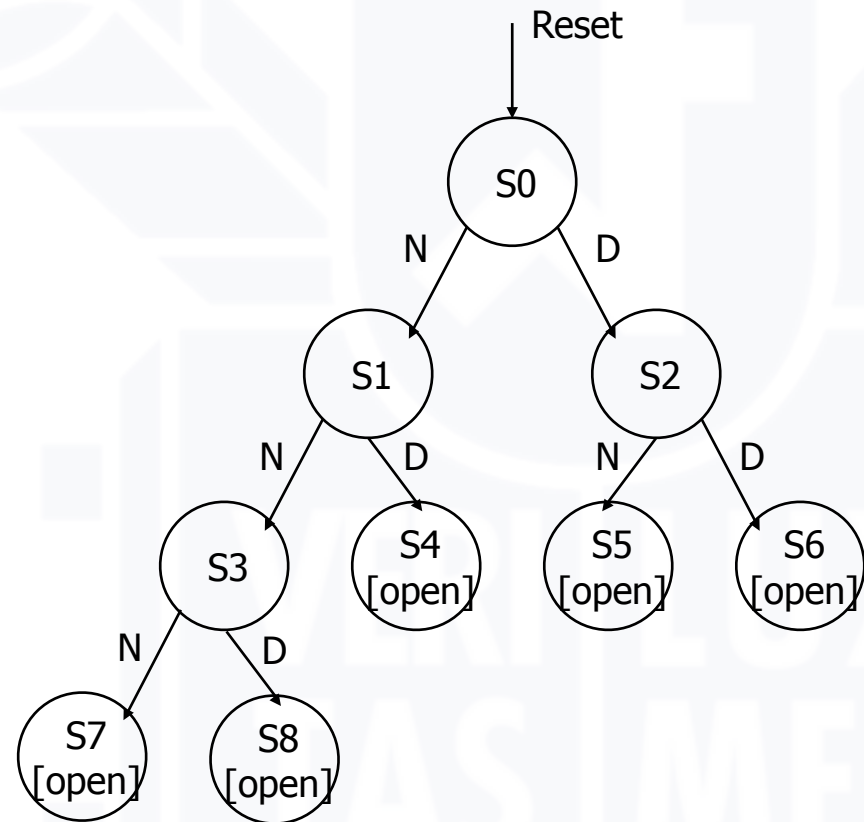- Suitable abstract representation
 - Tabulate typical input sequences:
 - 3 nickels
 - Nickel, dime
 - Dime, nickel
 - Two dimes
 - Draw state diagram:
 - Inputs: N, D, reset
 - Output: open chute
 - Assumptions:
 - Assume N and D asserted for one cycle
 - Each state has a self loop for $N = D = 0$ (no coin)



More complex example: vending machine

 - Minimize number of states - reuse states whenever possible



present state	inputs		next state	output open
	D	N		
0¢	0	0	0¢	0
	0	1	5¢	0
	1	0	10¢	0
	1	1	—	—
5¢	0	0	5¢	0
	0	1	10¢	0
	1	0	15¢	0
	1	1	—	—
10¢	0	0	10¢	0
	0	1	15¢	0
	1	0	15¢	0
	1	1	—	—
15¢	—	—	15¢	1

symbolic state table



More complex example: vending machine

- Uniquely encode states

present state		inputs		next state		output
Q1	Q0	D	N	D1	D0	open
0	0	0	0	0	0	0
		0	1	0	1	0
		1	0	1	0	0
		1	1	—	—	—
0	1	0	0	0	1	0
		0	1	1	0	0
		1	0	1	1	0
		1	1	—	—	—
1	0	0	0	1	0	0
		0	1	1	1	0
		1	0	1	1	0
		1	1	—	—	—
1	1	—	—	1	1	1

More complex example: vending machine

💡 Mapping to logic

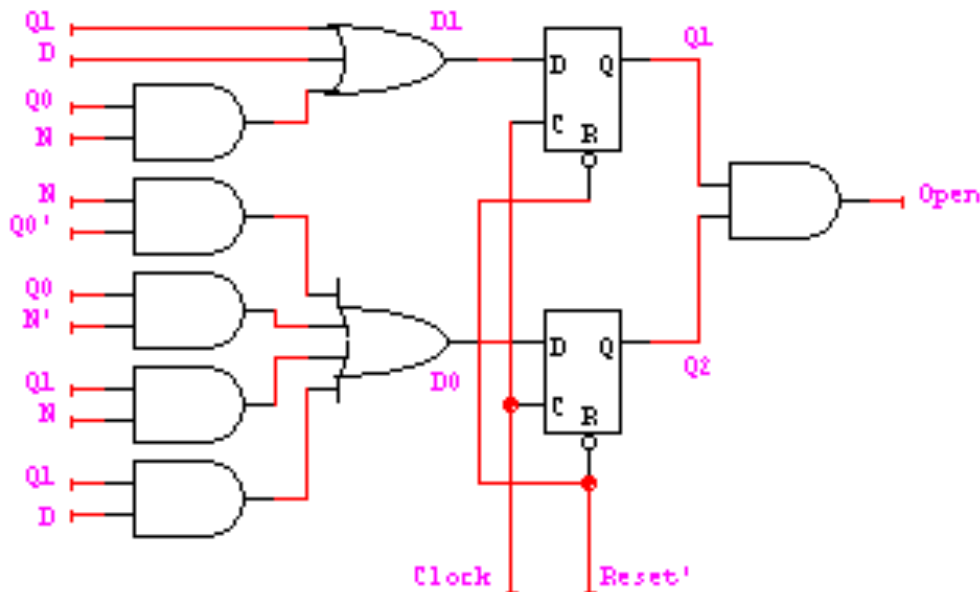 

$$D1 = Q1 + D + Q0 N$$

$$D0 = Q0' N + Q0 N' + Q1 N + Q1 D$$

OPEN = Q1 Q0

More complex example: vending machine

- One-hot encoding

present state				inputs		next state output				
Q3	Q2	Q1	Q0	D	N	D3	D2	D1	D0	open
0	0	0	1	0	0	0	0	0	1	0
				0	1	0	0	1	0	0
				1	0	0	1	0	0	0
				1	1	-	-	-	-	-
0	0	1	0	0	0	0	0	1	0	0
				0	1	0	1	0	0	0
				1	0	1	0	0	0	0
				1	1	-	-	-	-	-
0	1	0	0	0	0	0	1	0	0	0
				0	1	1	0	0	0	0
				1	0	1	0	0	0	0
				1	1	-	-	-	-	-
1	0	0	0	-	-	1	0	0	0	1

$$D0 = Q0 D' N'$$

$$D1 = Q0 N + Q1 D' N'$$

$$D2 = Q0 D + Q1 N + Q2 D' N'$$


$$D3 = Q1 D + Q2 D + Q2 N + Q3$$

$$OPEN = Q3$$

More complex example: vending machine


Moore machine

- Outputs associated with state

 


Mealy machine

- Outputs associated with transitions

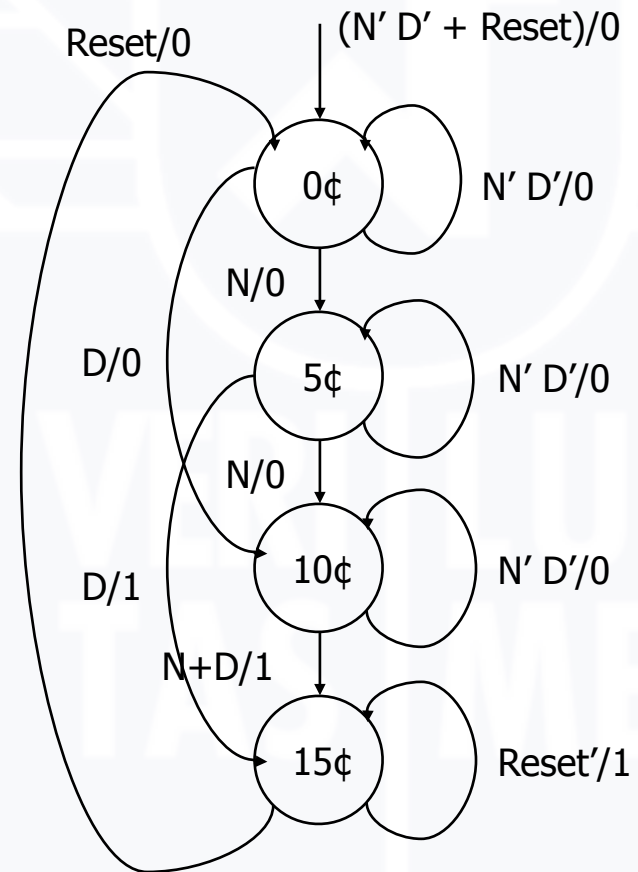

Example: Mealy implementation

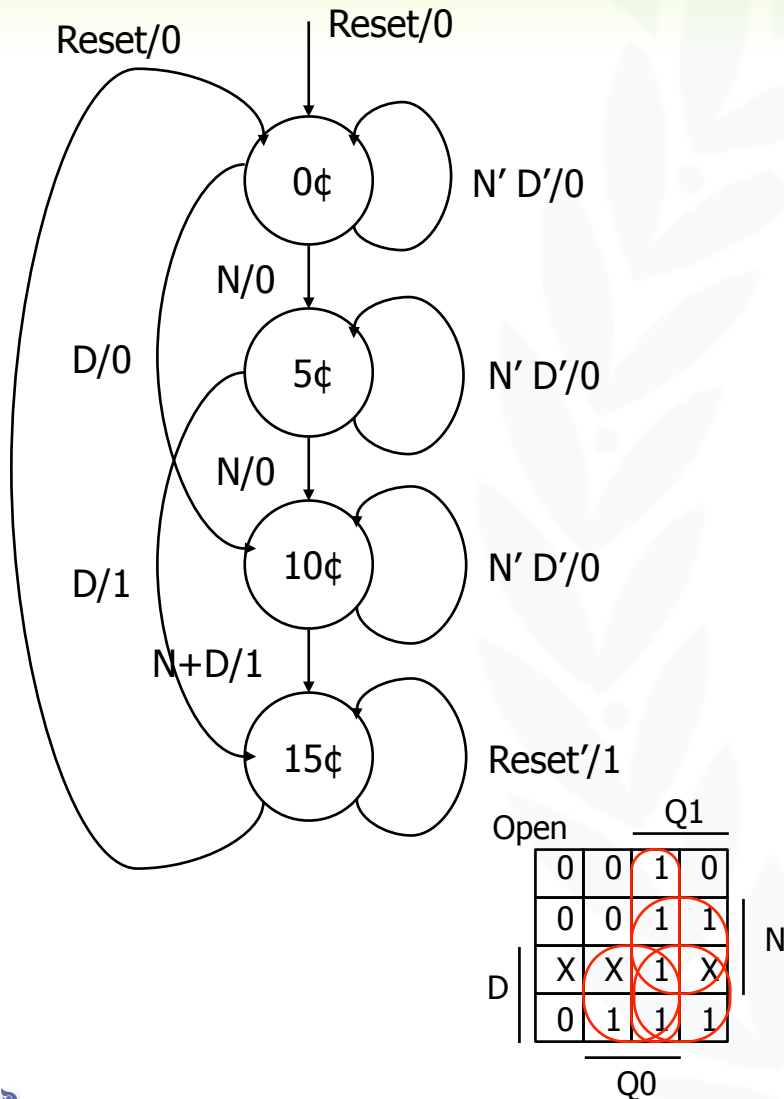

present state		inputs		next state		output
Q1	Q0	D	N	D1	D0	open
0	0	0	0	0	0	0
		0	1	0	1	0
		1	0	1	0	0
		1	1	—	—	—
0	1	0	0	0	1	0
		0	1	1	0	0
		1	0	1	1	1
		1	1	—	—	—
1	0	0	0	1	0	0
		0	1	1	1	1
		1	0	1	1	1
		1	1	—	—	—
1	1	—	—	1	1	1

$$D0 = Q0'N + Q0N' + Q1N + Q1D$$

$$D1 = Q1 + D + Q0N$$

$$OPEN = Q1Q0 + Q1N + Q1D + Q0D$$


Example: Mealy implementation

$$D0 = Q0'N + Q0N' + Q1N + Q1D$$

$$D1 = Q1 + D + Q0N$$

$$OPEN = Q1Q0 + Q1N + Q1D + Q0D$$


 
Make sure OPEN is 0 when reset
– by adding AND gate



Vending machine: Moore to synch. Mealy


- OPEN = Q1Q0 creates a combinational delay after Q1 and Q0 change in Moore implementation
- This can be corrected by retiming, i.e., move flip-flops and logic through each other to improve delay
- $$\text{OPEN.d} = (Q1 + D + Q0N)(Q0'N + Q0N' + Q1N + Q1D)$$
  
$$= Q1Q0N' + Q1N + Q1D + Q0'ND + Q0N'D$$
- Implementation now looks like a synchronous Mealy machine
 - It is common for programmable devices to have FF at end of logic



Vending machine: Mealy to synch. Mealy

 - OPEN.d = $Q_1Q_0 + Q_1N + Q_1D + Q_0D$
- OPEN.d = $(Q_1 + D + Q_0N)(Q_0'N + Q_0N' + Q_1N + Q_1D)$
 $= Q_1Q_0N' + Q_1N + Q_1D + Q_0'ND + Q_0N'D$



Open.d


		Q1	
		0	1
		0	1
D	1	0	1
	0	1	1
		Q0	

N

Open.d


		Q1	
		0	1
		0	1
D	X	X	1
	0	1	1
		Q0	

N

 



Output synchronization

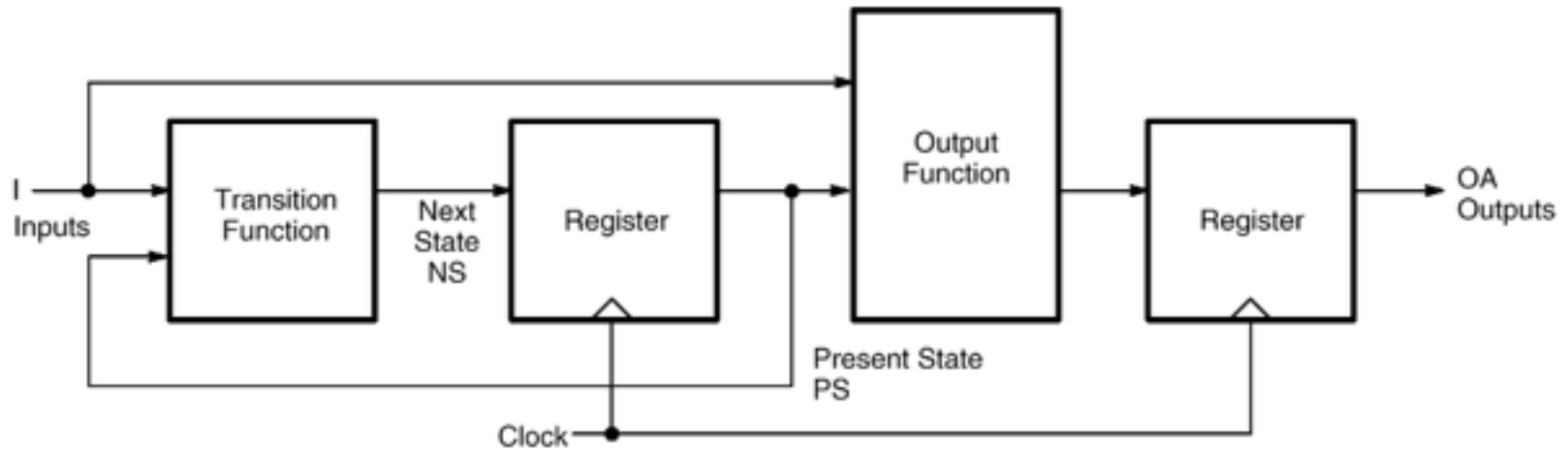- Prevent from glitch
- Increase output delay




Input synchronization

  - Prevent from timing fault
- Increase delay




Generic synchronous state machine


- I/O synchronization registers

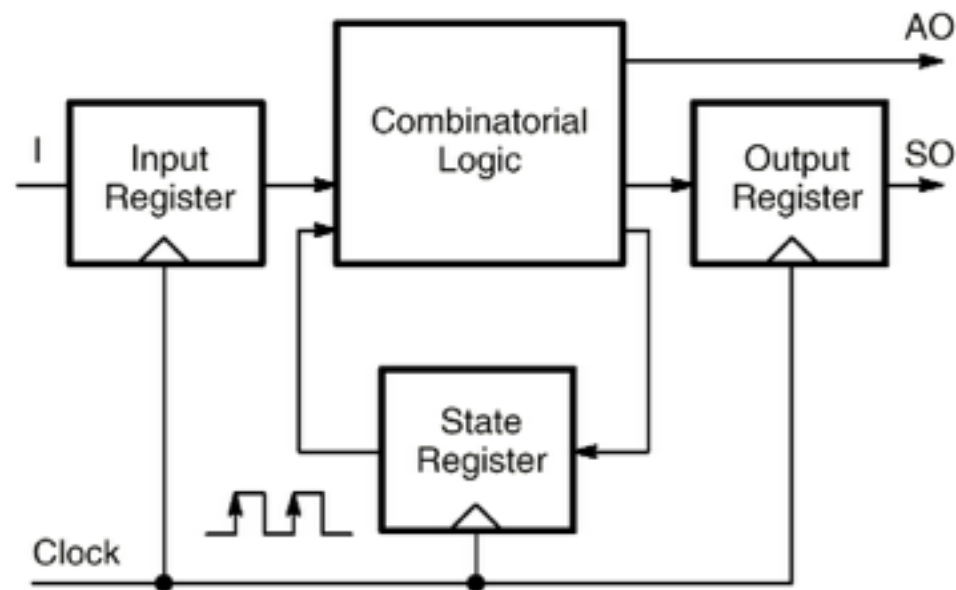

Timing diagram

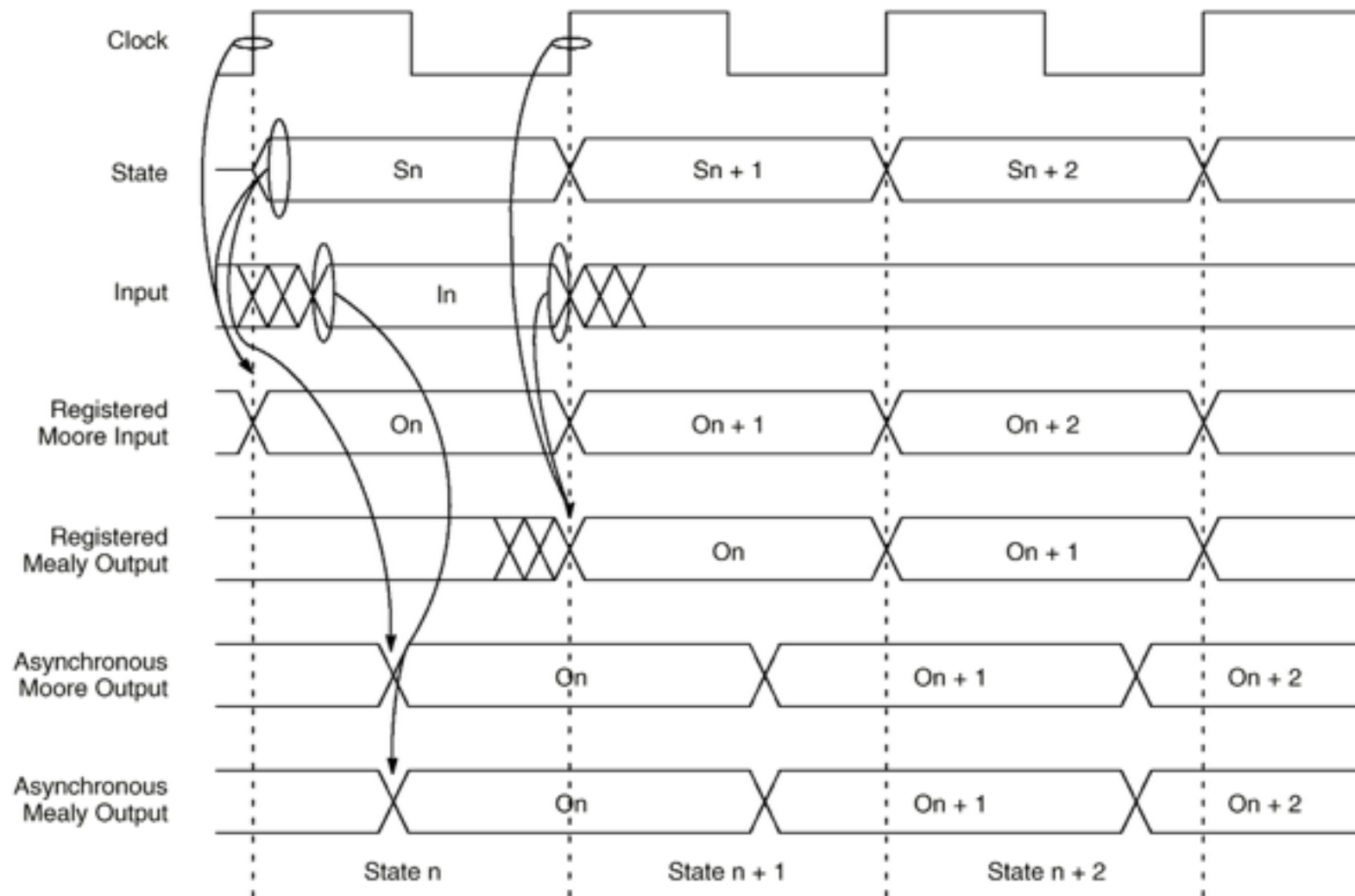


Maximum operating frequency

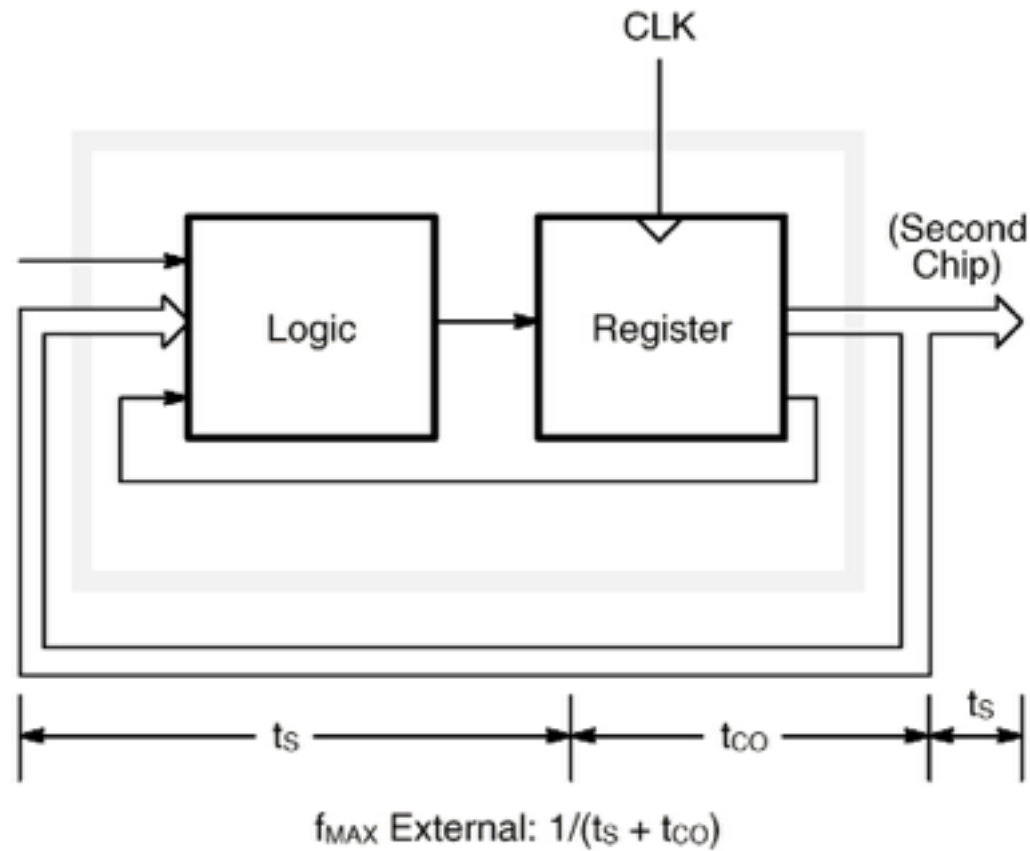


Clock skew

- Timing fault

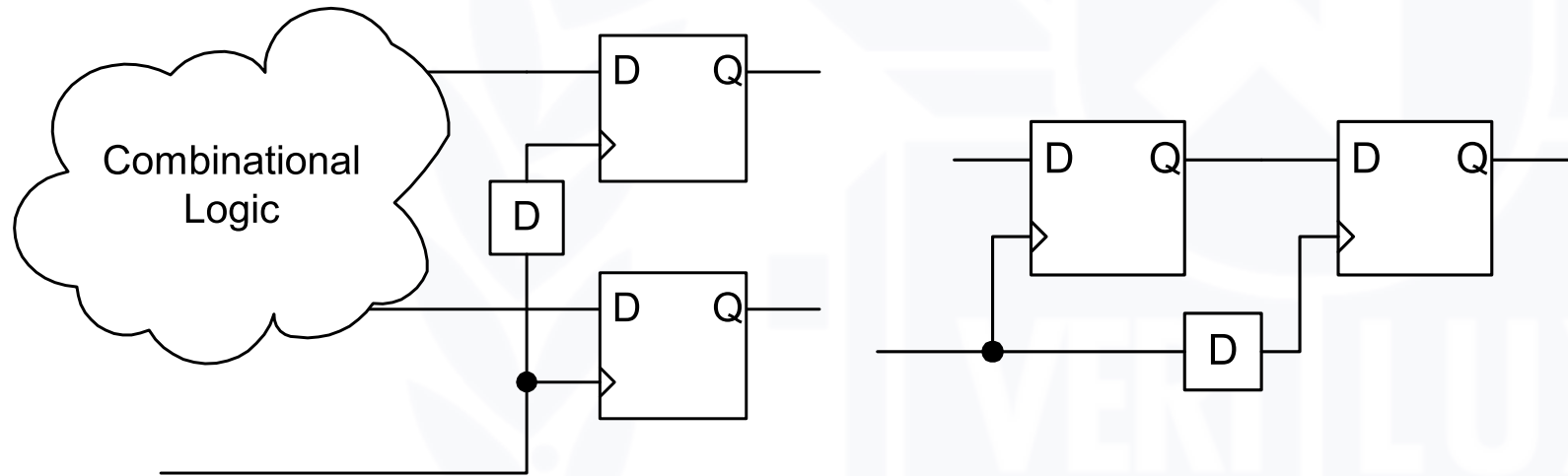

Clock skew (2)

 - Clock skew is caused by
 - Net delay
 - Artificial delay



Finite state machines summary

- Models for representing sequential circuits
 - Abstraction of sequential elements
 - Finite state machines and their state diagrams
 - Inputs/outputs
 - Mealy, Moore, and synchronous Mealy machines
- Finite state machine design procedure
 - Deriving state diagram
 - Deriving state transition table
 - Determining next state and output functions
 - Implementing combinational logic
- Hardware description languages